
DESIGN RECAP

SoP (ANDs-OR) → NAND
PoS (ORs-AND) → NOR

Given two unsigned numbers x and y, design a logic circuit to see

$$x \geq? y$$

Solution 1: $x - y$, if no last borrow

$$x \geq? y$$

Solution 2: logic circuit

$$x \geq? y$$

Solution 2: logic circuit

What is the range of x and y?

$$x \geq? y$$

Solution 2: logic circuit

What is the range of x and y?

$$x, y \in [0, 3]_{10}$$

Solution 2: logic circuit

What is the range of x and y?

$$x, y \in [0, 3]_{10} = [00, 11]_2$$

Solution 2: logic circuit

What is the range of output?

$$F \in \{0, 1\}$$

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=?
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=Σ m(0,1,2,3,5,6,7,10,11,15)
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=Π M(4,8,9,12,13,14)
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Y2	Y1	X2	X1	$F(Y2, Y1, X2, X1) = \sum m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y2, Y1, X2, X1) = \prod M(4, 8, 9, 12, 13, 14)$
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	1	1

Which design?

Which design?

SoP and PoS are both effective

SoP and PoS have same efficiency (2-levels)


Which design?

Cost: How many gates in SoP vs. PoS?

	$F(Y_2, Y_1, X_2, X_1) = \Sigma m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$
AND	Each minterm one 4-input-AND	Each MAXTERM one 4-input-OR
OR	One final 10-input-OR	One final 6-input-AND
NOT	Doesn't Matter Much	Doesn't Matter Much

	$F(Y_2, Y_1, X_2, X_1) =$ $\Sigma m(0,1,2,3,5,6,7,10,11,15)$	$F(Y_2, Y_1, X_2, X_1) =$ $\Pi M(4,8,9,12,13,14)$
AND	$10 \times 4\text{-input-AND}$	$6 \times 4\text{-input-OR}$
OR	$10\text{-input-OR} = 3 \times 4\text{-input-OR}$	$6\text{-input-AND} = 2 \times 4\text{-input-AND}$
NOT	Doesn't Matter Much	Doesn't Matter Much

	$F(Y_2, Y_1, X_2, X_1) = \Sigma m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$
AND	$10 \times 4\text{-input-AND}$	$6 \times 4\text{-input-OR}$
OR	$10\text{-input-OR} = 3 \times 4\text{-input-OR}$	$6\text{-input-AND} = 2 \times 4\text{-input-AND}$
NOT	Doesn't Matter Much	Doesn't Matter Much

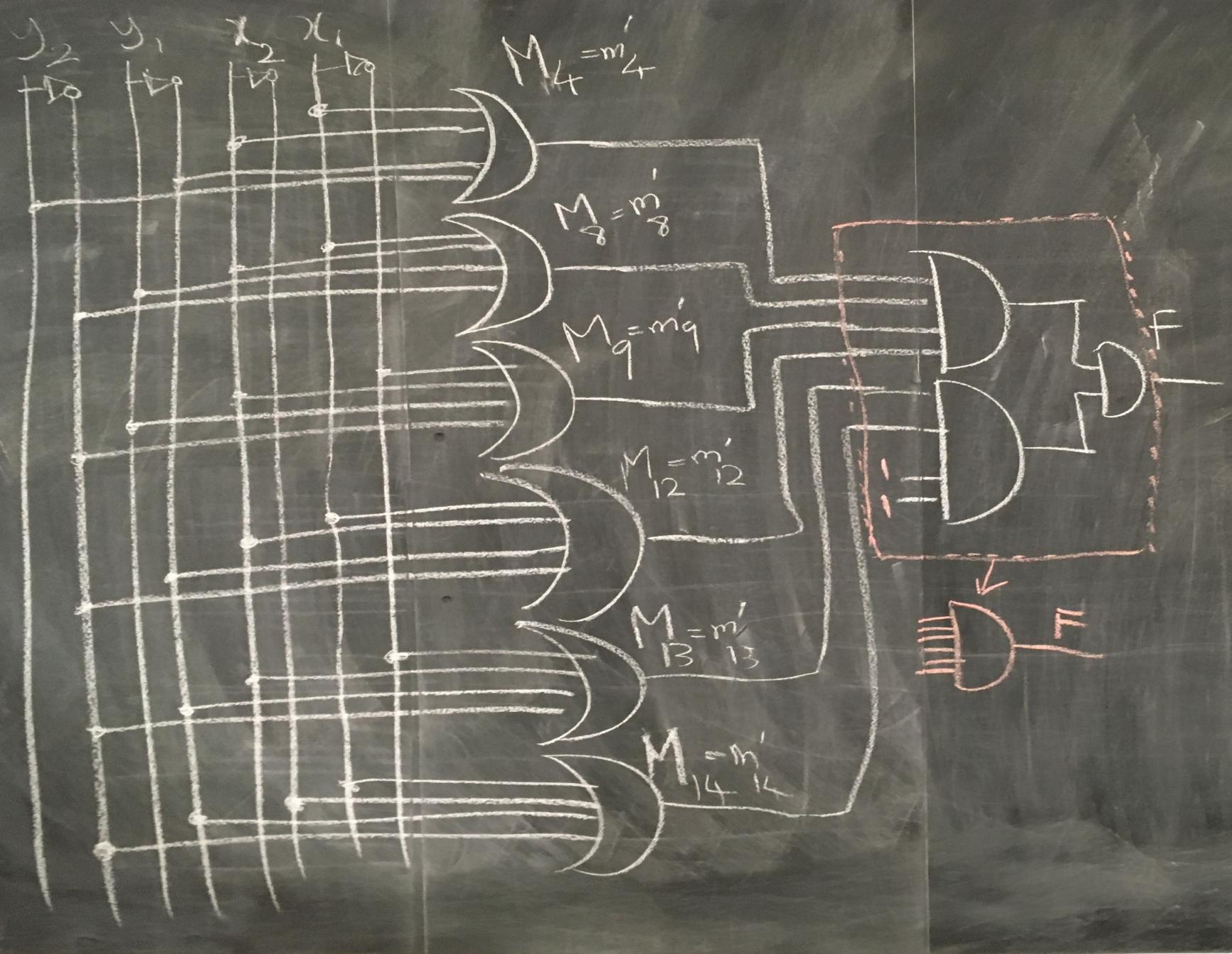

$$\begin{aligned}
 F &= \prod M(4, 8, 9, 12, 13, 14) \\
 &= M_4 M_8 M_9 M_{12} M_{13} M_{14} \\
 &= m'_4 m'_8 m'_9 m'_{12} m'_{13} m'_{14} \\
 &= (y'_2, x'_2, x'_1) \quad m'_4 \rightarrow y'_2 + x'_1 + x'_2, \\
 &\quad (y'_2, x'_2, x'_1) \quad m'_8 \rightarrow y'_2 + y'_1 + x'_1 + x'_2, \\
 &\quad (y'_2, x'_2, x'_1) \quad m'_9 \rightarrow y'_2 + y'_1 + x'_2 + x'_1, \\
 &\quad (y'_2, y'_1, x'_1) \quad m'_{12} \rightarrow y'_2 + y'_1 + x'_1 + x'_2, \\
 &\quad (y'_2, y'_1, x'_1) \quad m'_{13} \rightarrow y'_2 + y'_1 + x'_2 + x'_1, \\
 &\quad (y'_2, y'_1, x'_1) \quad m'_{14} \rightarrow y'_2 + y'_1 + x'_1 + x'_2
 \end{aligned}$$

$$F(Y_2, Y_1, X_2, X_1) = \Sigma m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$$

$$F(Y_2, Y_1, X_2, X_1) = \Pi M(4, 8, 9, 12, 13, 14)$$

NAND

$10 \times 4\text{-input-NAND}$

+


$1 \times 10\text{-input-NAND}$

NOR

$6 \times 4\text{-input-NOR}$

+

$1 \times 6\text{-input-NOR}$

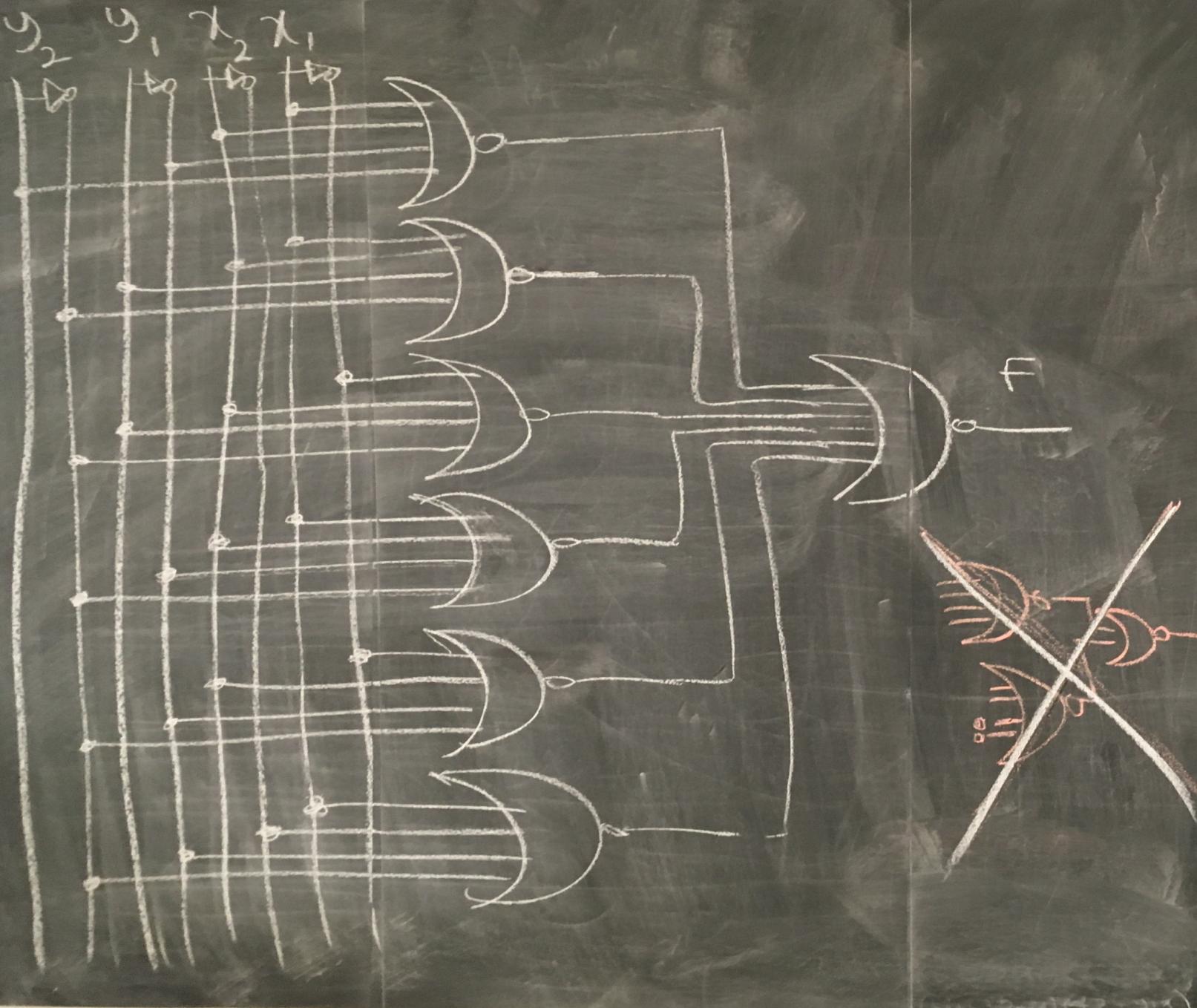

$$\begin{aligned}
 F &= \overline{\prod M(4, 8, 9, 12, 13, 14)} \\
 &= M_4 M_8 M_9 M_{12} M_{13} M_{14} \\
 F &= (F')' \\
 &= ((\overline{M_4 M_8 M_9 M_{12} M_{13} M_{14}}))' \\
 &= (\overline{M'_4 + M'_8 + M'_9 + M'_{12} + M'_{13} + M'_{14}})' \\
 &= ((y_2 + y_1) + x_2 + x_1)' + \\
 &\quad ((y'_2 + y_1) + x_2 + x_1)' + \\
 &\quad ((y_2 + y'_1) + x_2 + x_1)' + \\
 &\quad ((y_2 + y'_1) + x_2 + x_1)' + \\
 &\quad ((y'_2 + y_1) + x_2 + x_1)' + \\
 &\quad ((y'_2 + y_1) + x_2 + x_1)' + \\
 &\quad ((y'_2 + y'_1) + x_2 + x_1)'
 \end{aligned}$$

MINIMIZATION

aka. Simplification

MINIMIZATION

Number of Gates

Number of Inputs (2-input vs 4-input)

Number of Interconnections

Propagation Time

Cost of Gates

Circuit Area

...

A circuit may not satisfy all due to conflicting constraints!

MINIMIZATION

aka. Simplification

SoP (ANDs-OR) → Simplify → NAND
PoS (ORs-AND) → Simplify → NOR

MINIMIZATION

I) Boolean Algebra (algebraically)

MINIMIZATION

II) Map (Karnaugh map, K-map)

ALGEBRA

A set of elements

A set of operators

A set of axioms | postulates | assumptions | definitions

ALGEBRA

A set of elements: e.g.,

$$\{0,1\}$$

$$\{-1,0,1\}$$

$$\{1,2,3,4,\dots\}$$

$$\{\dots, -2, -1, 0, 1, 2, \dots\}$$

ALGEBRA

A set of operators

$$\{+, \times\}$$

$$\{+, -, \times, \div\}$$

$$\{\sim, \leq, \geq\}$$

ALGEBRA

Unary: !x, -x, x', ...

Binary: x+y, x÷y, x[^]y, ...

Ternary: x?y:z (Elvis), x BETWEEN y AND z (SQL)



George Boole (/bu:l/)
Mathematician
Philosopher
Logician

The Laws of Thought (1854)

Boolean Algebra!



Edward Vermilye Huntington
1874 – 1952

In 1904, he put Boolean algebra
on a sound axiomatic foundation

POSTULATE

aka. Axiom, Assumption

<https://en.wikipedia.org/wiki/Axiom>

A statement that is taken to be TRUE

Serve as a premise or starting point for further reasoning

I. CLOSURE

A set is closed with respect to an operator \S if the result of $\S \in S$:

Unary: $x \in S: \S x \in S$

Binary: $x, y \in S: x \S y \in S$

I. CLOSURE

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

\S = + (addition), - (subtraction), \times (multiplication), \neg (negation), ! (fact)

S is closed with respect to +, -, \times , \neg , !

I. CLOSURE

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

$\S = ^\wedge$ (power)

S is NOT closed with respect to \wedge for $2^\wedge(-1) \notin S$

I. CLOSURE

$$S = \{0,1\}$$

$\S = +$ (OR), \times (AND), $'$ (NOT)

S is closed with respect to $+, \times, '$

I. CLOSURE

$S = \{0,1\}$
 $\S = -$ (negation)

S is NOT closed with respect to $-$ for $(-1) \notin S$

II. COMMUTATIVE

A **binary** operator \S on a set S is commutative iff for **all** $x,y \in S$:

$$x \S y = y \S x$$

($x \S y$ may or may not be in S)

II. COMMUTATIVE

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

$\S = +$ (addition), \times (multiplication)

+ and \times are commutative on S for $x+y=y+x$ and $x\times y=y\times x$

II. COMMUTATIVE

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

$\S = -$ (subtraction)

- is NOT commutative on S for $x-y \neq y-x$

II. COMMUTATIVE

$$S = \{0,1\}$$

$\S = +$ (OR), \times (AND), \uparrow (NAND), \downarrow (NOR), \oplus (XOR), \odot (XNOR)

All are commutative on S for $x \in S$, $y \in S$

III. ASSOCIATIVE

A **binary** operator \S on a set S is associative iff for **all** $x,y,z \in S$:

$$x \S (y \S z) = (x \S y) \S z = x \S y \S z$$

III. ASSOCIATIVE

$$S = \{..., -2, -1, 0, 1, 2, ...\}$$

$\S = +$ (addition), \times (multiplication), $-$ (subtraction)
 $+, -, \times$ are associative on S for

$$x \pm (y \pm z) = (x \pm y) \pm z = x \pm y \pm z$$

$$x \times (y \times z) = (x \times y) \times z = x \times y \times z$$

III. ASSOCIATIVE

$S = \{..., -2, -1, 0, 1, 2, ...\}$

$\S = ^\wedge$ (power)

\wedge is NOT associative on S for $2^\wedge(1^\wedge 3) \neq (2^\wedge 1)^\wedge 3$

III. ASSOCIATIVE

$$S = \{0,1\}$$

$\S = +$ (OR), \times (AND)

$+, \times$ are associative on S for

$$x + (y + z) = (x + y) + z = x + y + z$$

$$x \times (y \times z) = (x \times y) \times z = x \times y \times z$$

IV. IDENTITY

$e \in S$ is an identity element w.r.t binary operator \S iff for all $x \in S$:

$$x \S e = x = e \S x$$

IV. IDENTITY

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

$\S = +$ (addition), \times (multiplication)

$$e_+ = 0 : x + 0 = 0 + x = x$$

$$e_\times = 1 : x \times 1 = 1 \times x = x$$

IV. IDENTITY

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

$\S = -$ (subtraction)

$$e = 0$$

$$x - 0 \neq 0 - x \neq x$$

NO identity element for $-$ (subtraction) in S

IV. IDENTITY

$$S = \{0,1\}$$

$\S = +$ (OR), \times (AND)

$e_+ = 0 : x+0=0+x=x$

$e_\times = 1 : x\times 1=1\times x=x$

V. INVERSE

For all $x \in S$, there should be $y \in S$ w.r.t binary operator \S iff:

$$x \S y = e_{\S} = y \S x$$

We denote $y = x^{-1}$ and $x = y^{-1}$

V. INVERSE

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

\S = + (addition)

$$\begin{aligned} x + (-x) &= (-x) + x = e_+ = 0 \\ x^{-1} &= -x \end{aligned}$$

V. INVERSE

$$S = \{\dots, -2, -1, 0, 1, 2, \dots\}$$

$\S = \times$ (multiplication)

S does not have the inverse property for \times since

$$2 \times \frac{1}{2} = \frac{1}{2} \times 2 = e_x = 1 \text{ but } \frac{1}{2} \notin S$$

V. INVERSE

$$S = \{0,1\}$$

$\S = +$ (OR), \times (AND)

$$1+?= ?+1 \neq e_+ = 0$$

$$0\times?= ?\times0 \neq e_x = 1$$

VI. DISTRIBUTIVE

If \S and $+$ are two binary operators on a set S , \S is distributive over $+$ iff:

$$x \S (y + z) = (x \S y) + (x \S z) = (y + z) \S x$$

BOOLEAN ALGEBRA

- A set S with at least two elements x, y and $x \neq y$.
- Two binary operators $\&$ and \oplus
- S is closed, commutative, and distributive w.r.t $\&$, \oplus
- $e_{\&}$ and e_{\oplus} exist
- Complement: for any $x \in S$, there is $y \in S$ such that
 - $x \& y = e_{\oplus}$
 - $x \oplus y = e_{\&}$we denote $y = x'$