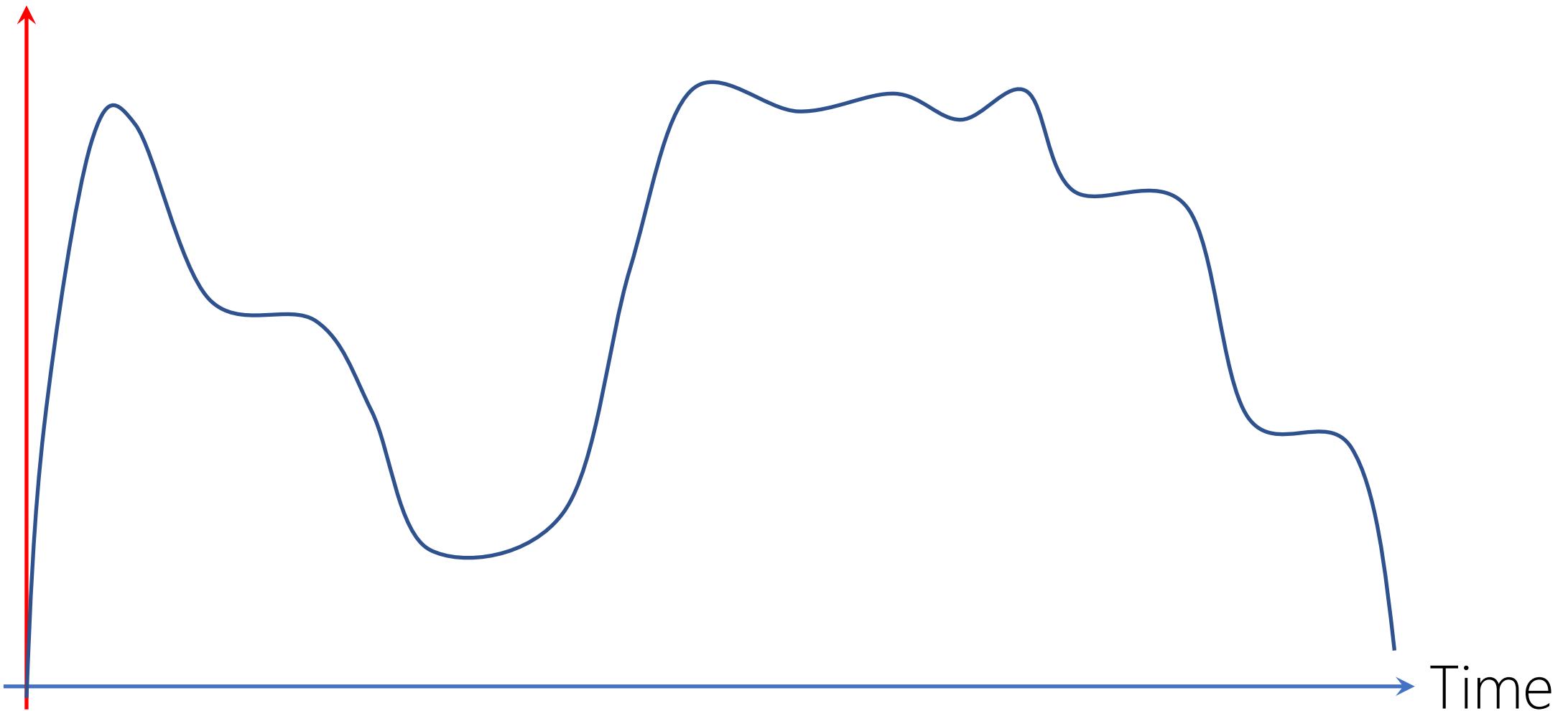

ANALOG SYSTEMS

Continuous

Voltage



DIGITAL SYSTEMS


Discrete

ELECTRICITY NUMBER SYSTEM


BASE-?

BASE-10


Voltage

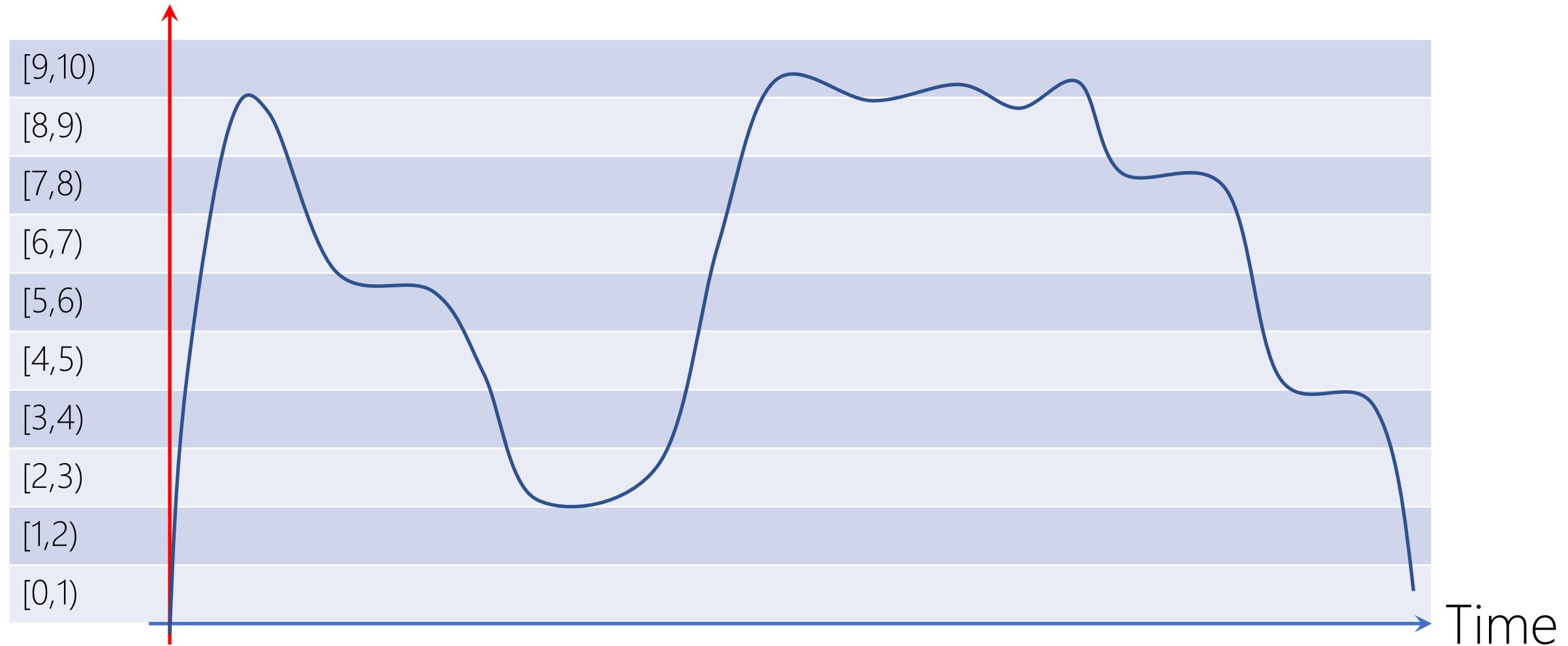


Voltage

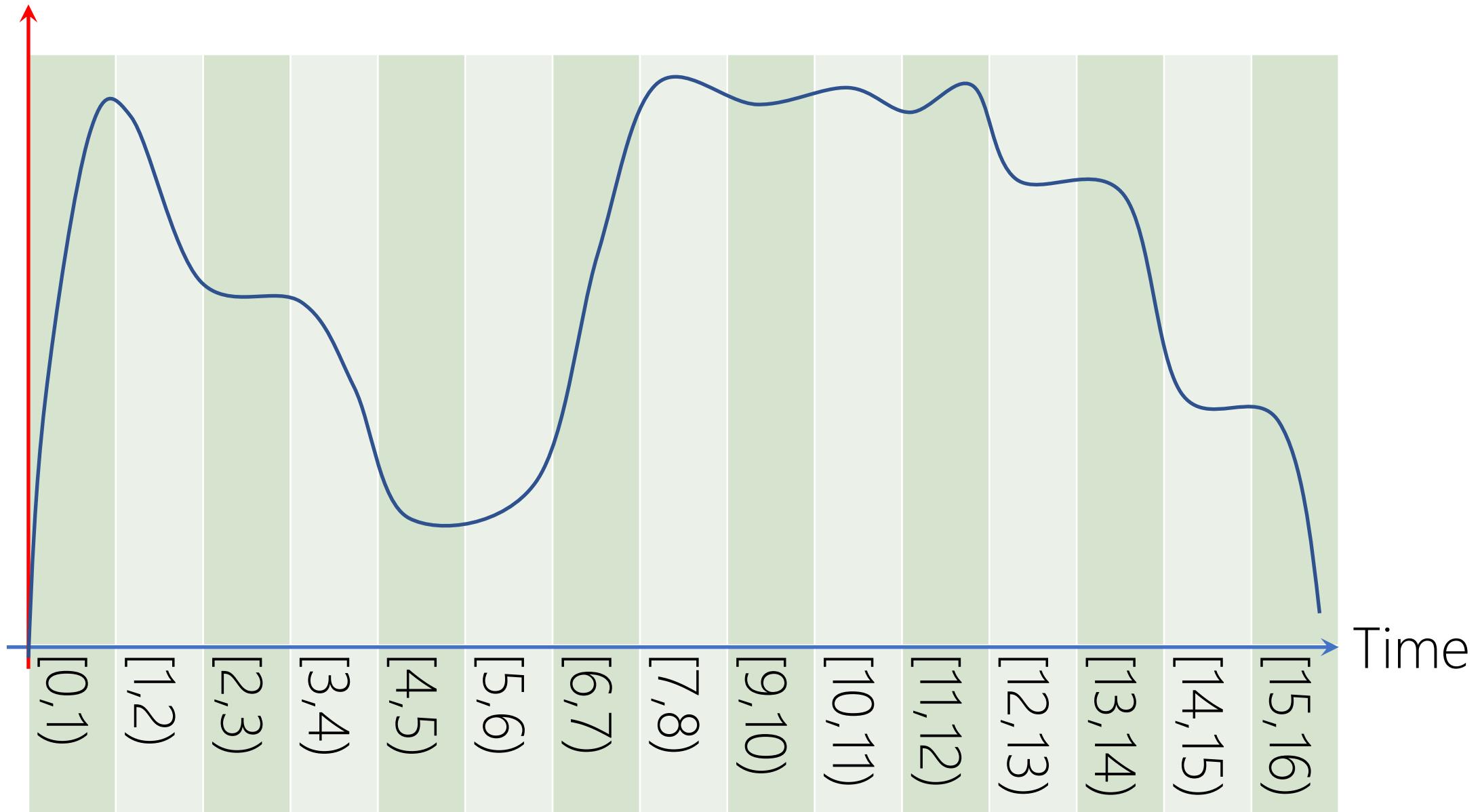

Voltage

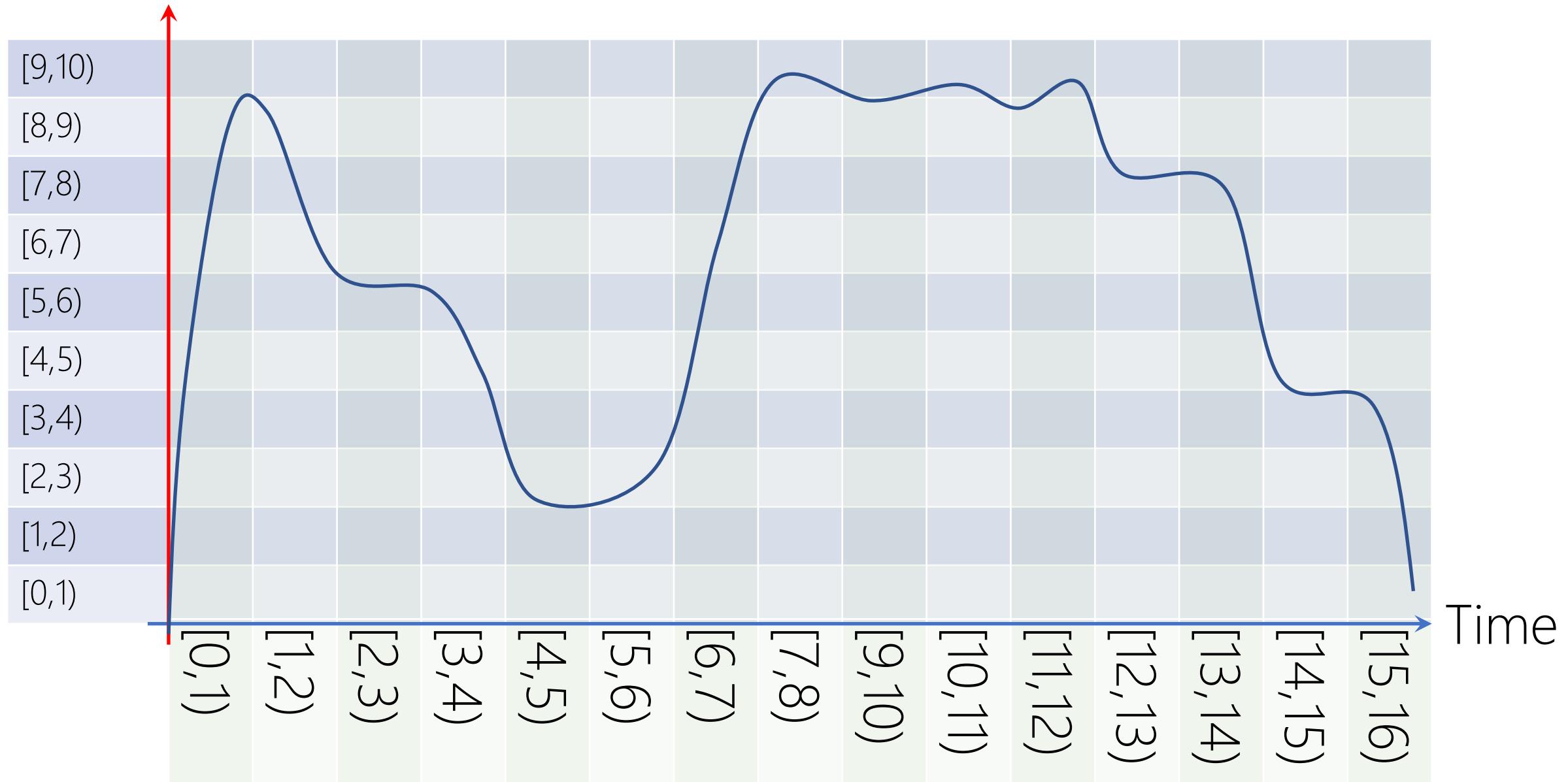


Voltage

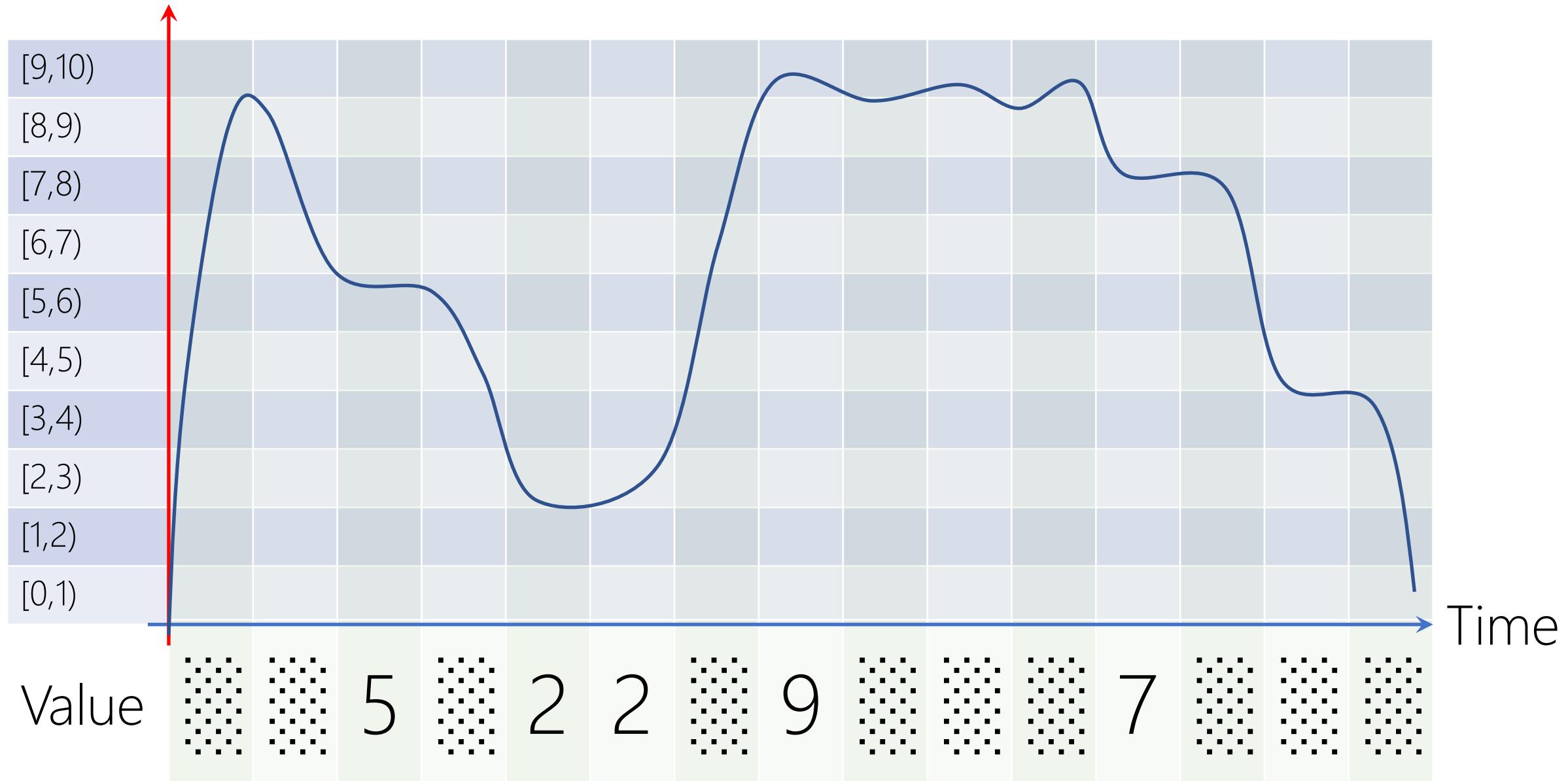


GRANULARITY


Voltage

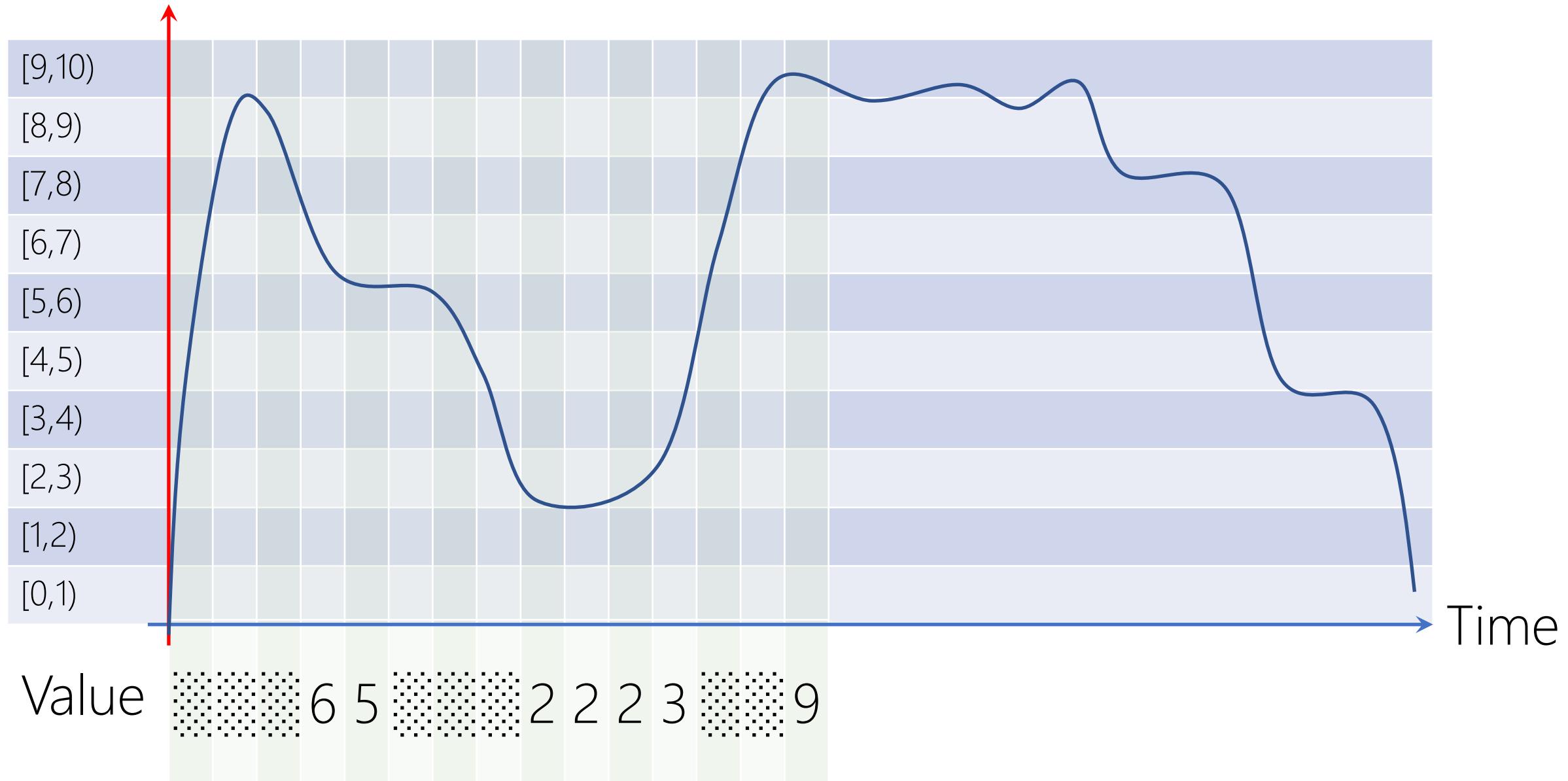

Voltage

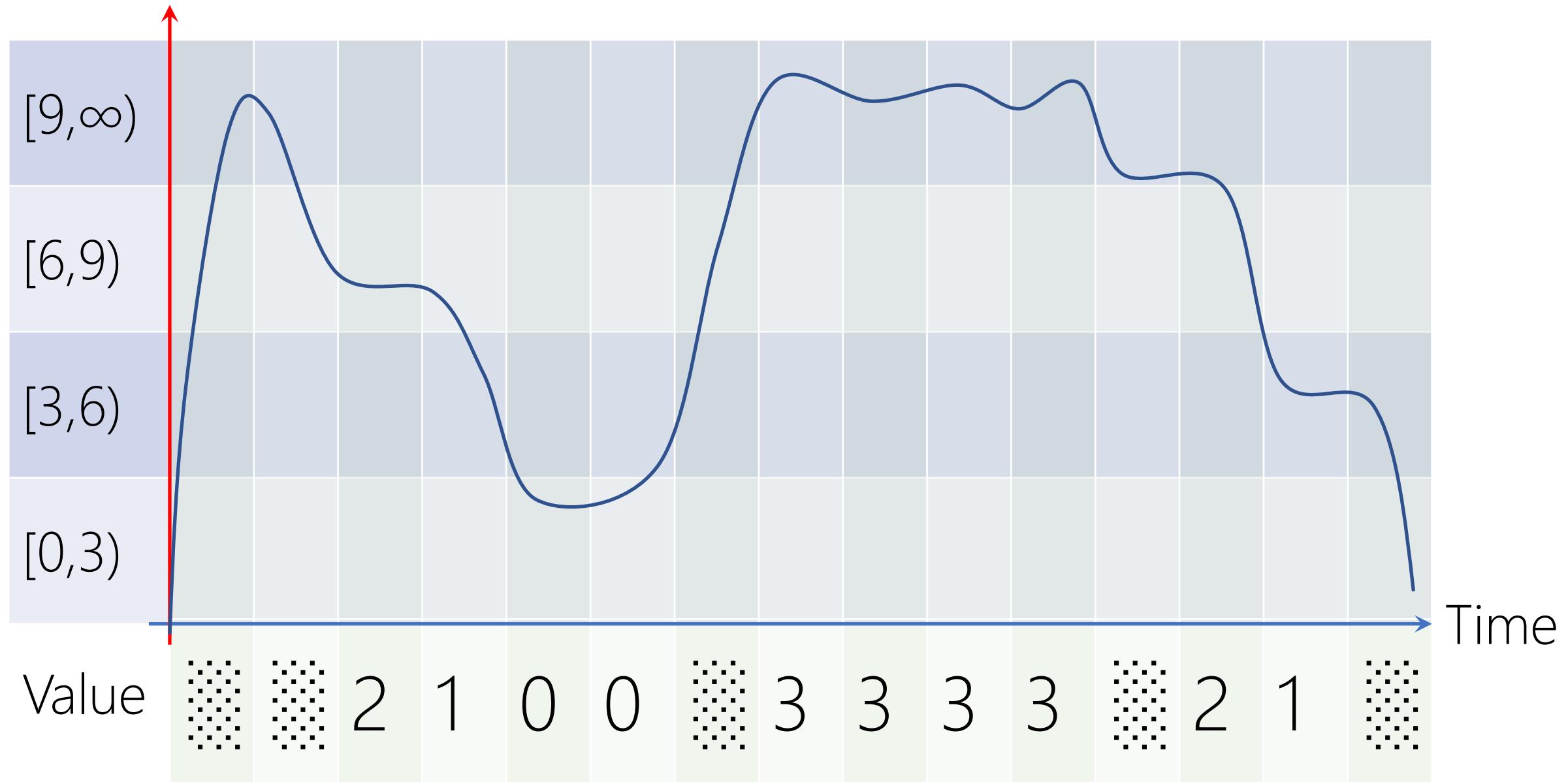

Voltage

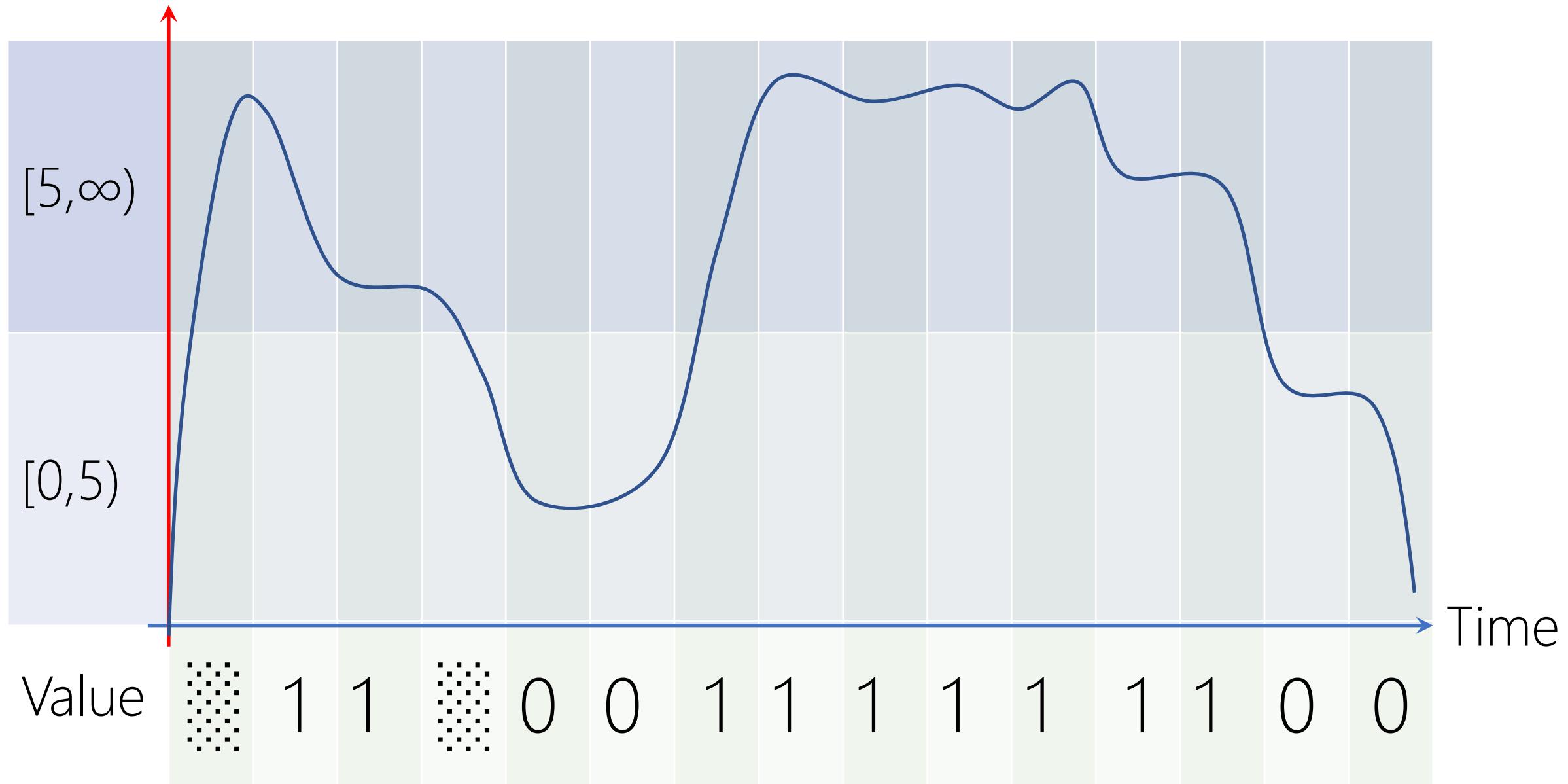

RELIABILITY

Robust to Noise

Fundamentally Hardware/Engineering Problem

TERNARY COMPUTER

https://en.wikipedia.org/wiki/Ternary_computer

Balanced Trinary $\{-1,0,1\}$

Entirely from *Wood!*

Thomas Fowler 1840

More History and Etymology → <https://en.wikipedia.org/wiki/Computer>

DECIMAL COMPUTER

https://en.wikipedia.org/wiki/Decimal_computer

They are not actually base-10! We'll cover them later.

TRUE VS. FALSE



George Boole (/bu:l/)
Mathematician
Philosopher
Logician

The Laws of Thought (1854)

Boolean Algebra!

Claude Elwood Shannon

Mathematician
Electrical Engineer
Cryptographer


M.Sc. Thesis (1937)

A Symbolic Analysis of Relay and Switching Circuits
21 years old!

Switching Algebra!






BINARY COMPUTER

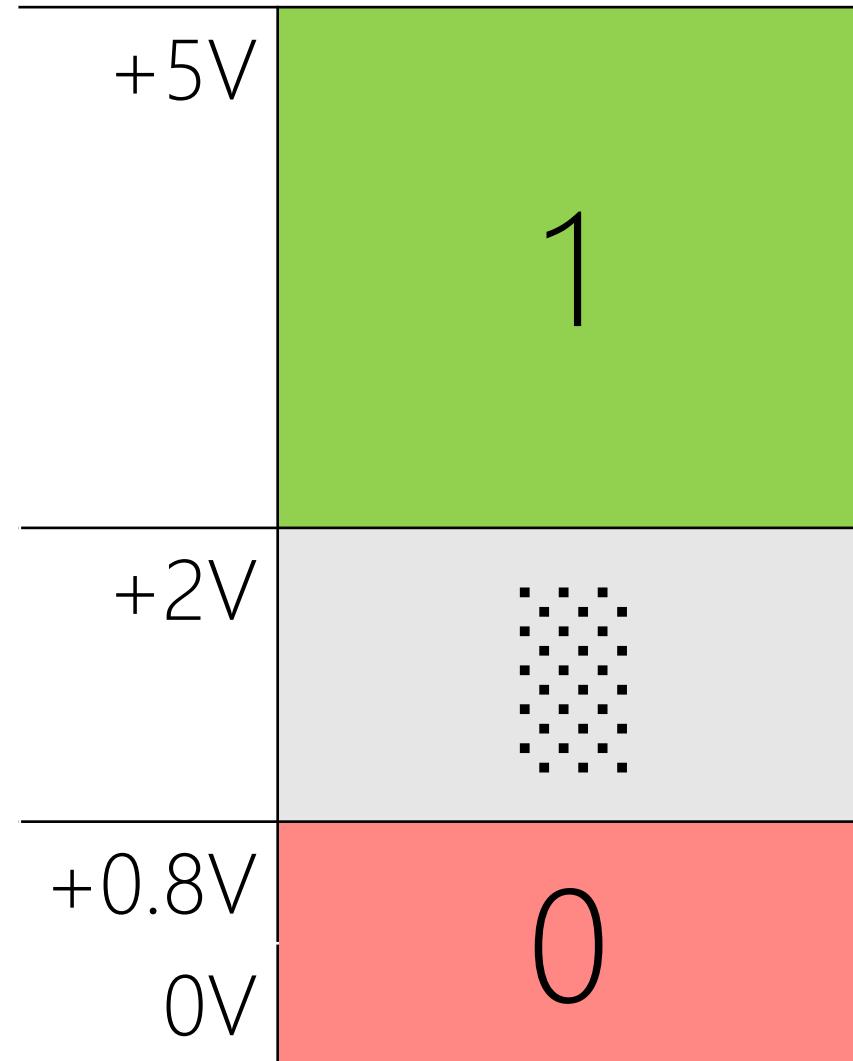


POSITIVE
LOGIC

Voltage

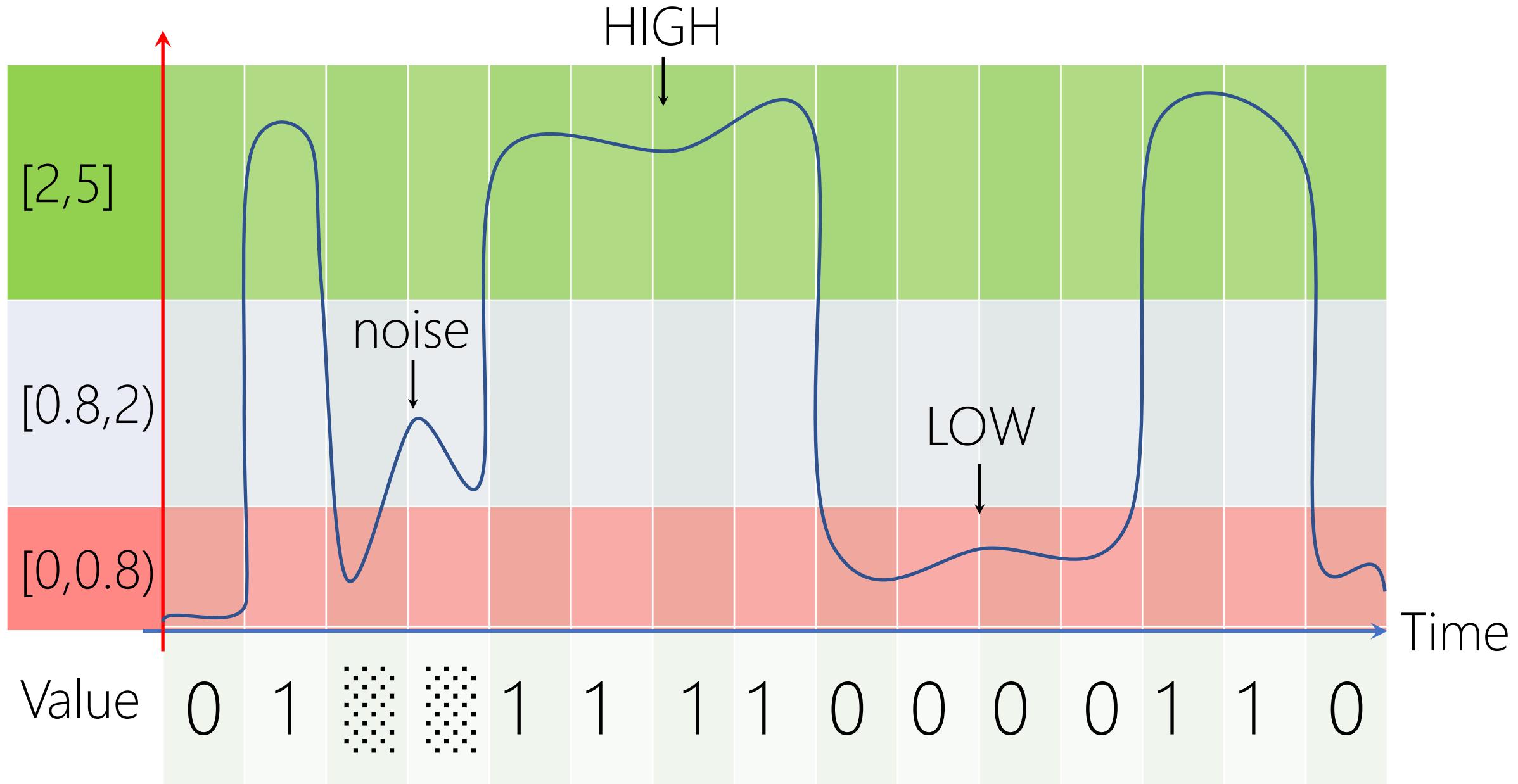



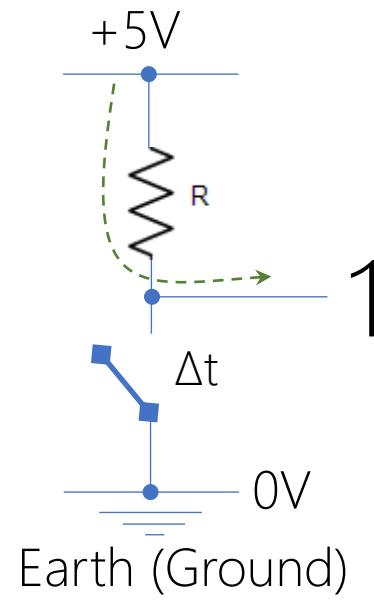
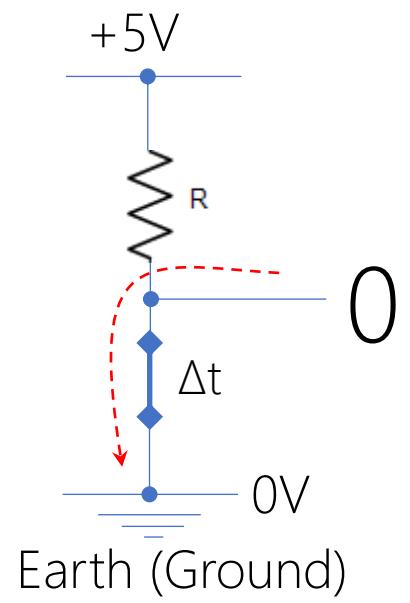


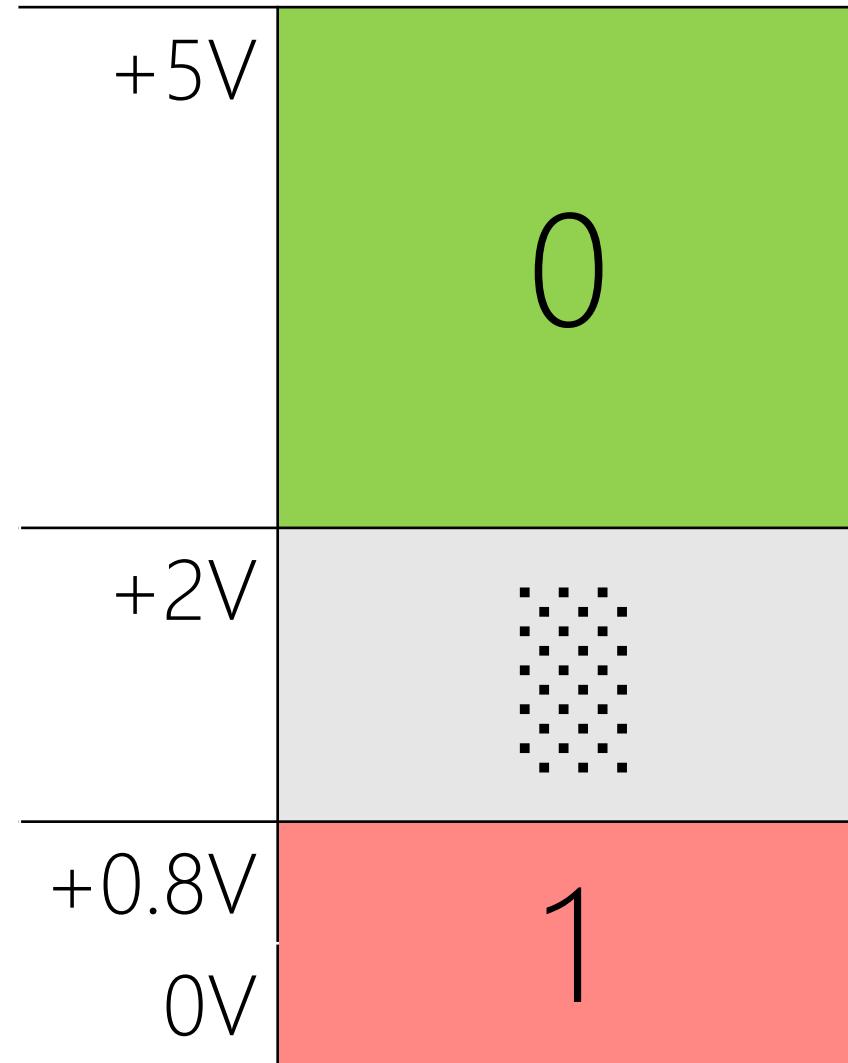

NEGATIVE
LOGIC

Voltage

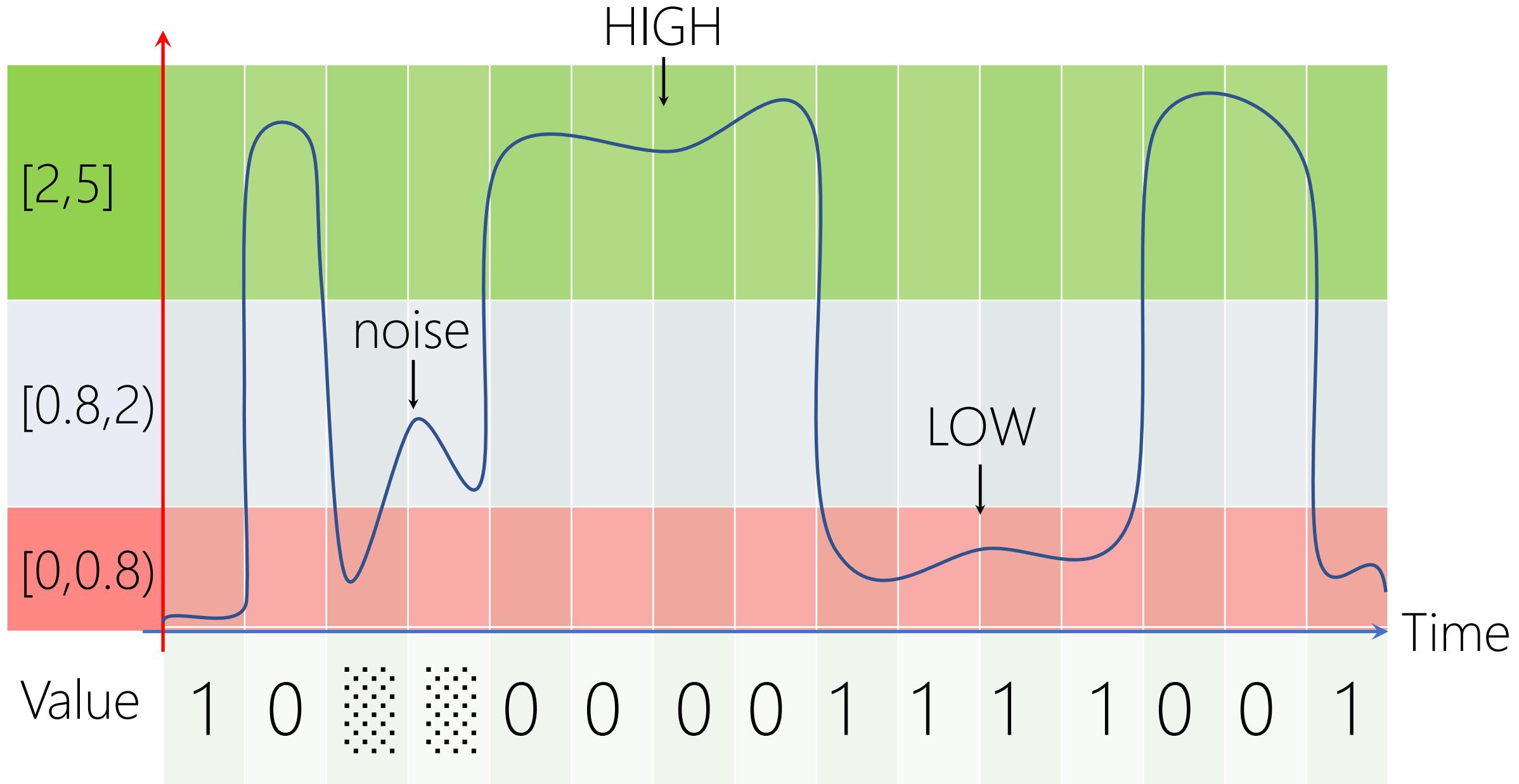

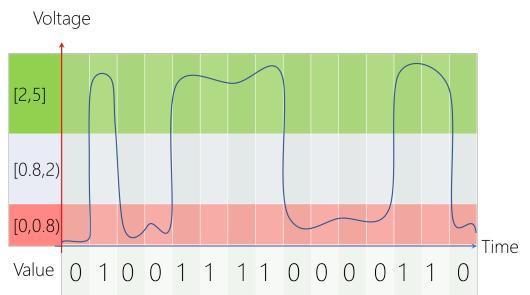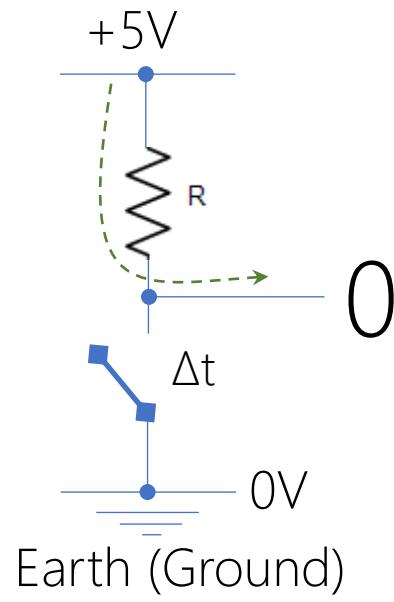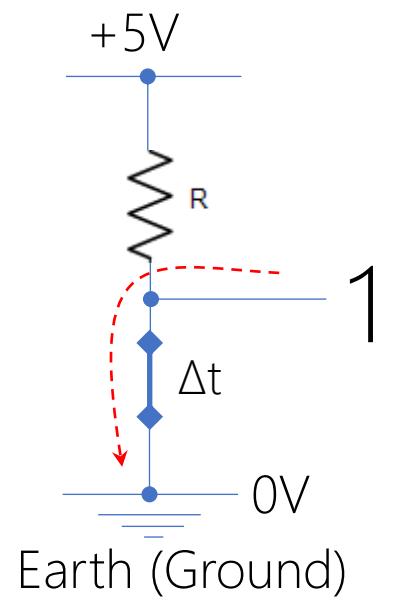

DESIGN COMPUTER

Positive Logic
Button-Up Approach

DESIGN COMPUTER

Positive Logic
Button-Up Approach


Finding simpler, but equivalent, computers reduces the overall cost!
Rely primarily on mathematical methods in Boolean algebra!


BUILD COMPUTER

Electrical and Computer Engineering

LOGIC GATES

BOOLEAN GATES

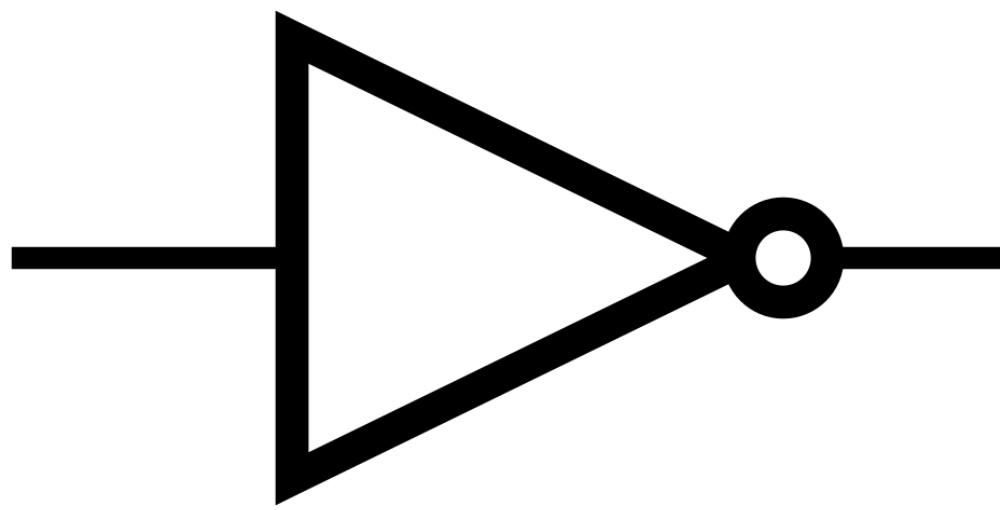

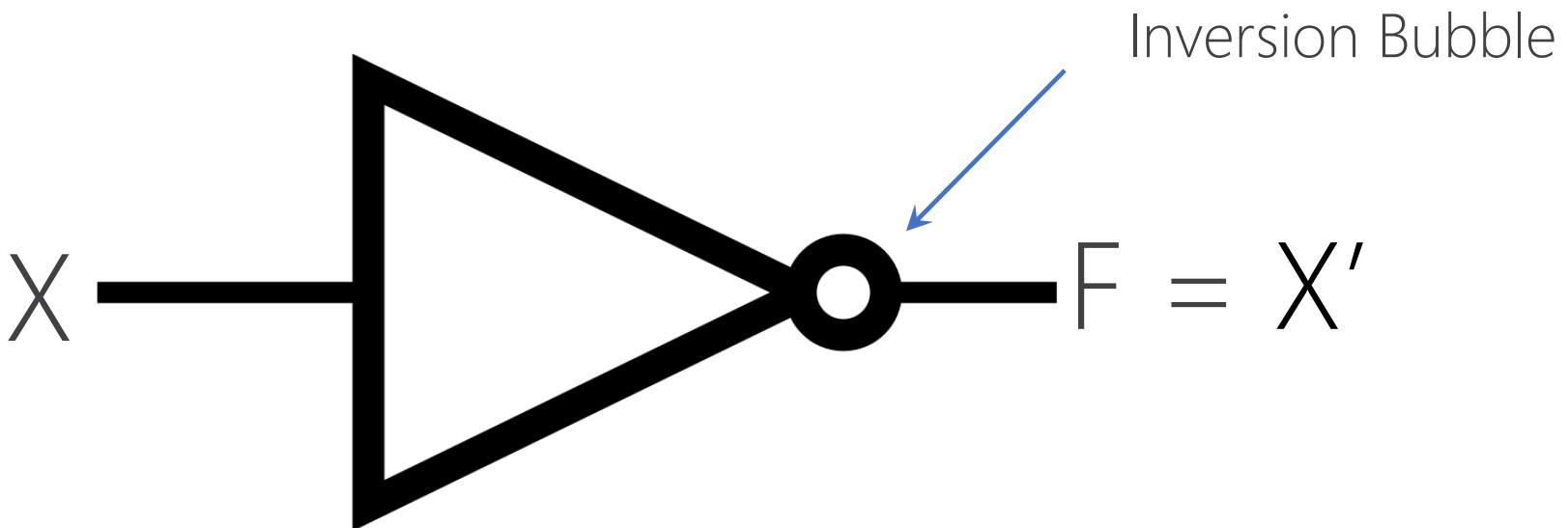

X	NOT X	Invertor X	X'	\bar{X}
0			1	
1			0	


Boolean Expression/Function: $F = X'$
 > inverse of X gives F <

W

Z

Y

X

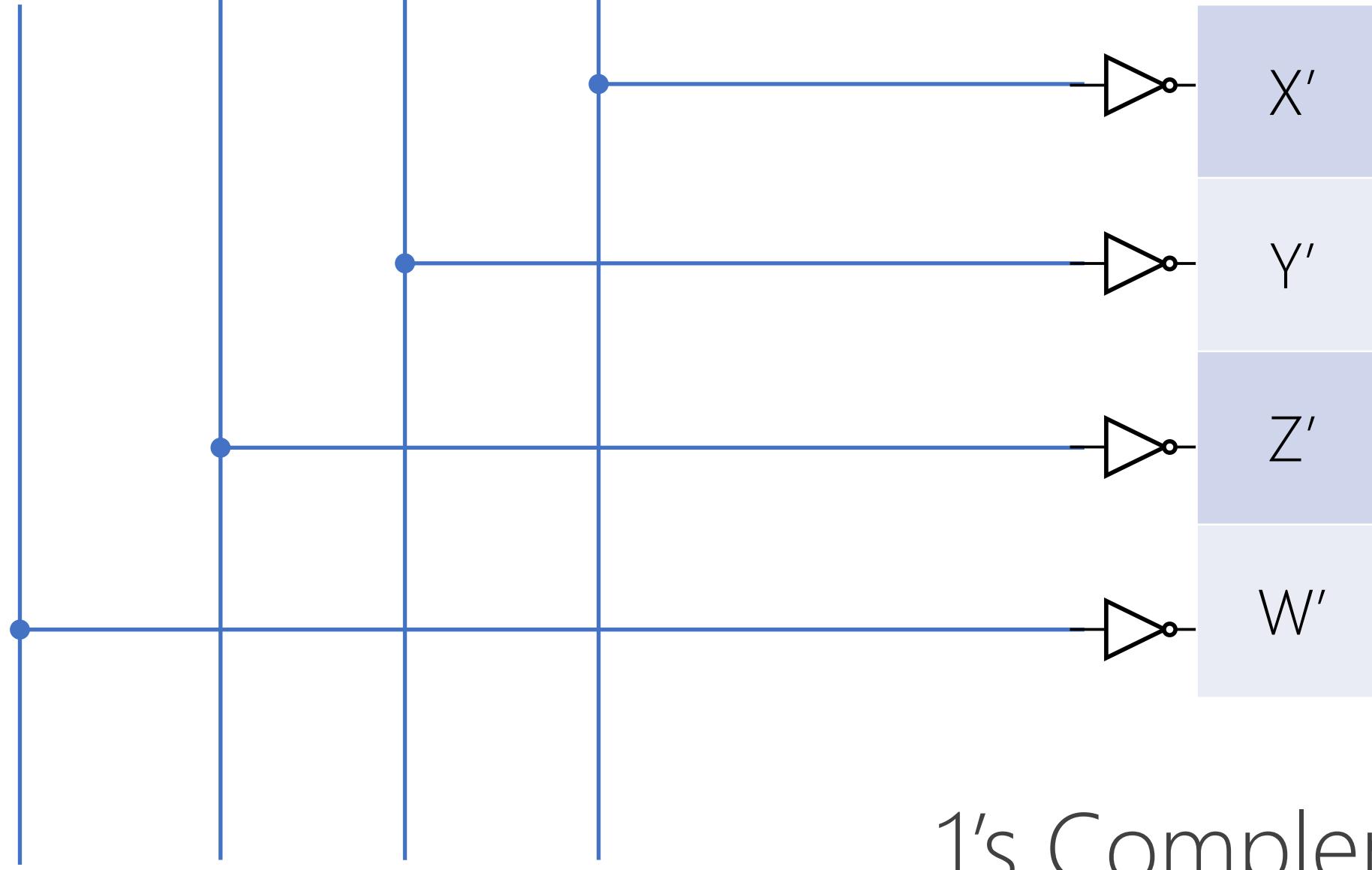

X'

$$F_1 = X'$$

Y'

$$F_2 = Y'$$

Z'

$$F_3 = Z'$$

W'

$$F_4 = W'$$

1's Complement

BINARY VARIABLE


aka. Boolean variable


A variable that can have a value in {0,1}
X, Y, Z, W, ...

BOOLEAN FUNCTION


aka. Boolean Expression

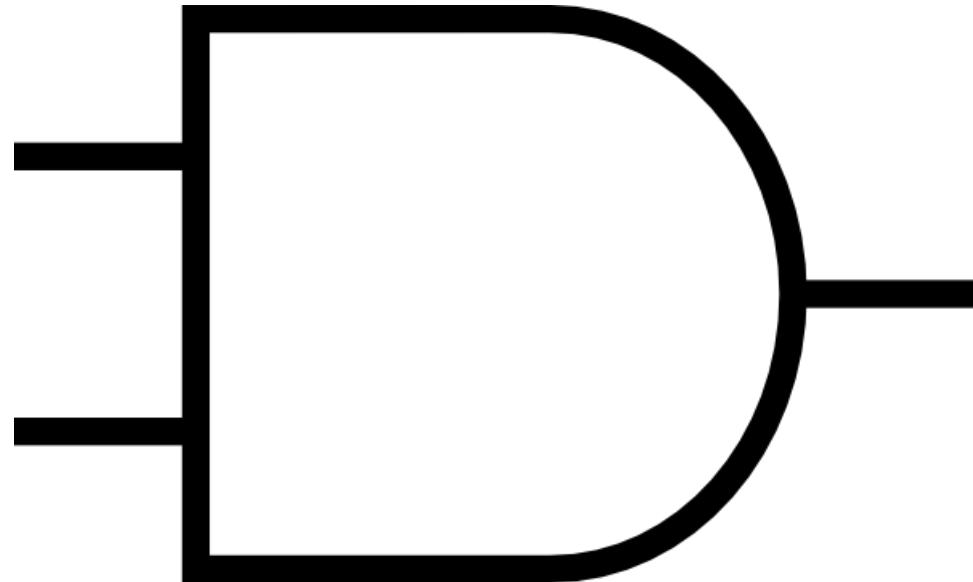A function that accept Boolean variable(s) and output a value in {0,1}, e.g., $F(X) = X'$




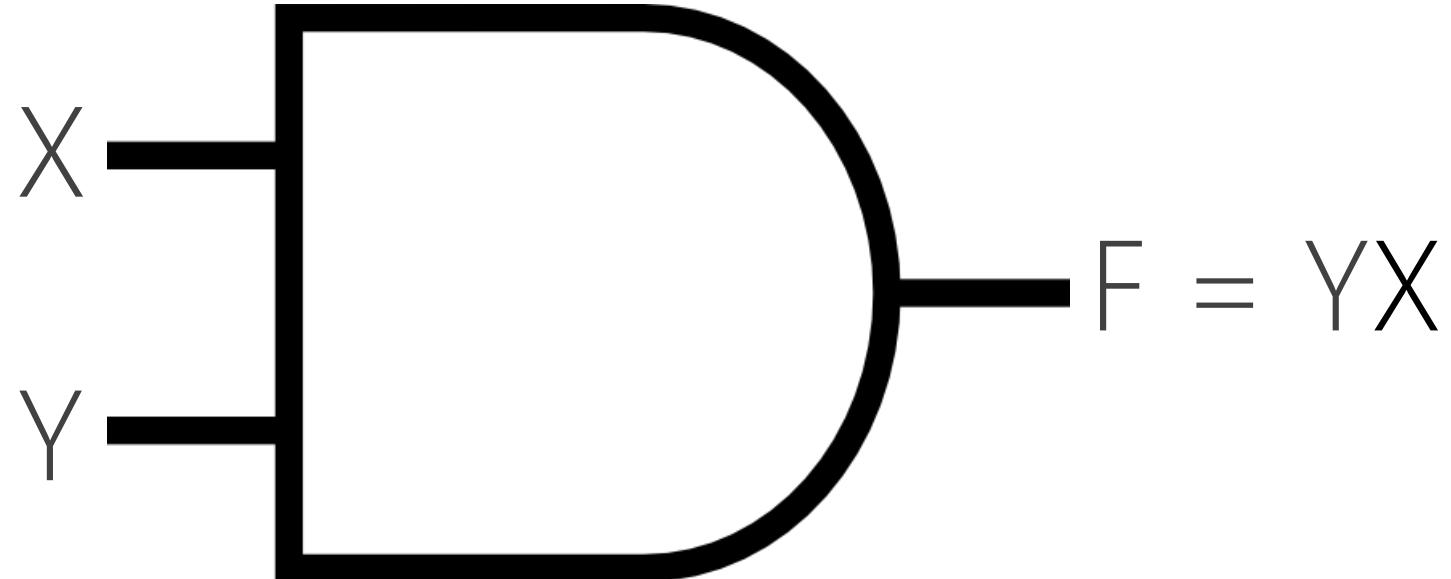

Y	X	X AND Y	$Y \cdot X$	$Y * X$
0	0		0	
0	1		0	
1	0		0	
1	1		1	

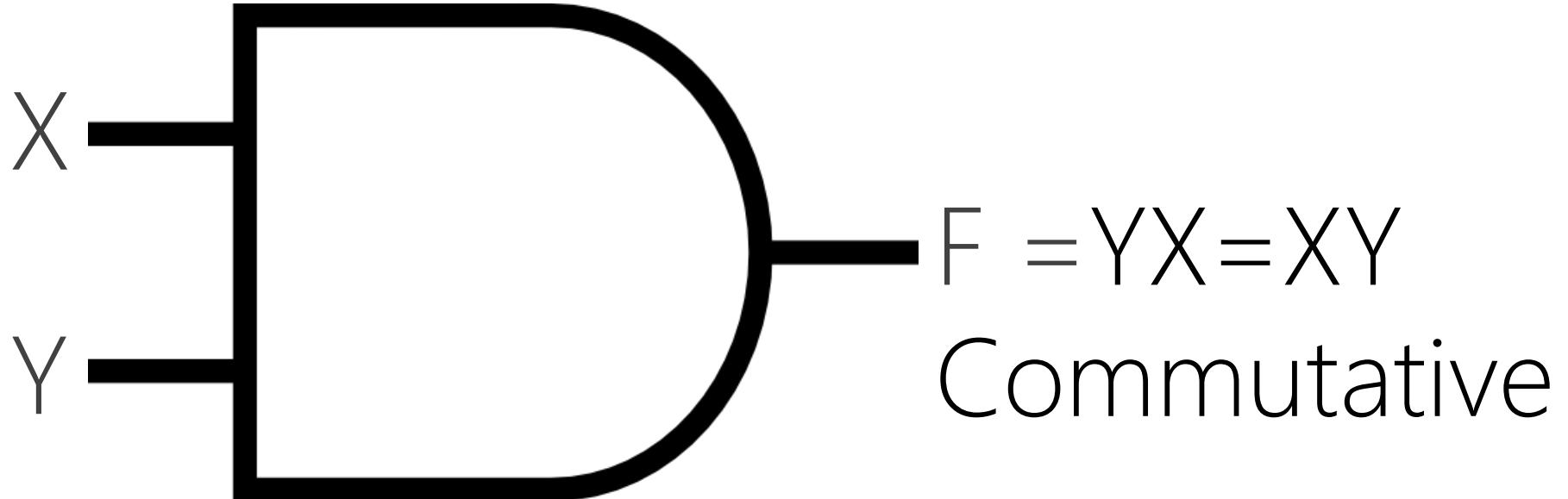


X	Y	$Y \text{ AND } X$	$X \cdot Y$	$X * Y$
0	0		0	
0	1		0	
1	0		0	
1	1		1	

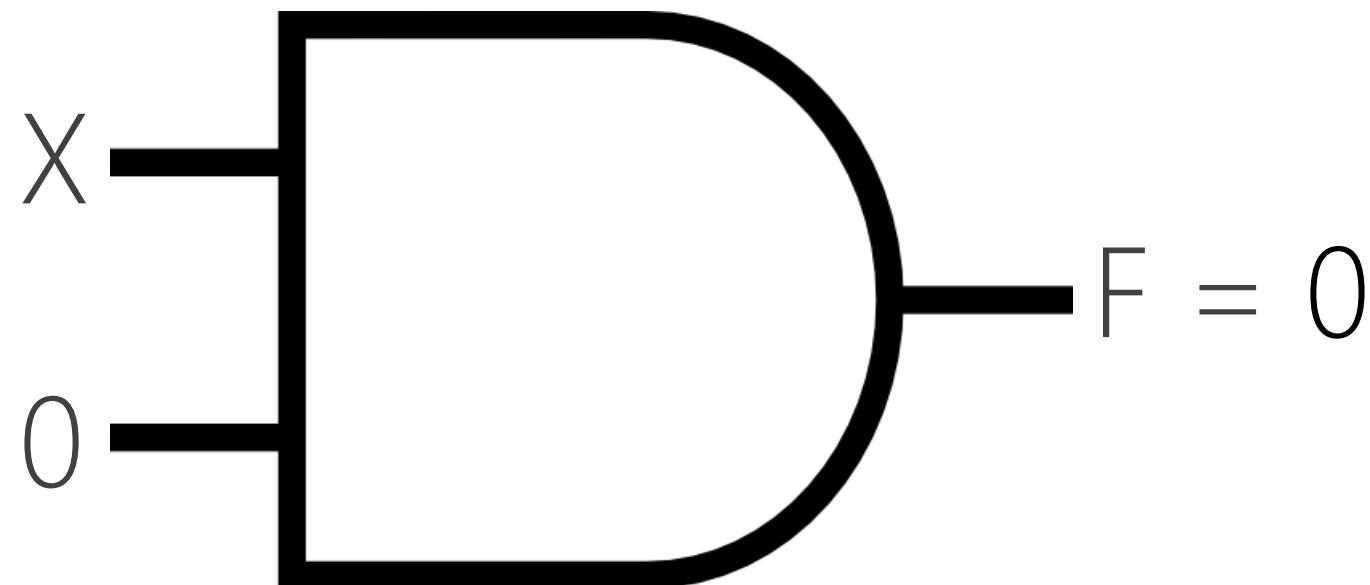


Y	X	YX
0	1	0
0	0	0

$$F = X0 = 0$$

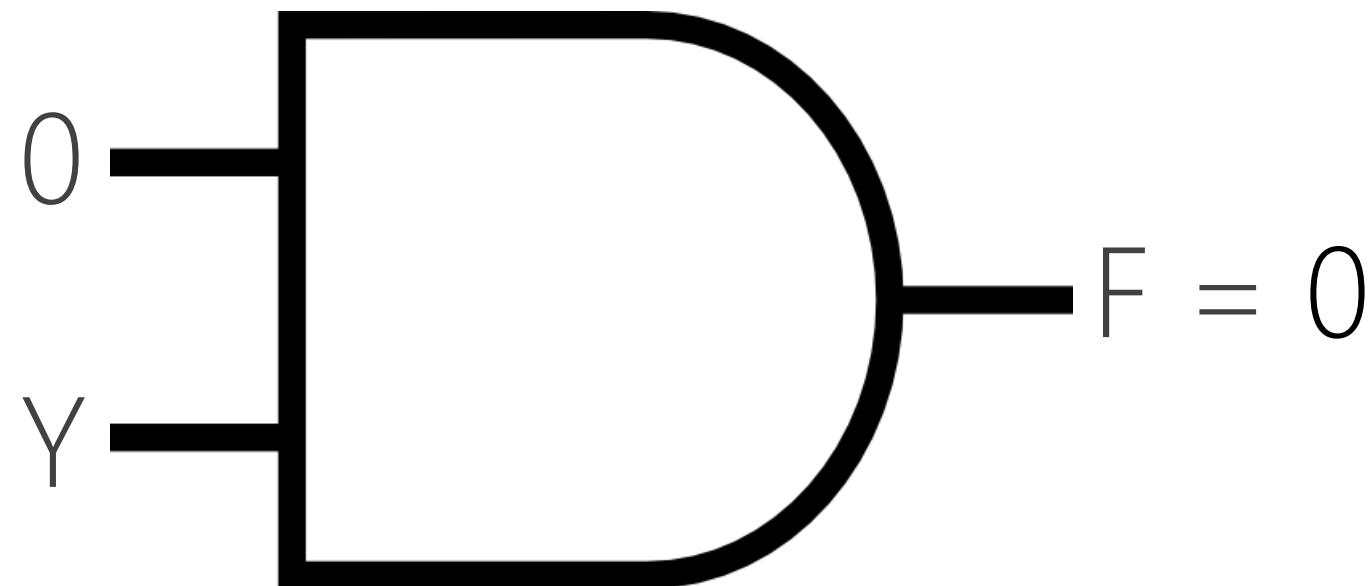


Y	X	YX
0	0	0
1	0	0

$$F = 0 \cdot Y = 0$$

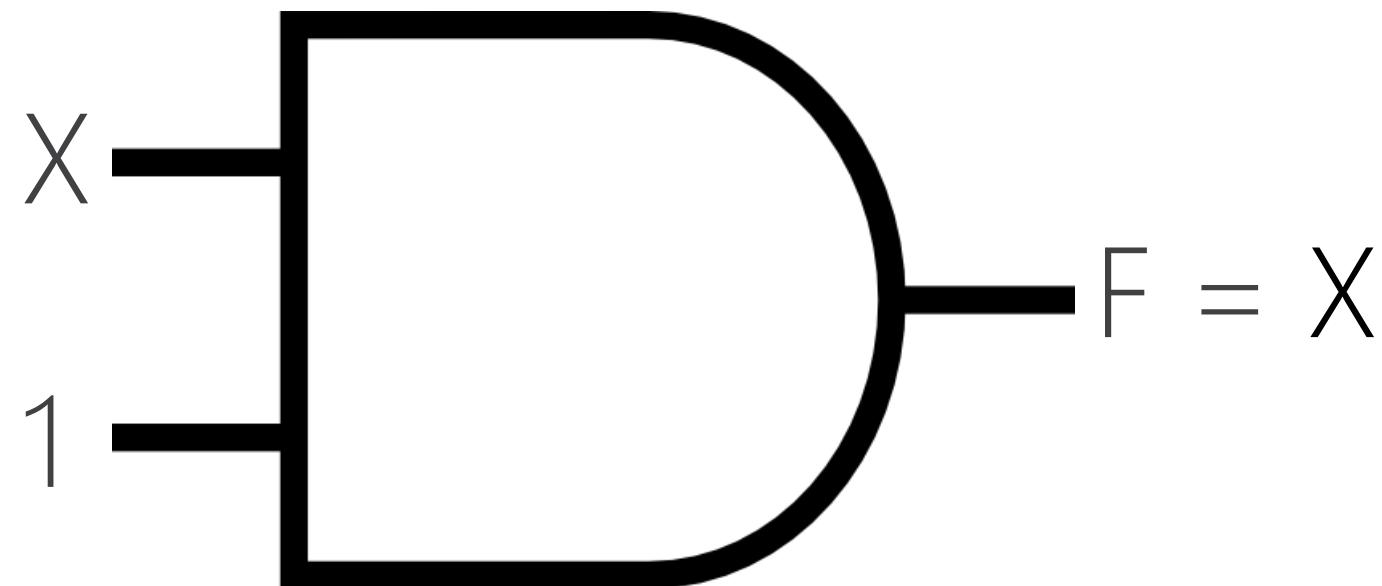

Y	X	YX
1	0	0
1	1	1


$$F = X1 = 1111 \times 1111 = X$$

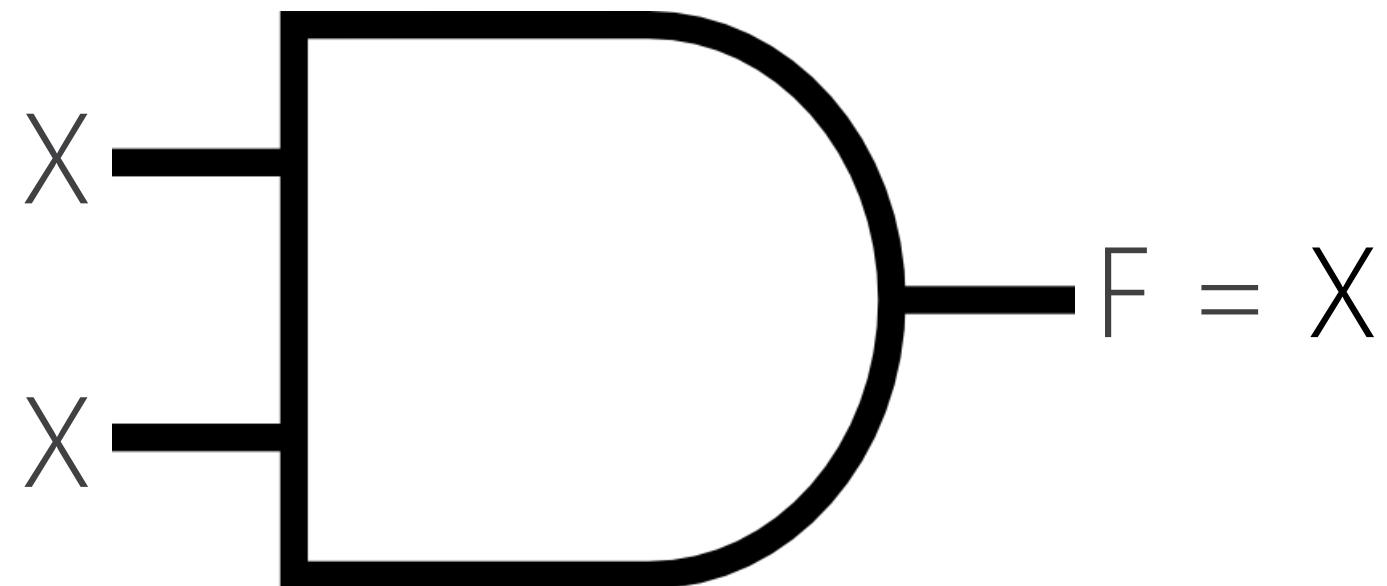

X	X	XX
0	0	0
1	1	1


$$F = XX = X$$

X

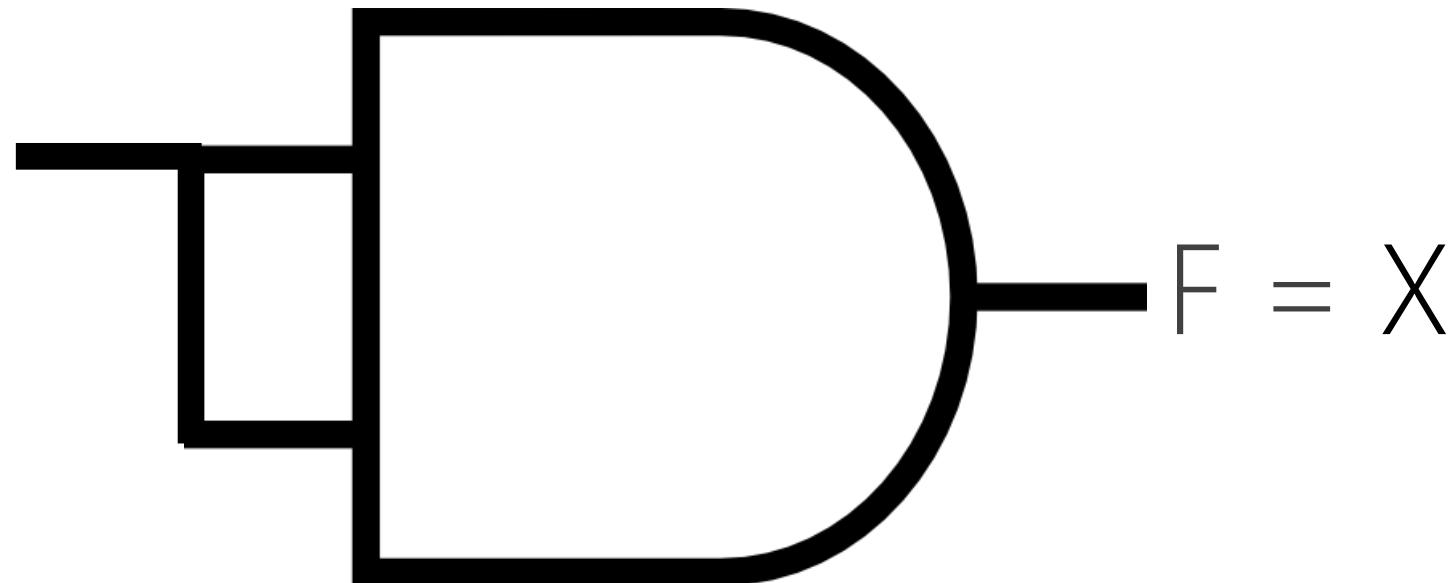


X	X	XX
0	0	0
1	1	1

$$F = XX = X$$

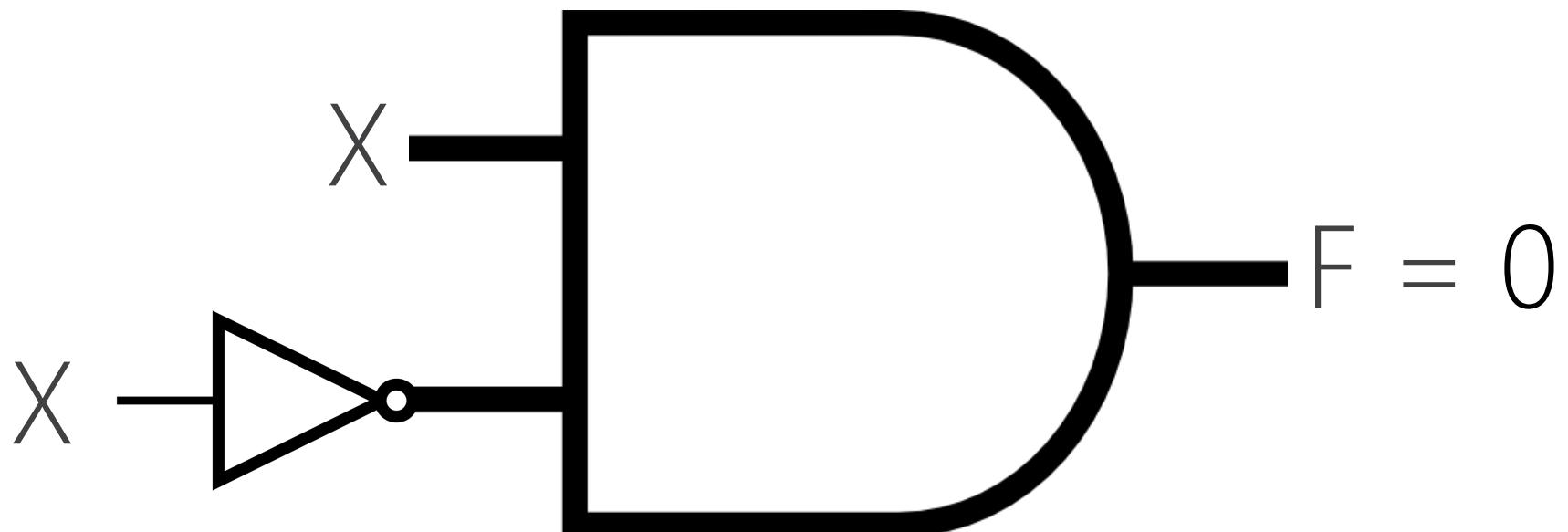


X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

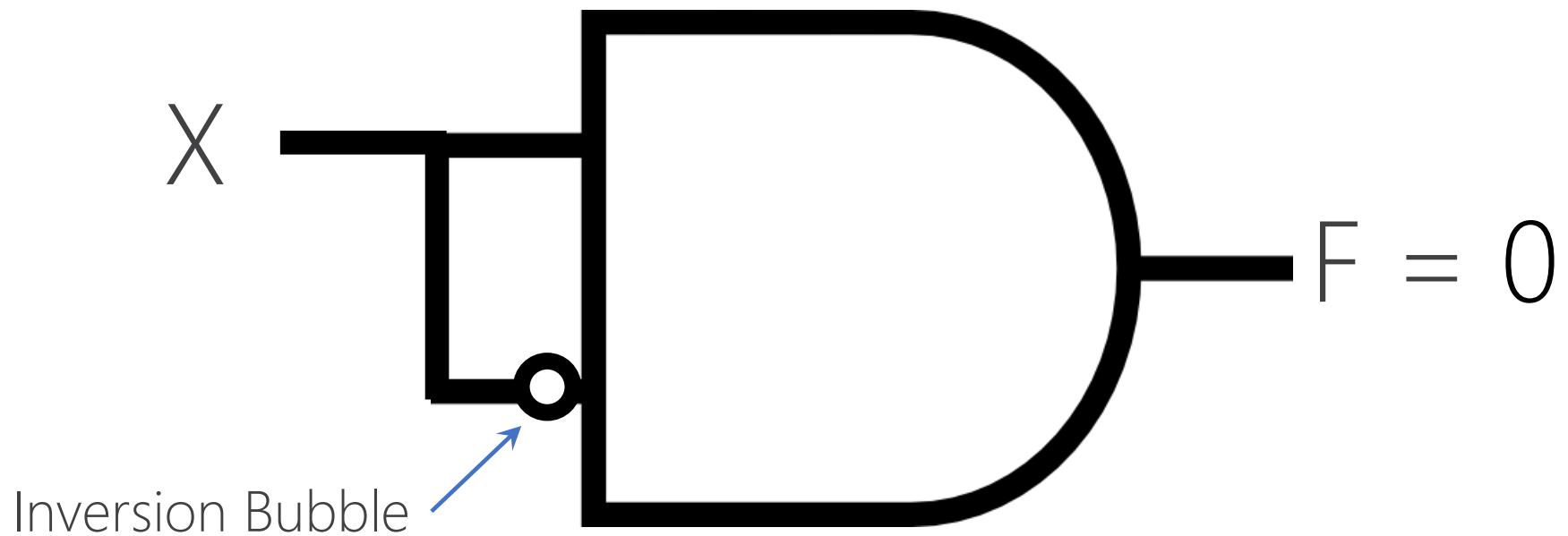

X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

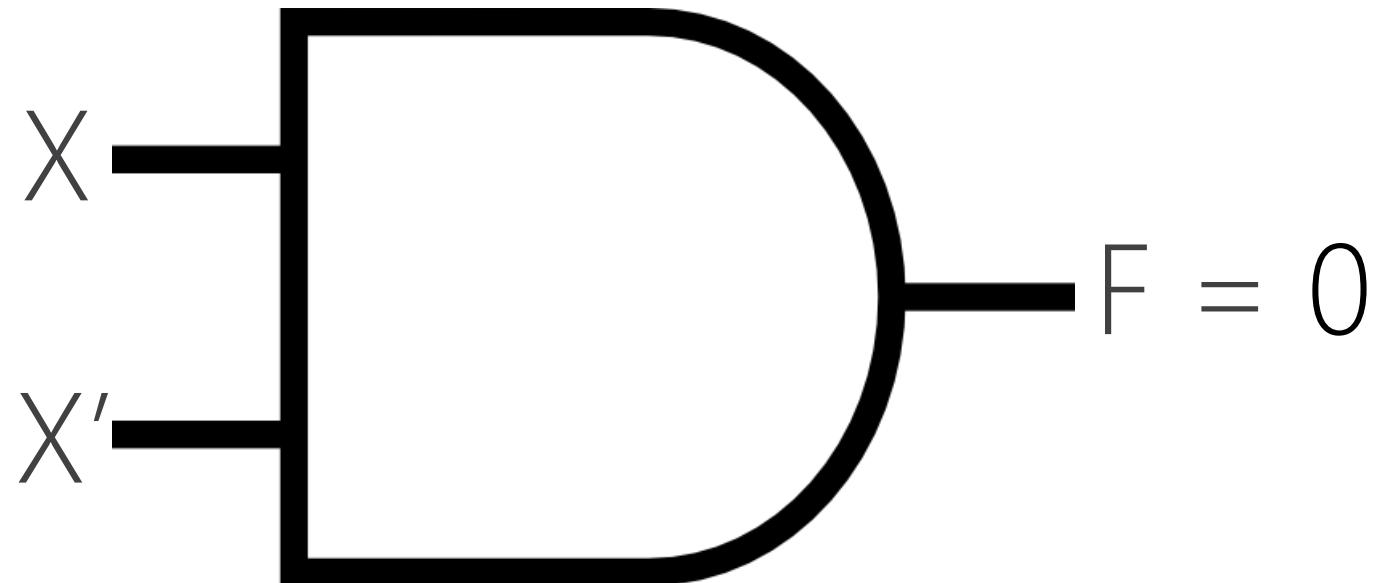


X'	X	$X'X$
1	0	0
0	1	0


$$F = XX' = 0$$

3-INPUT AND

Z	Y	X	ZYX
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

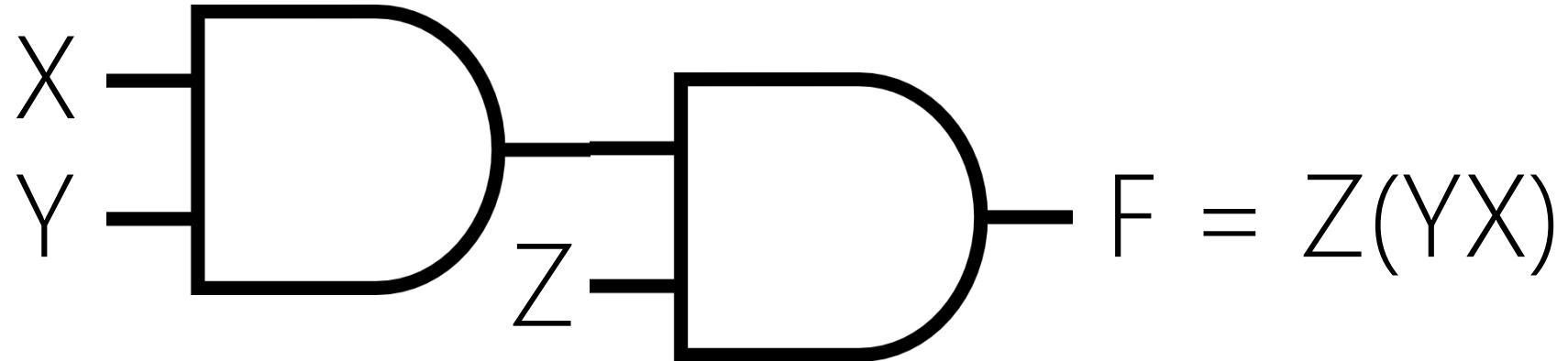


Z	Y	X	Z(YX)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

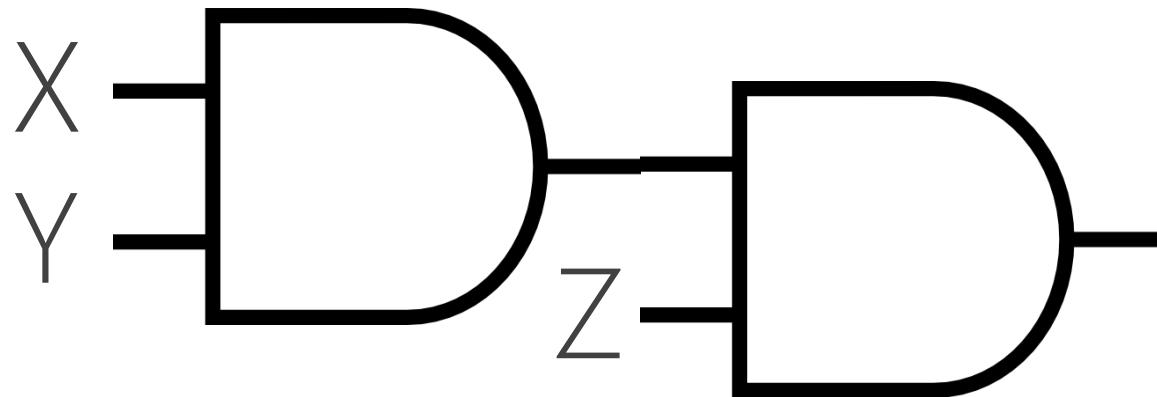



$$F = Z(YX) = Z(XY) = (ZX)Y = (XZ)Y = XZY$$



Associative

Z	Y	X	$Z(YX)$	$Z(XY)$	$(ZX)Y$	XZY
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	1	1	1	1


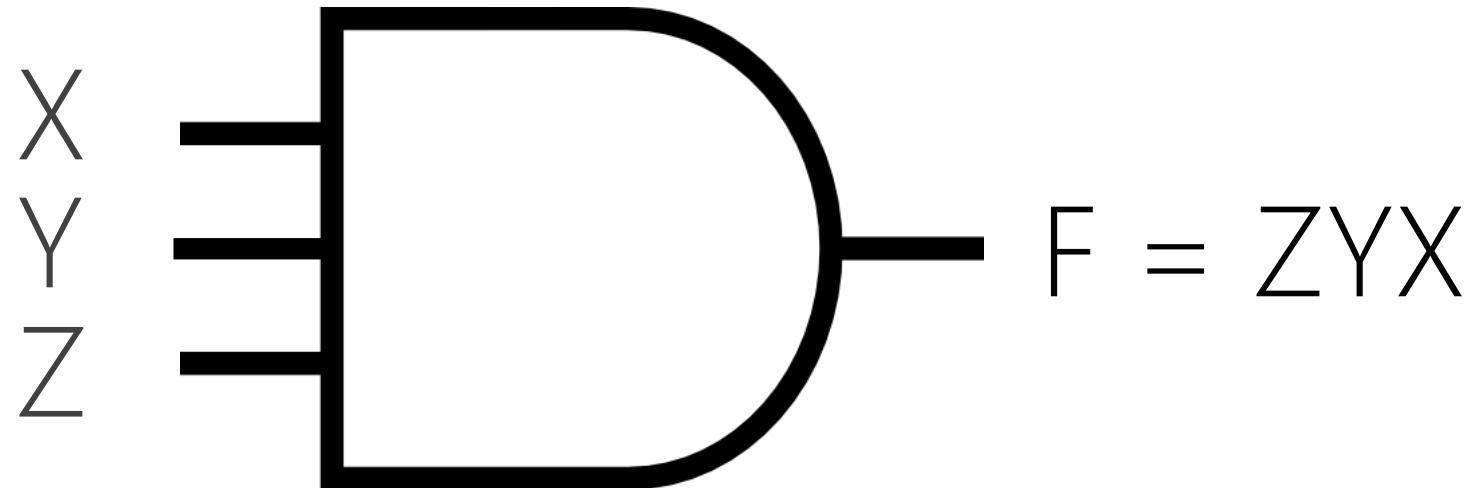



Z	Y	X	ZYX
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

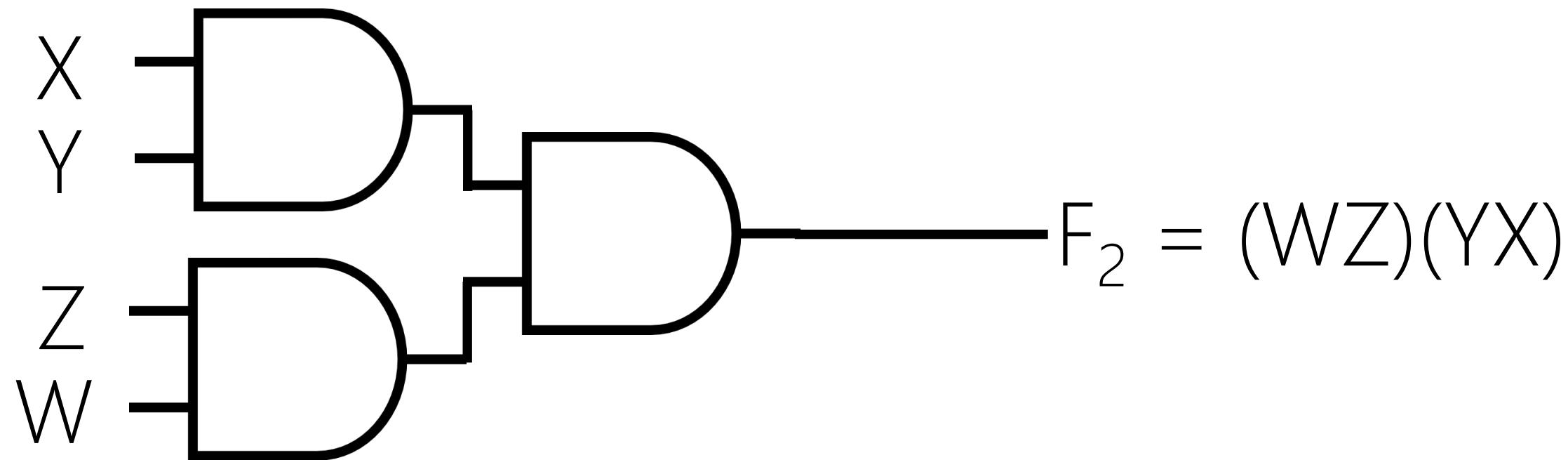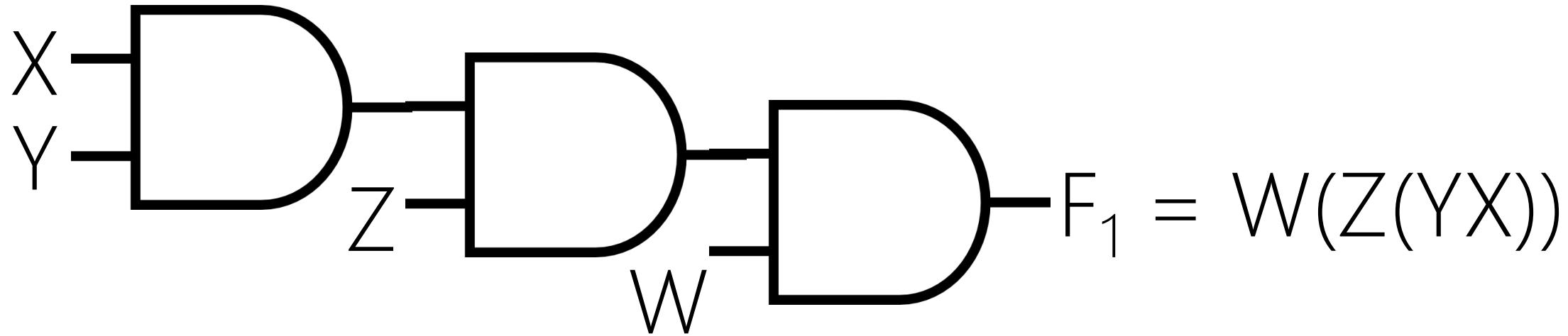

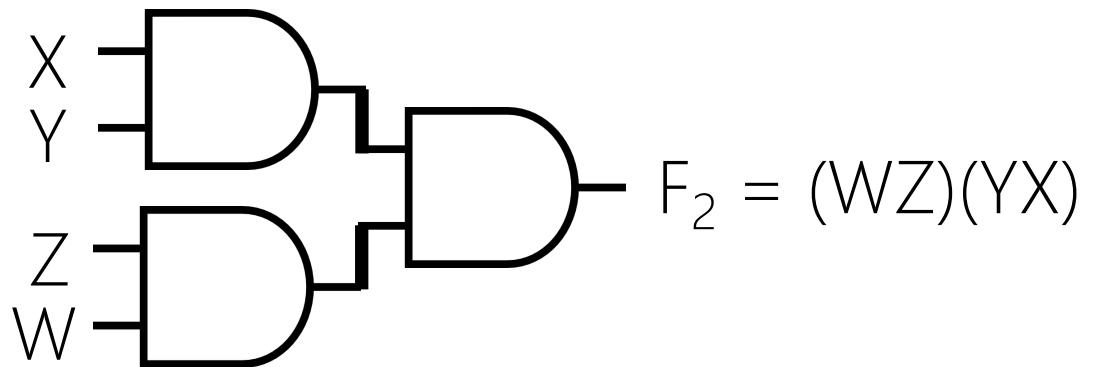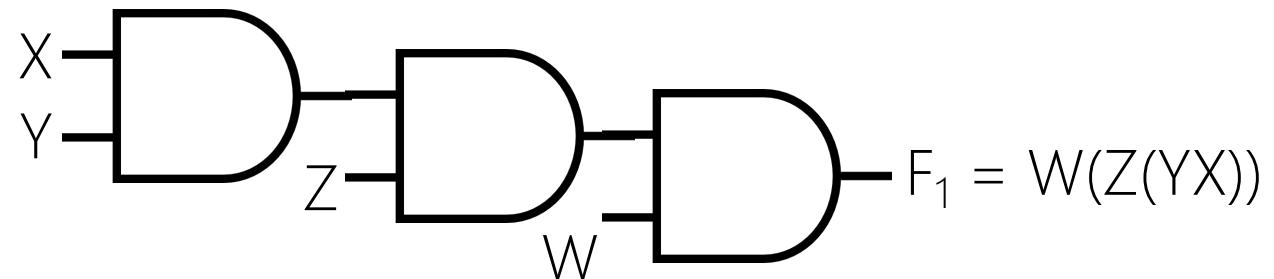


$F = WZYX$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)	Hmm, 3 levels, No!	Yes! 2 levels
Min. Cost	3 gates, Yes	3 gates, Yes

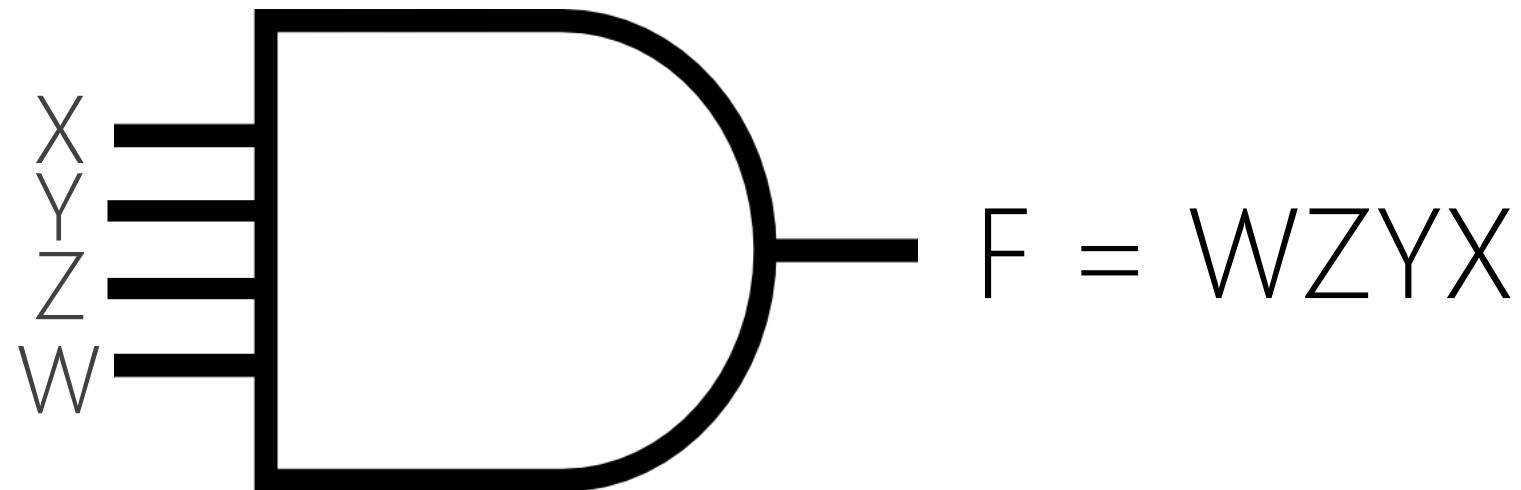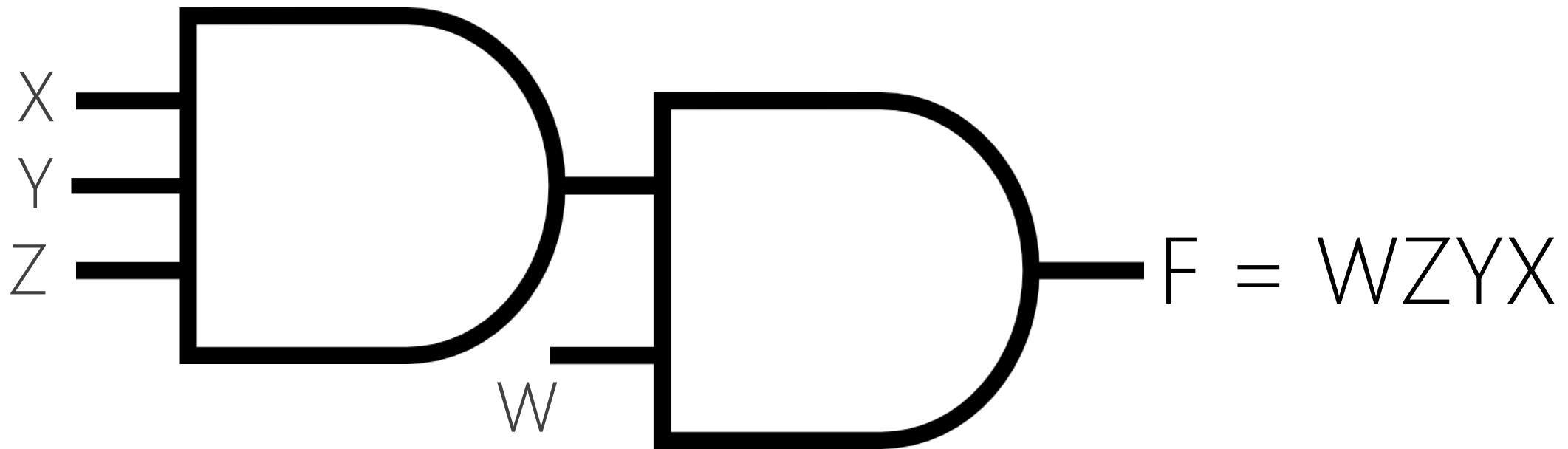


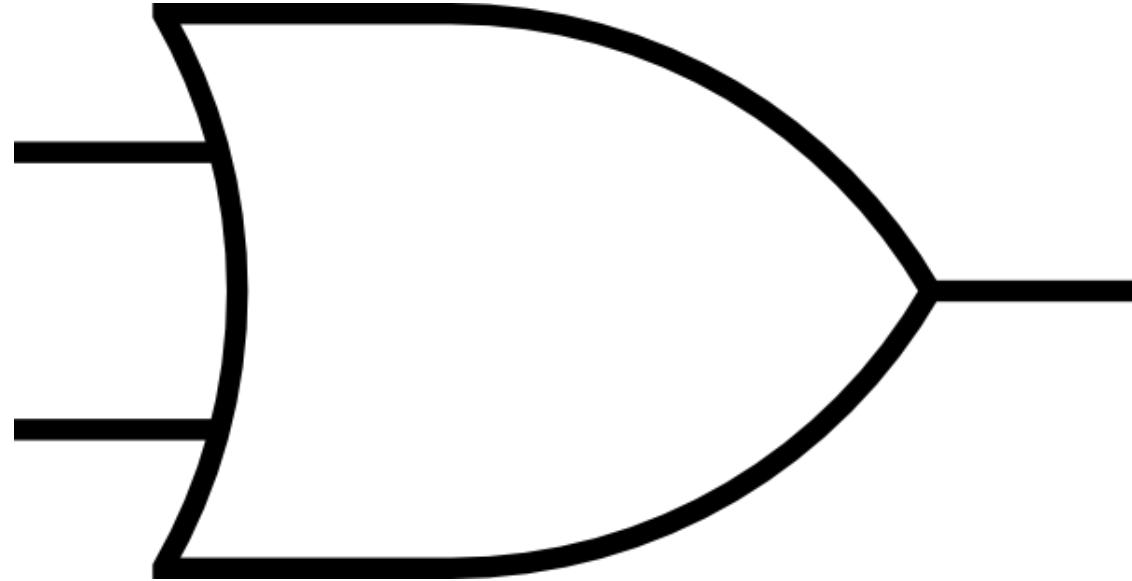

OR

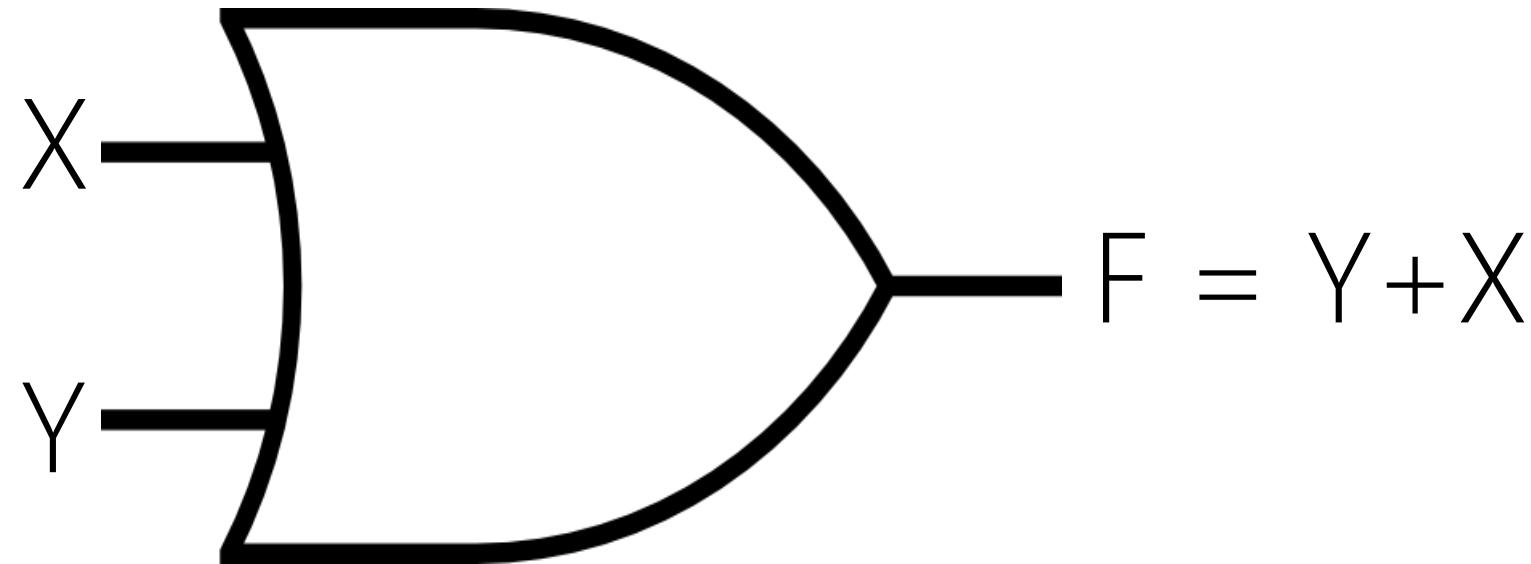


Y	X	Y OR X	Y+X
0	0		0
0	1		1
1	0		1
1	1		1

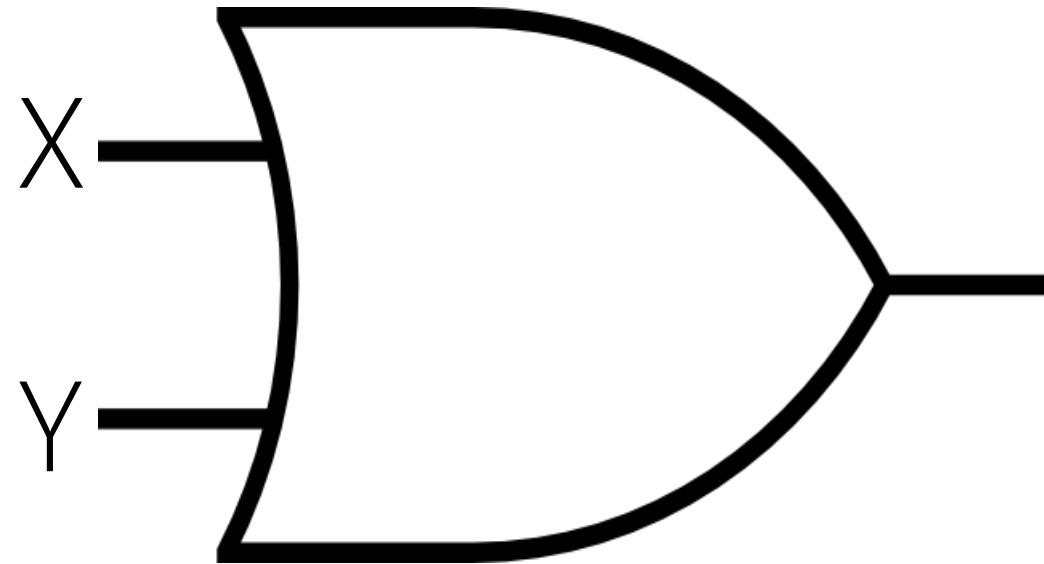


$F = Y + X = X + Y$
Commutative

X	Y	X OR Y	X+Y
0	0		0
0	1		1
1	0		1
1	1		1

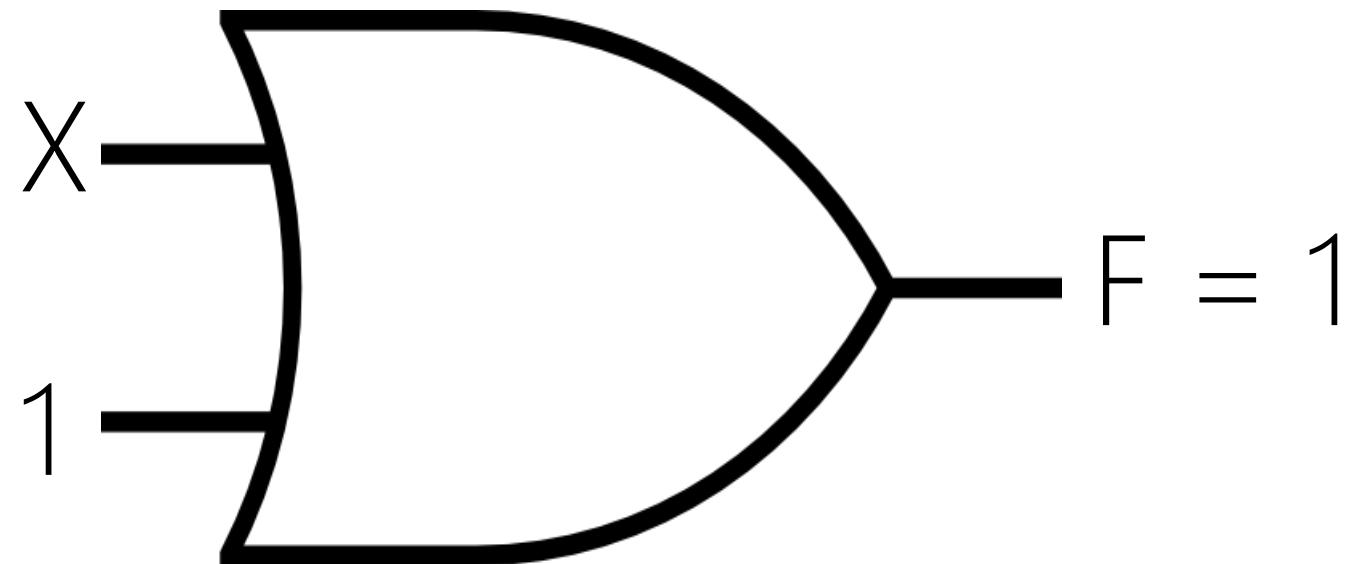


Y	X	Y+X
1	0	1
1	1	1

$$F = X + 1 = 1$$

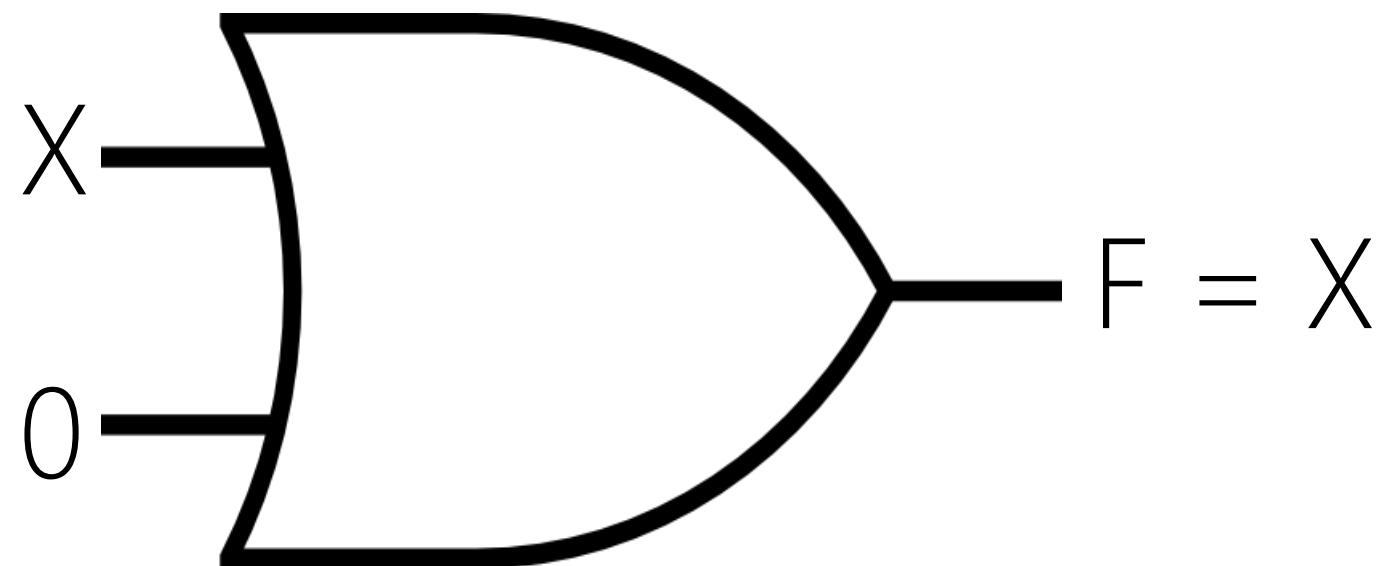


Y	X	$Y+X$
0	0	0
0	1	1

$$F = X + 0 = X$$

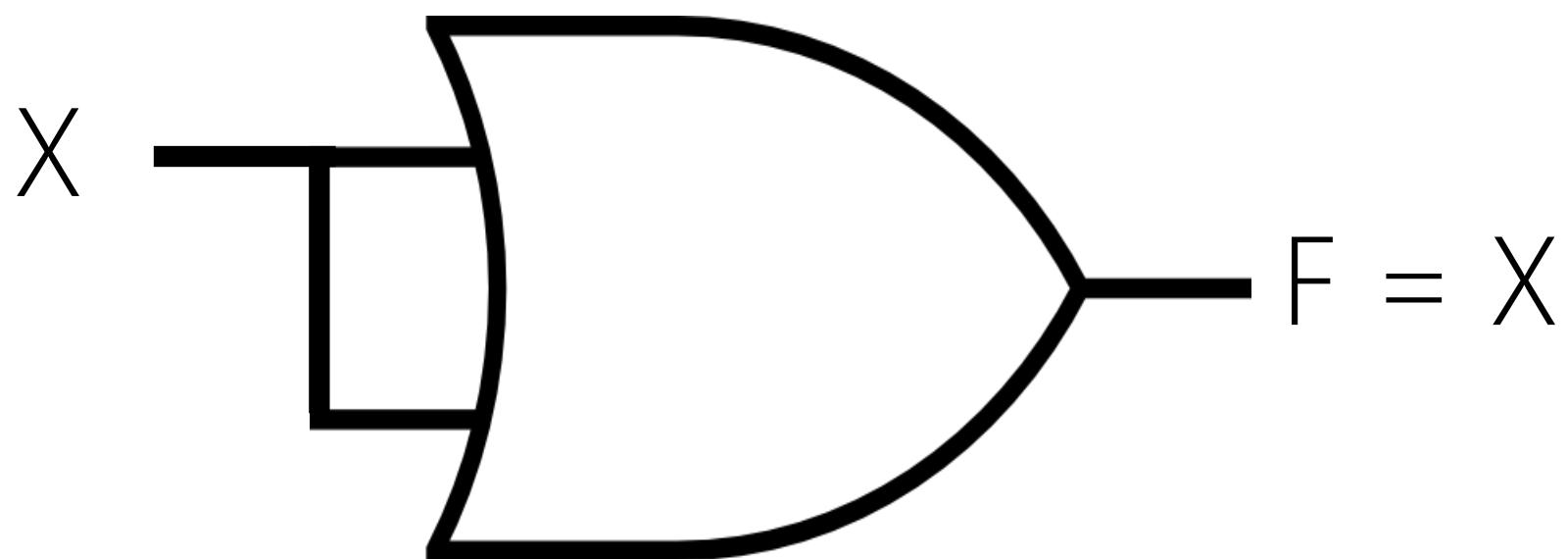

X	X	$X+X$
0	0	0
1	1	1


$$F = X+X = X$$

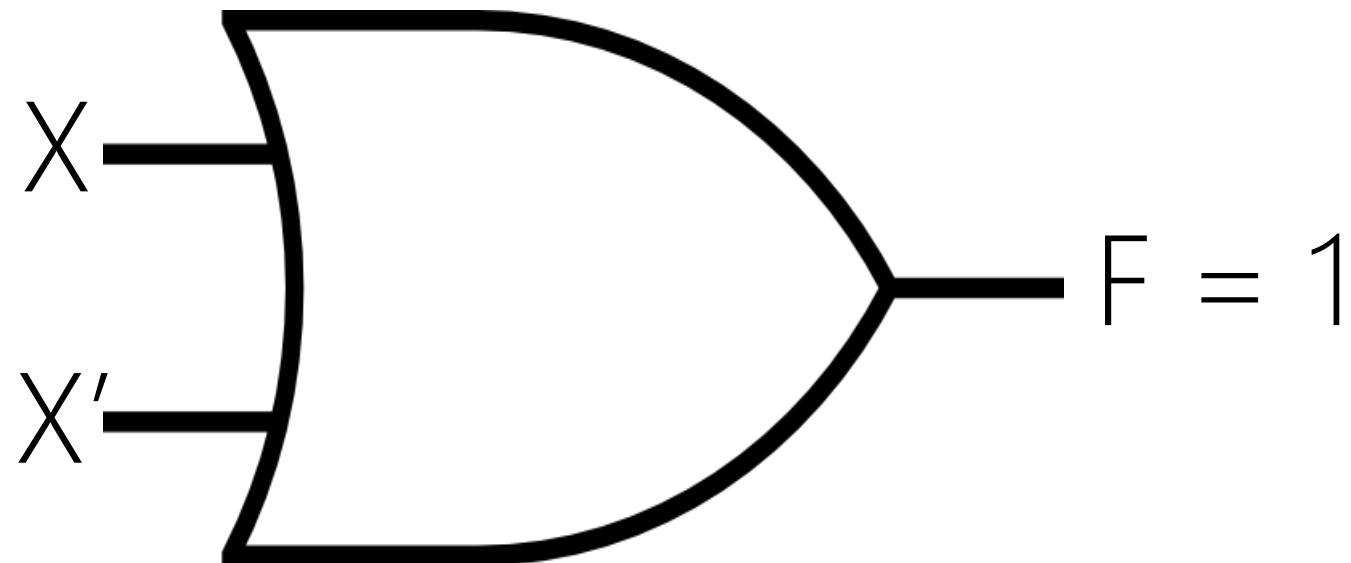


X'	X	$X' + X$
1	0	1
0	1	1

$$F = X + X' = 1$$

3-INPUT OR

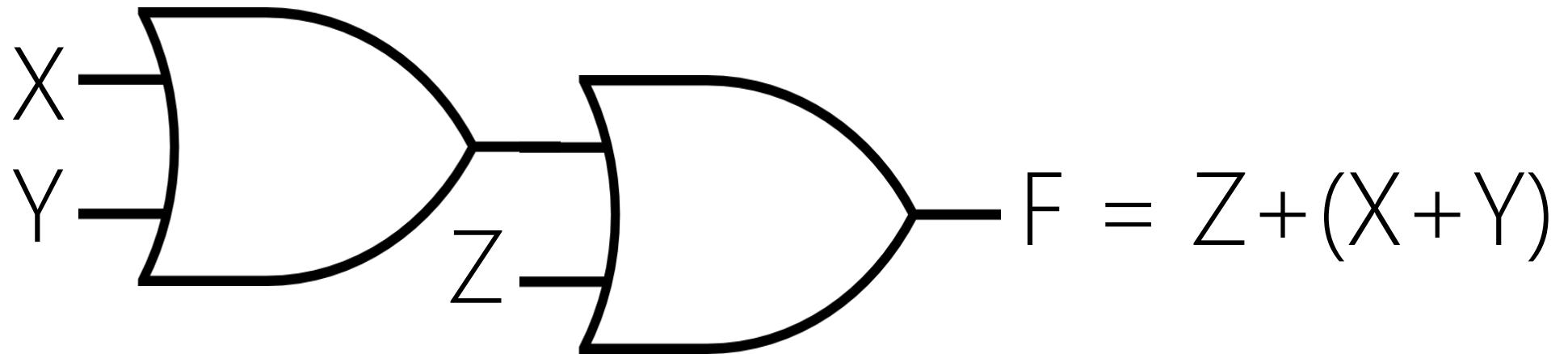


Z	Y	X	$Z+(X+Y)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

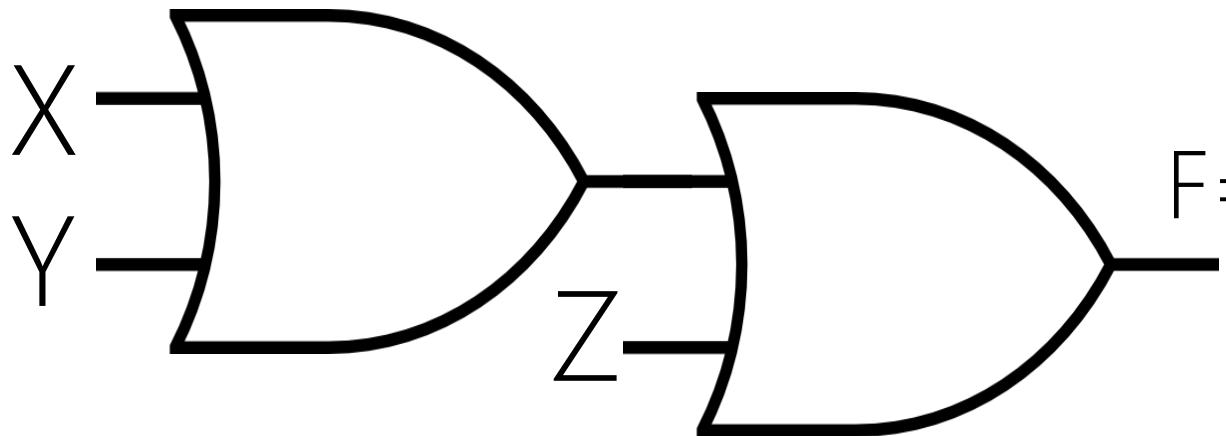



$$\begin{aligned}
 F &= Z + (Y + X) = Z + (X + Y) = (Z + X) + Y \\
 &= Z + Y + X
 \end{aligned}$$


Associative

Z	Y	X	$Z + (Y + X)$	$Z + (X + Y)$	$(Z + X) + Y$	ZXY
0	0	0			0	
0	0	1			1	
0	1	0			1	
0	1	1			1	
1	0	0			1	
1	0	1			1	
1	1	0			1	
1	1	1			1	

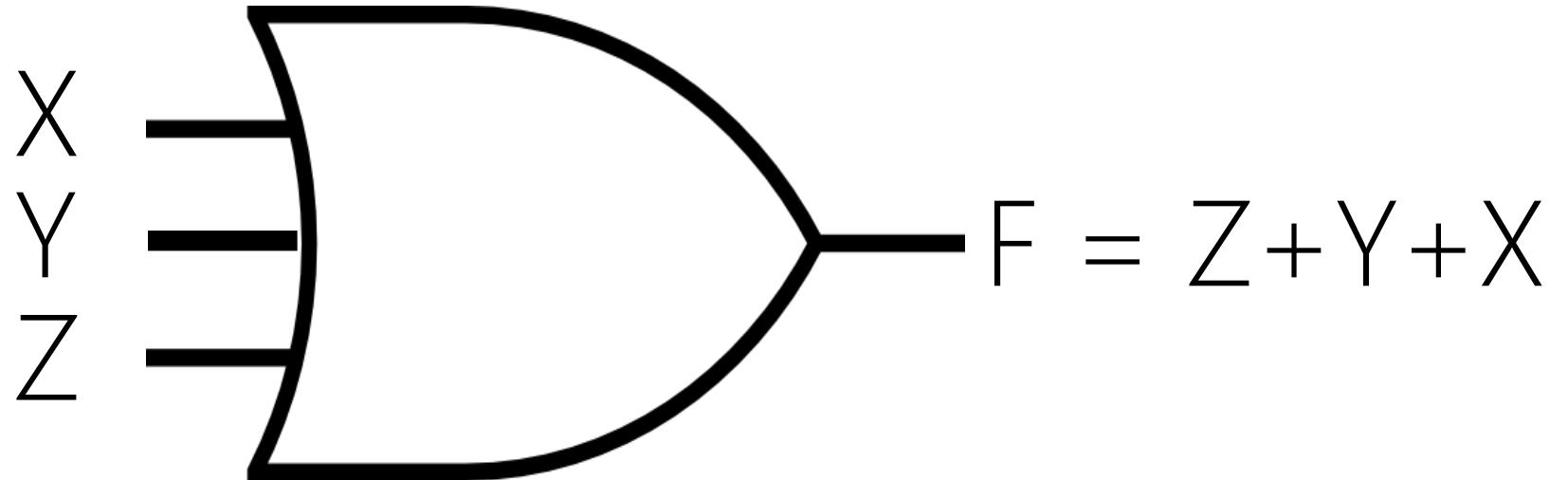


Z	Y	X	$Z+(Y+X)$	$Z+(X+Y)$	$(Z+X)+Y$	ZXY
0	0	0			0	
0	0	1			1	
0	1	0			1	
0	1	1			1	
1	0	0			1	
1	0	1			1	
1	1	0			1	
1	1	1			1	

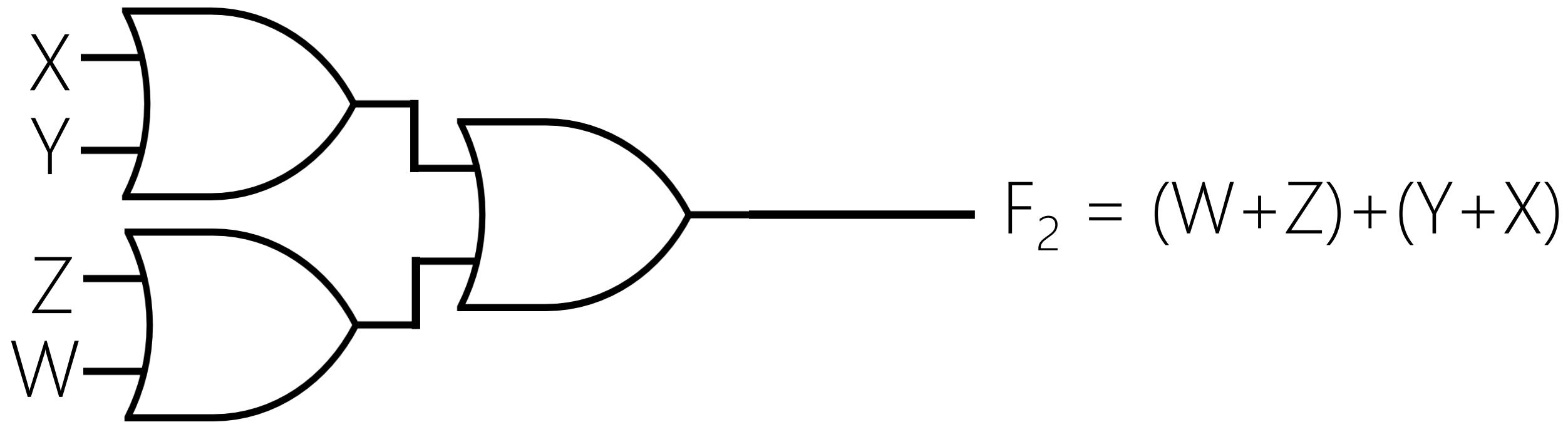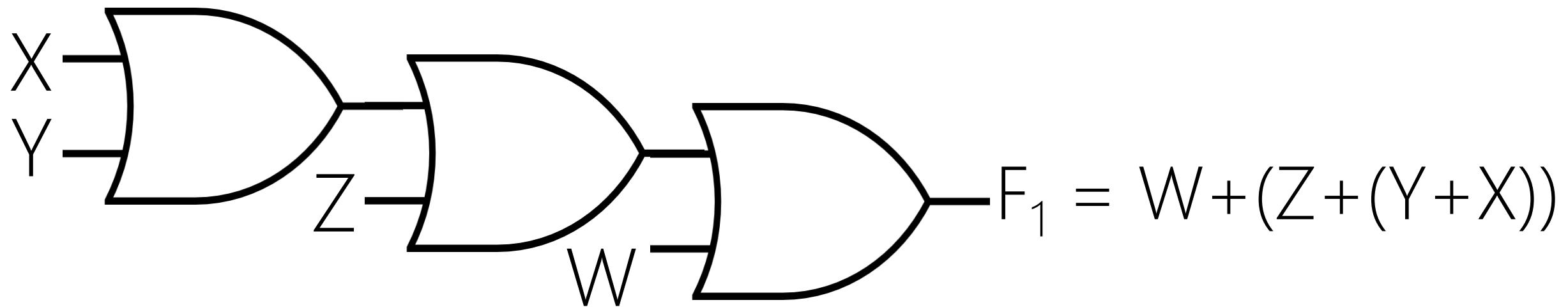

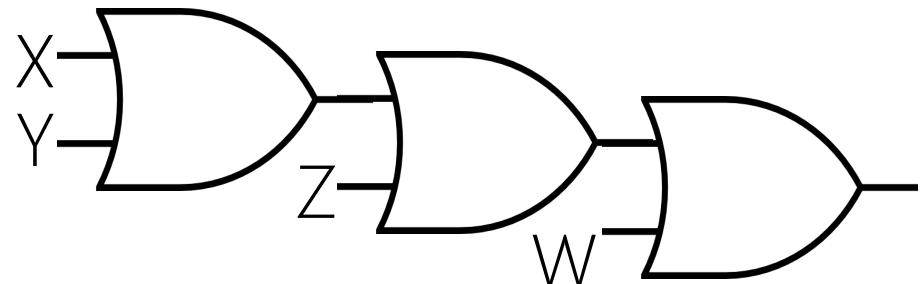

$$F_1 = W + (Z + (Y + X))$$

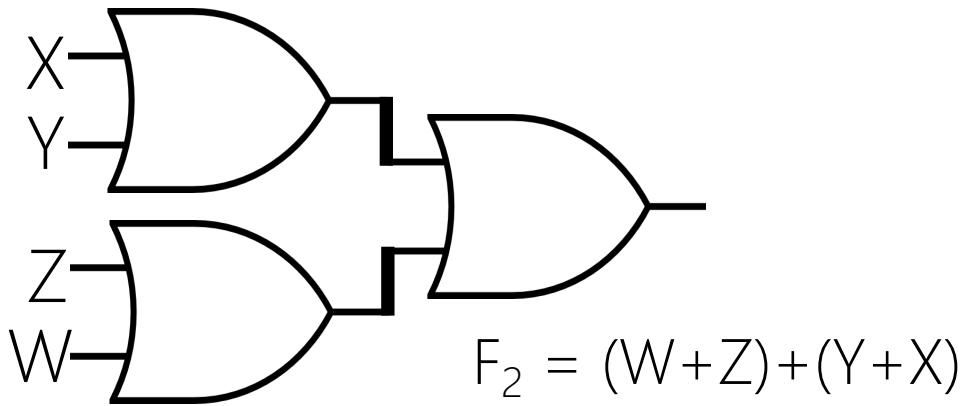


$$F_2 = (W + Z) + (Y + X)$$


$F = W + Z + Y + X$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)	Hmm, 3 levels, No!	Yes! 2 levels
Min. Cost	3 gates, Yes	3 gates, Yes

ANALYSIS I


System analysis is given the structure of a system, find its functionality.

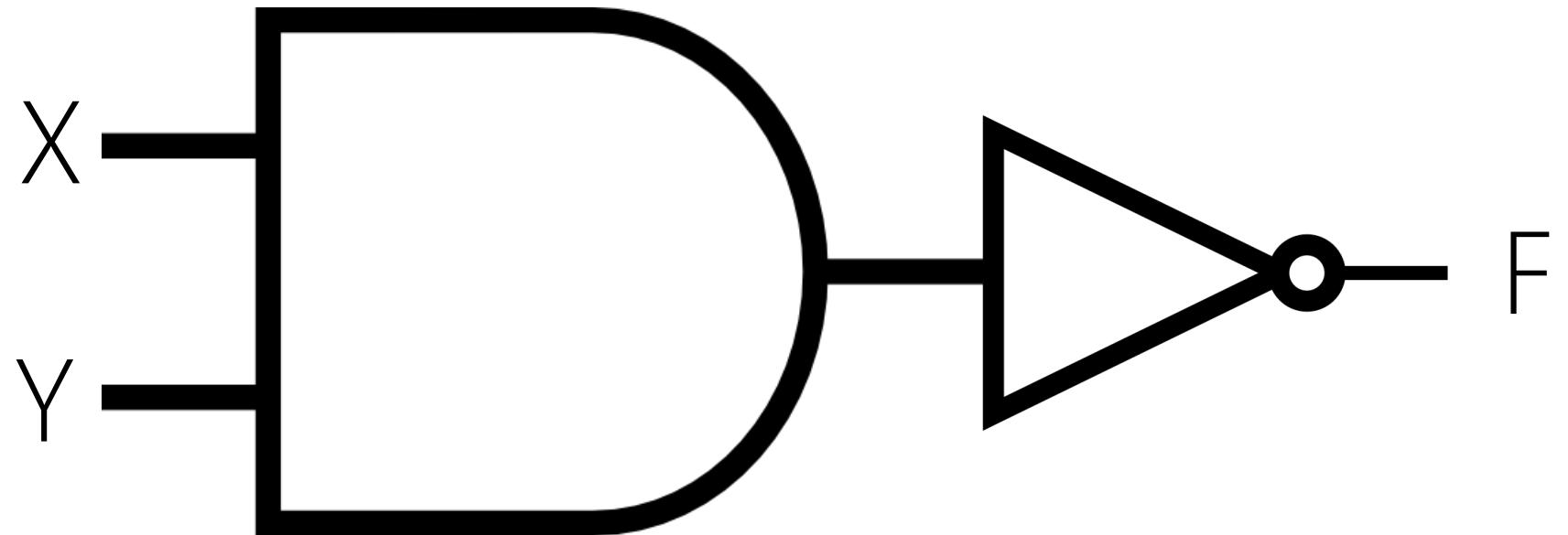Determine the functionality exhibited by a structure.




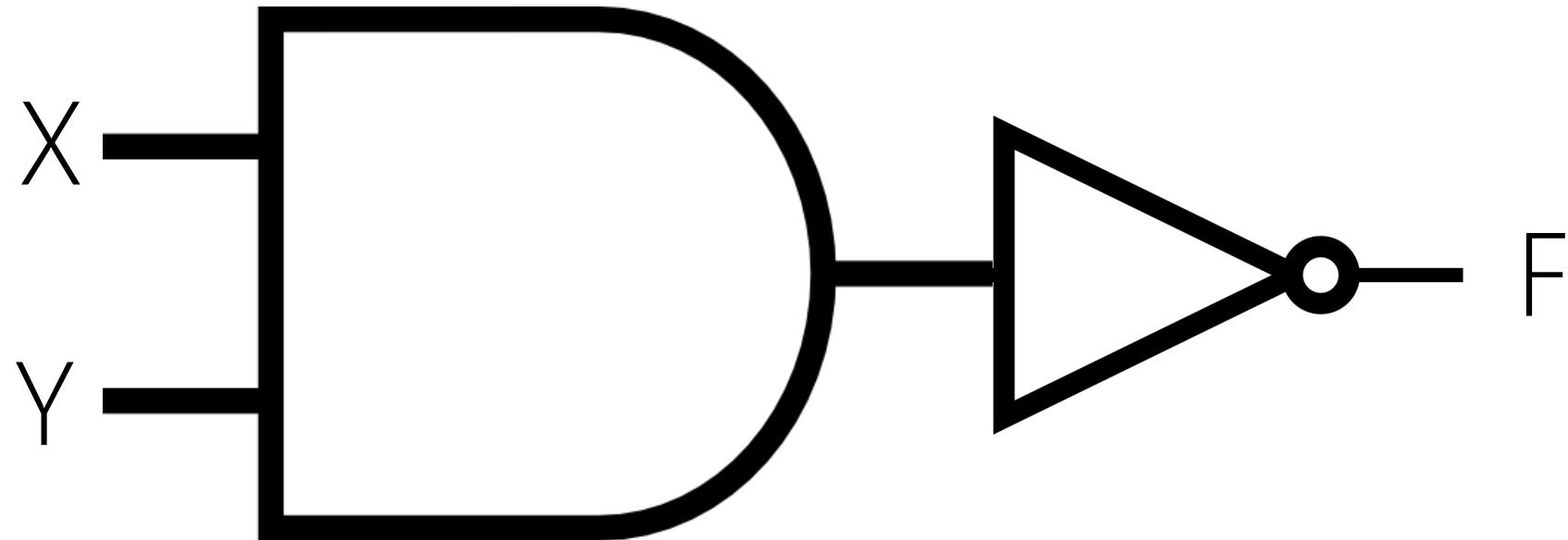


Y	X	$F = ?$
0	0	?
0	1	?
1	0	?
1	1	?

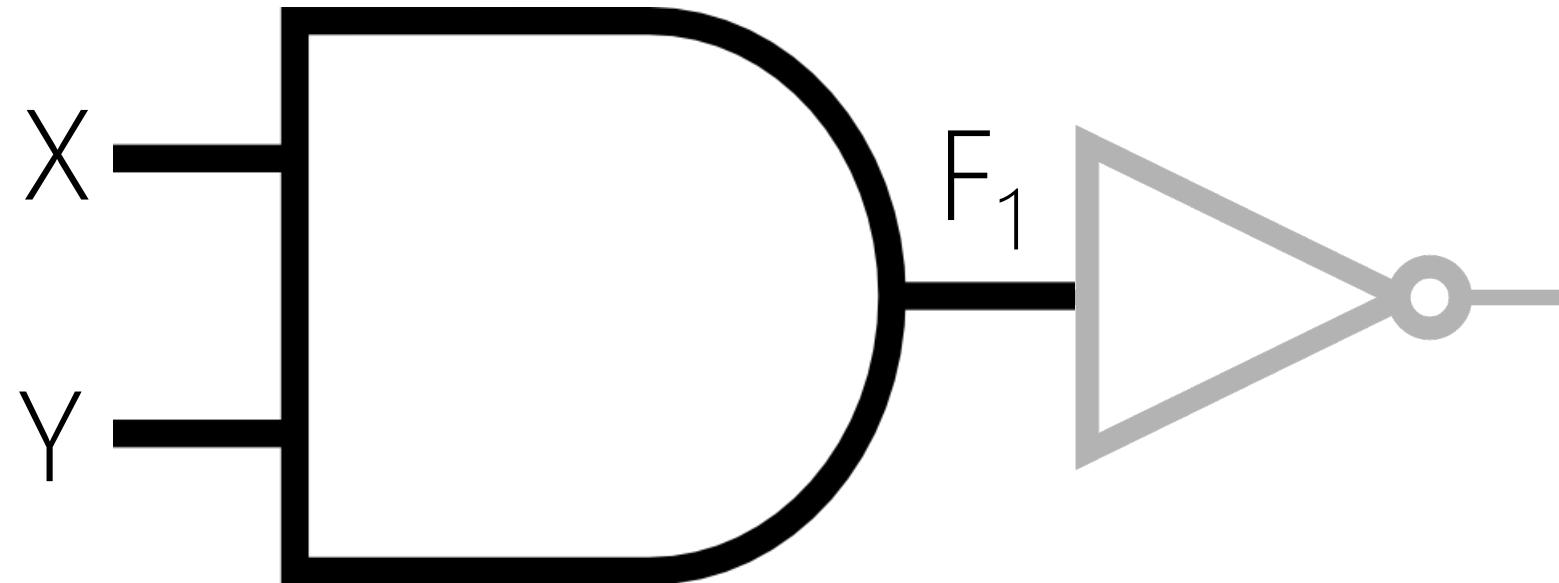


Y	X	$F_1 = YX$
0	0	0
0	1	0
1	0	0
1	1	1

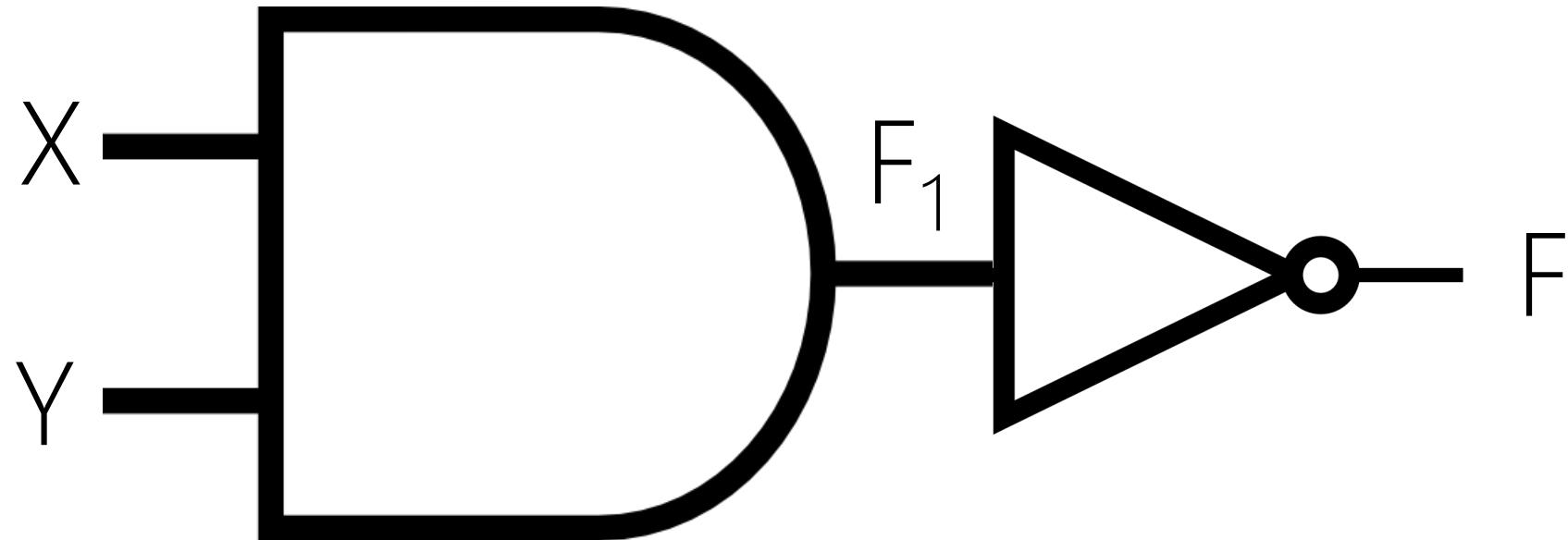


Y	X	$F_1 = YX$	$F = (YX)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

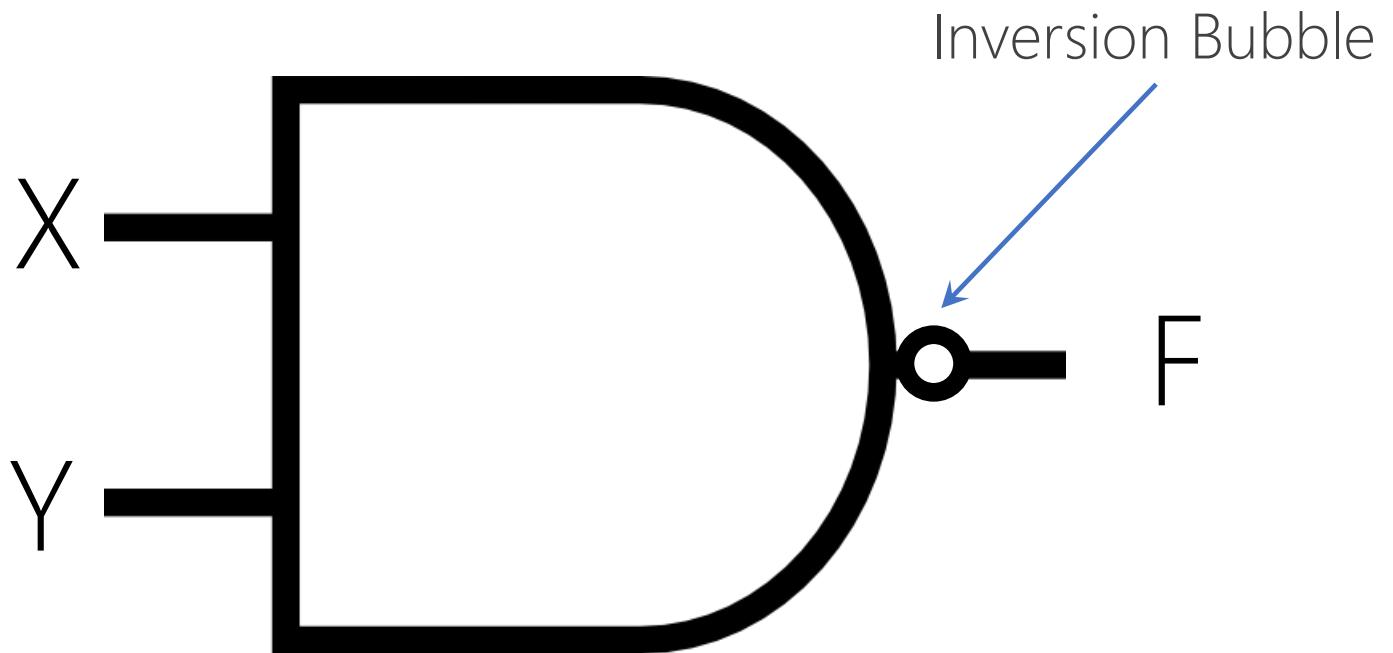

NAND (Not – AND)

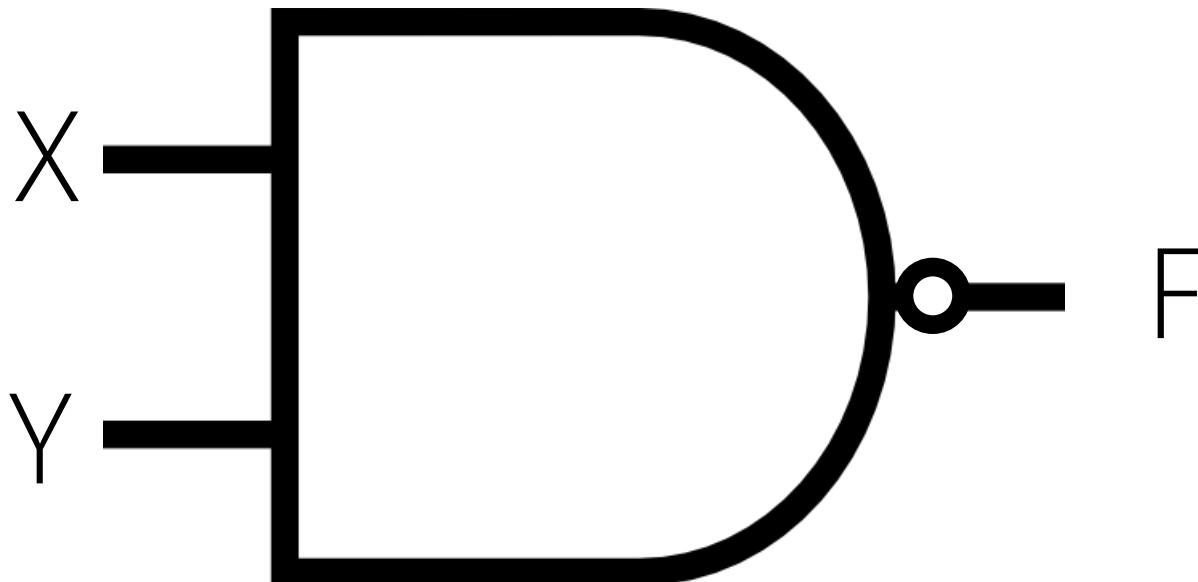


Y	X	$F = (YX)'$	$F=Y \uparrow X$
0	0	1	
0	1	1	
1	0	1	
1	1	0	

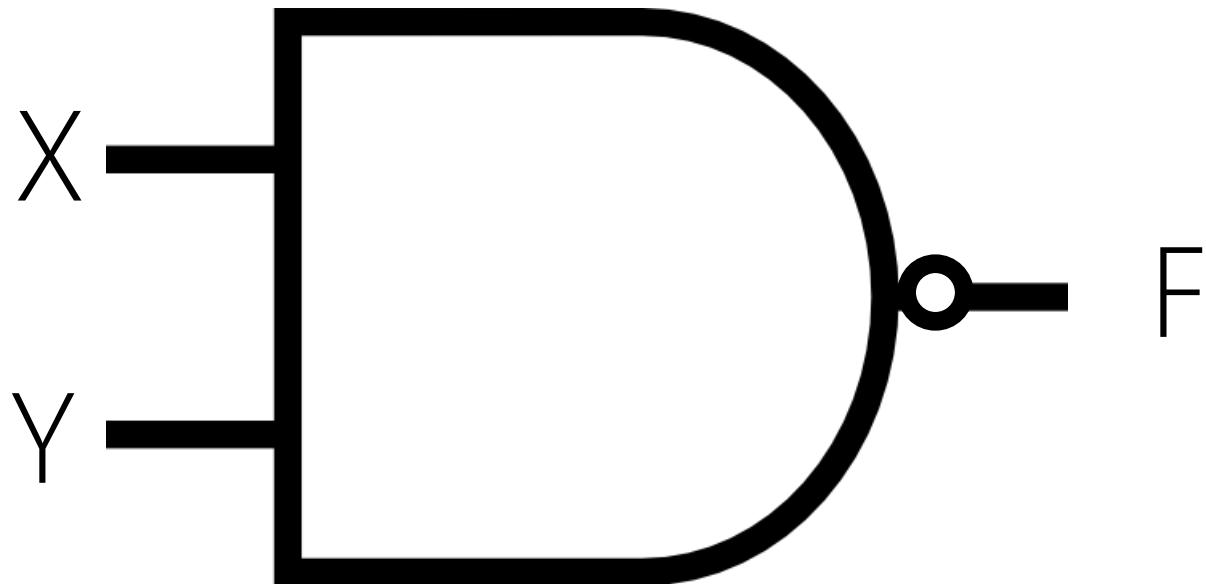

$$F = (YX)' = (XY)' = Y \uparrow X = X \uparrow Y$$

Commutative

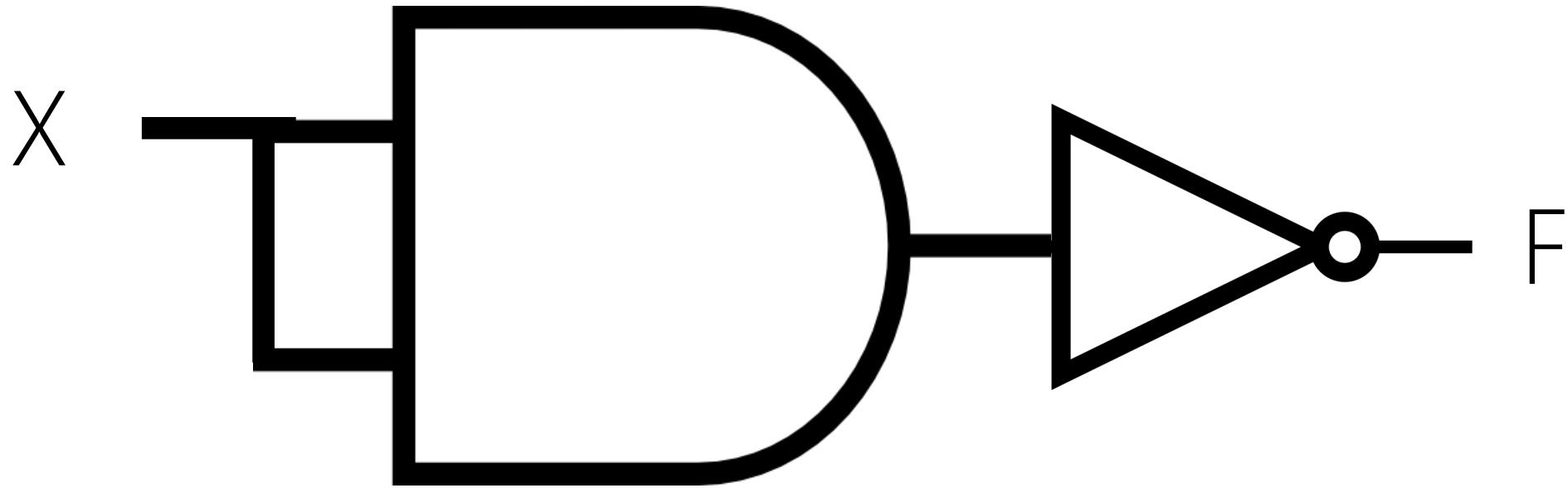


X

$F = ?$

0

1

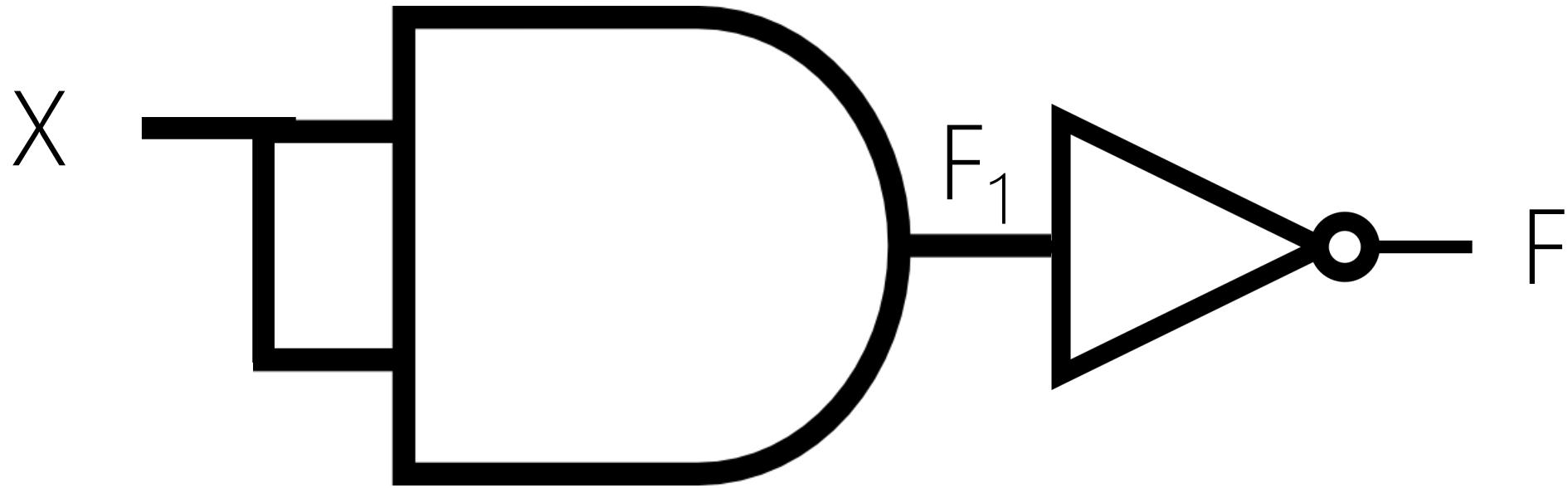

X

$$F_1 = XX$$


0

0

1

1

$F = ?$

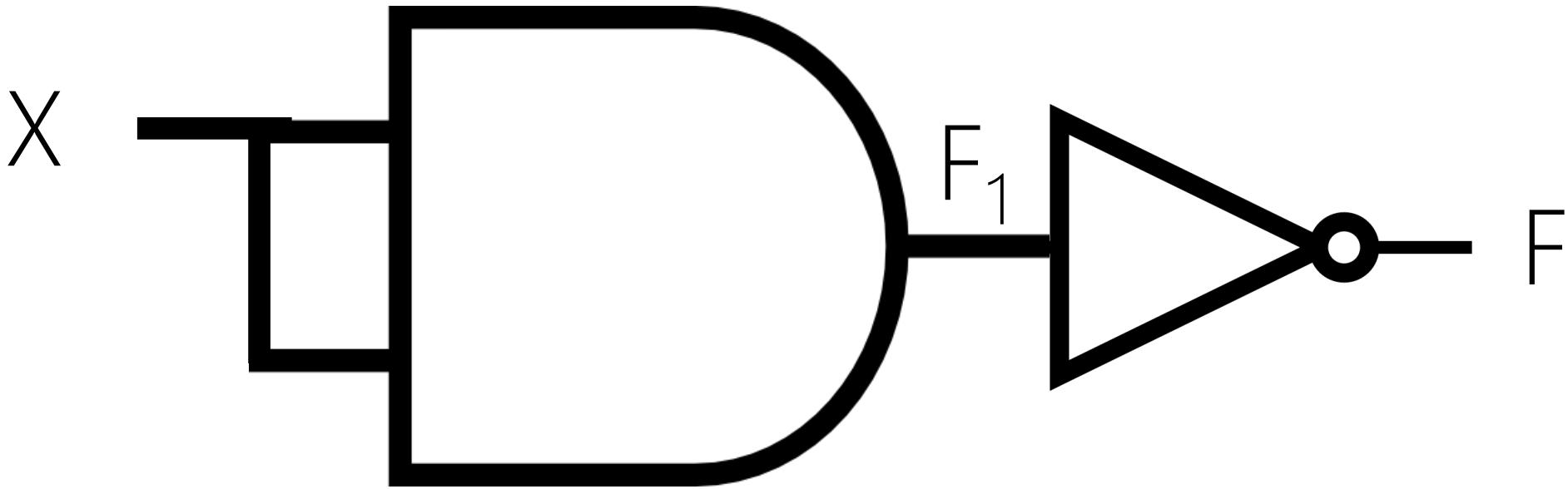

X

$F_1 = XX$

$F = (XX)'$

0


0

1

1

1

0

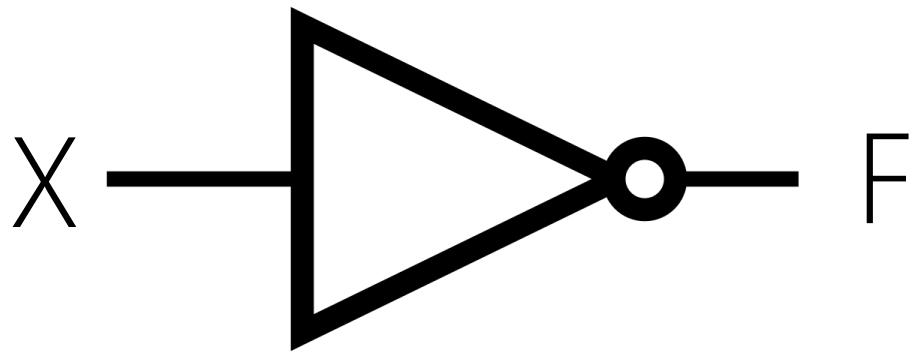

X

$$F = (XX)' = X \uparrow X = X'$$

0


1

1


0

3-INPUT NAND


Z	Y	X	F=(ZYX)'
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

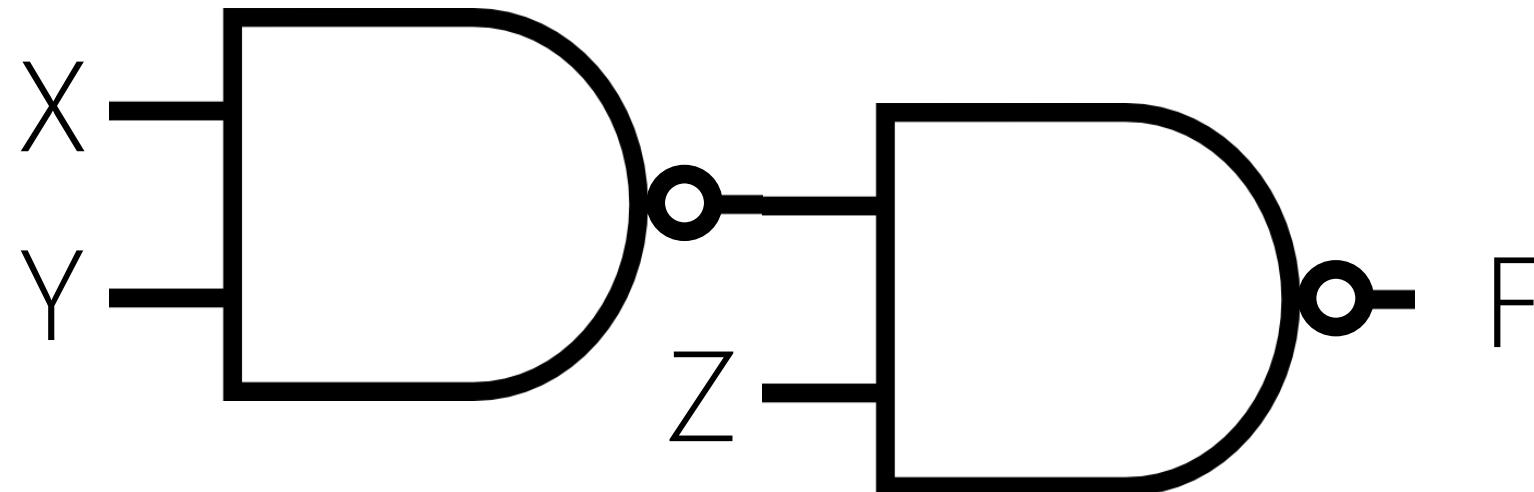


Z	Y	X	F = ?
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

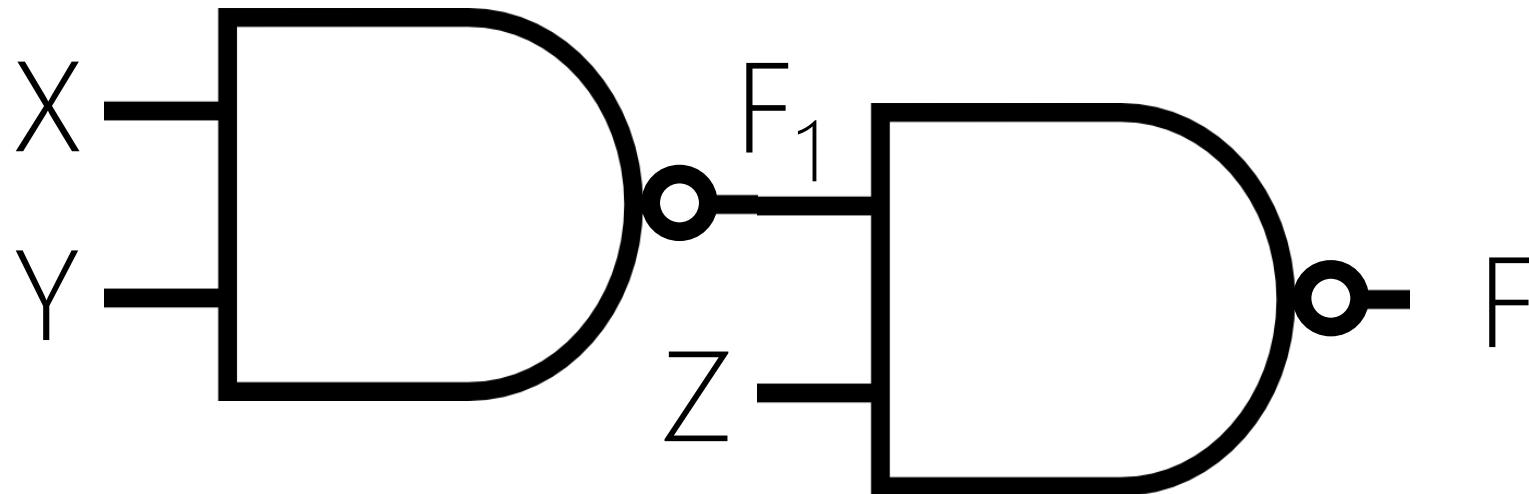

Z	Y	X	$F_1 = (YX)'$	F = ?
0	0	0	1	
0	0	1	1	
0	1	0	1	
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	1	
1	1	1	0	

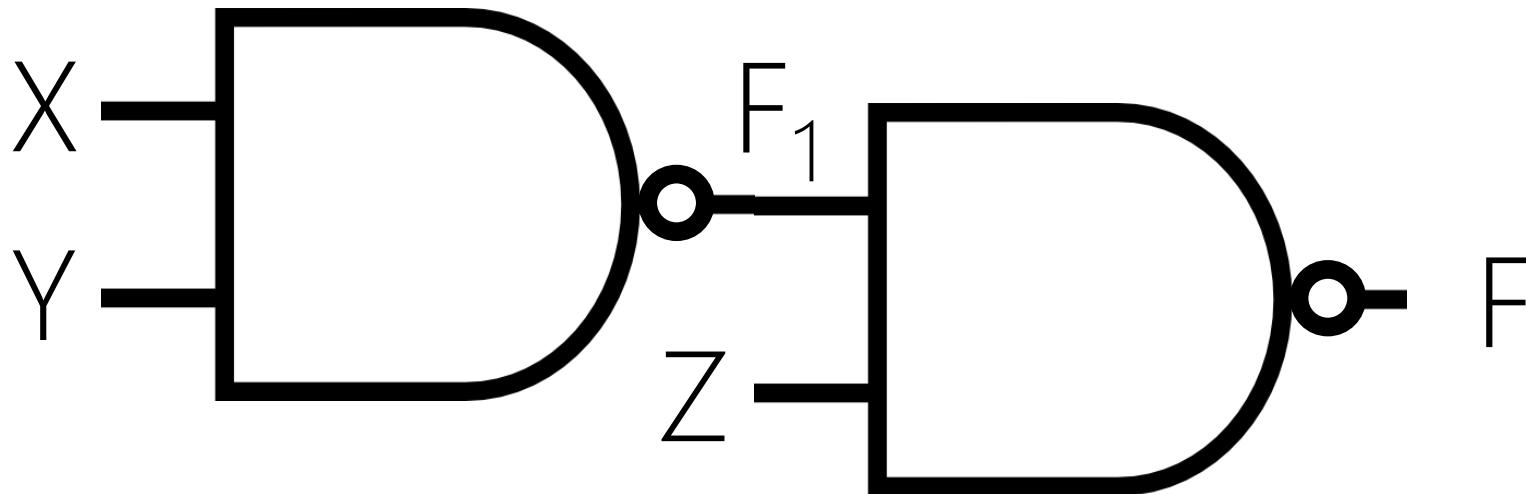


Z	Y	X	$F_1 = (YX)'$	$F = (ZF_1)' = (Z(YX))'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

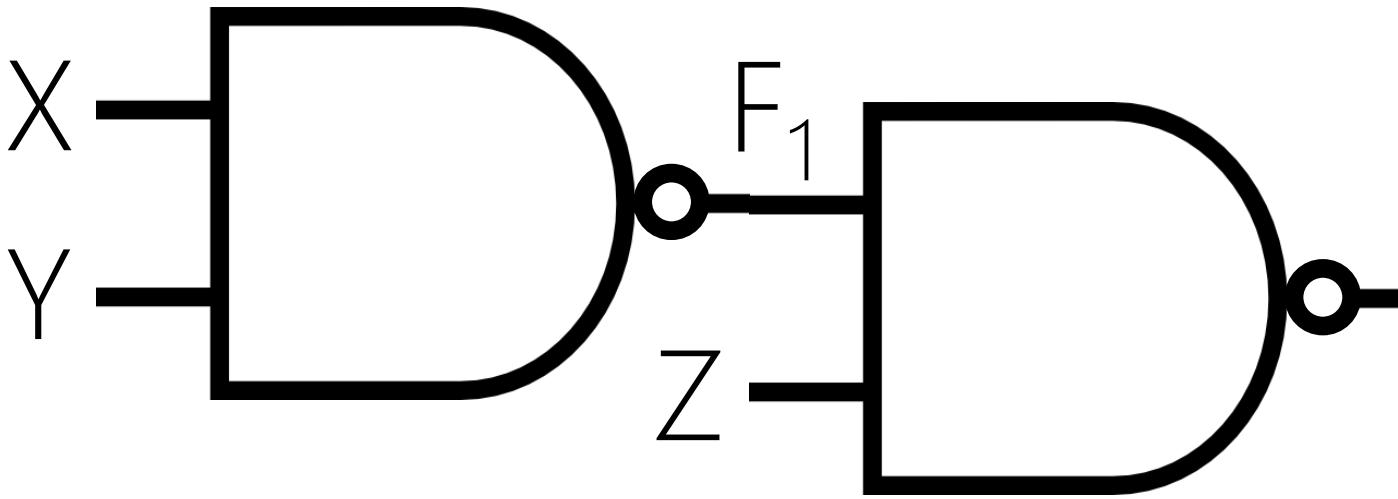


$$F = (Z(YX)')' \\ \neq (ZYX)'$$

Z	Y	X	$F_1 = (YX)'$	$F = (ZF_1)' = (Z(YX))'$	$F = (ZYX)'$
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	0	1	0


NOT (3-INPUT AND)

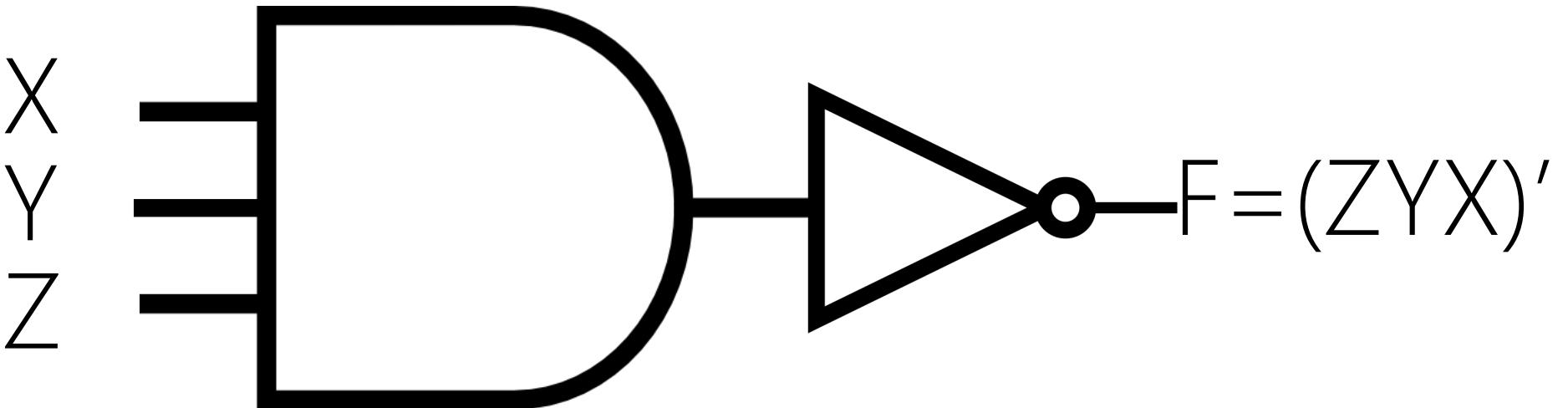


Z	Y	X	F=(ZYX)'	F=(ZYX)'
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

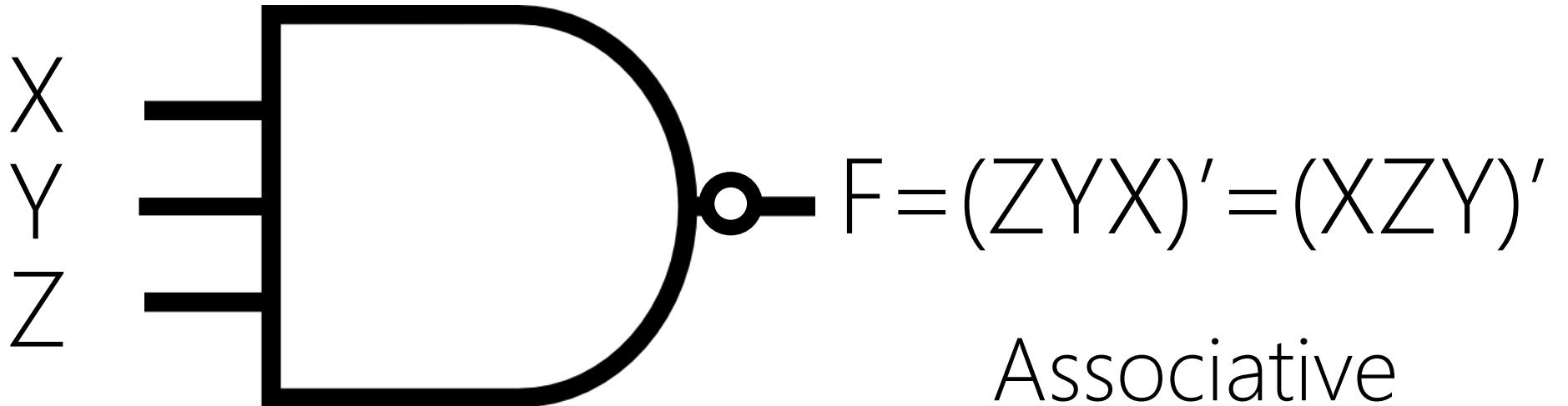

Z	Y	X	$F = (ZYX)'$	$F = (Z(YX))'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

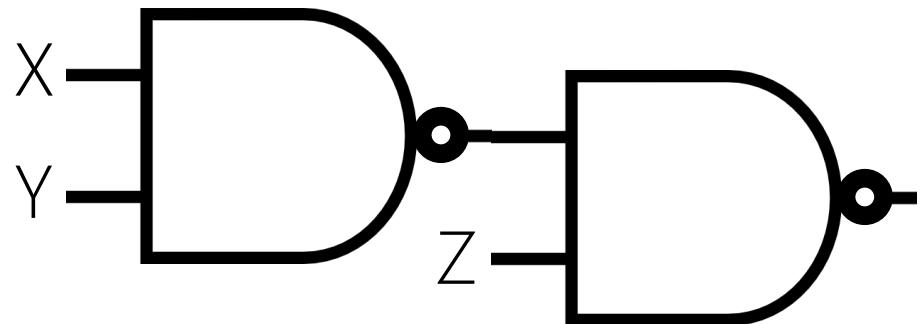


$$F_1 = (Z(YX))'$$

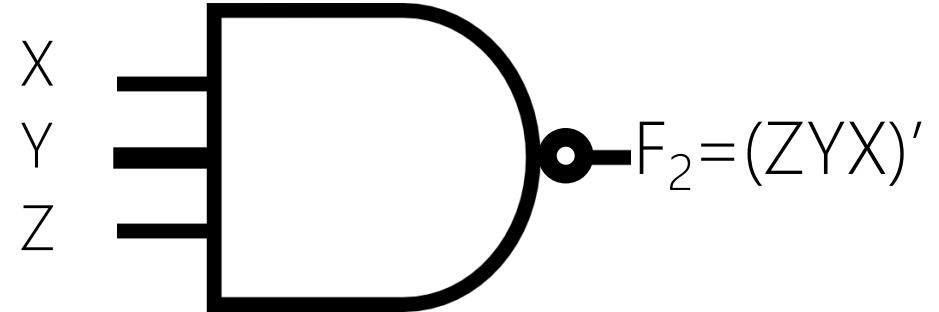

$$F_2 = (ZYX)'$$

$F = (ZYX)'$	F_1	F_2
Effective (True)	No!	Yes
Efficient (Fast)
Min. Cost

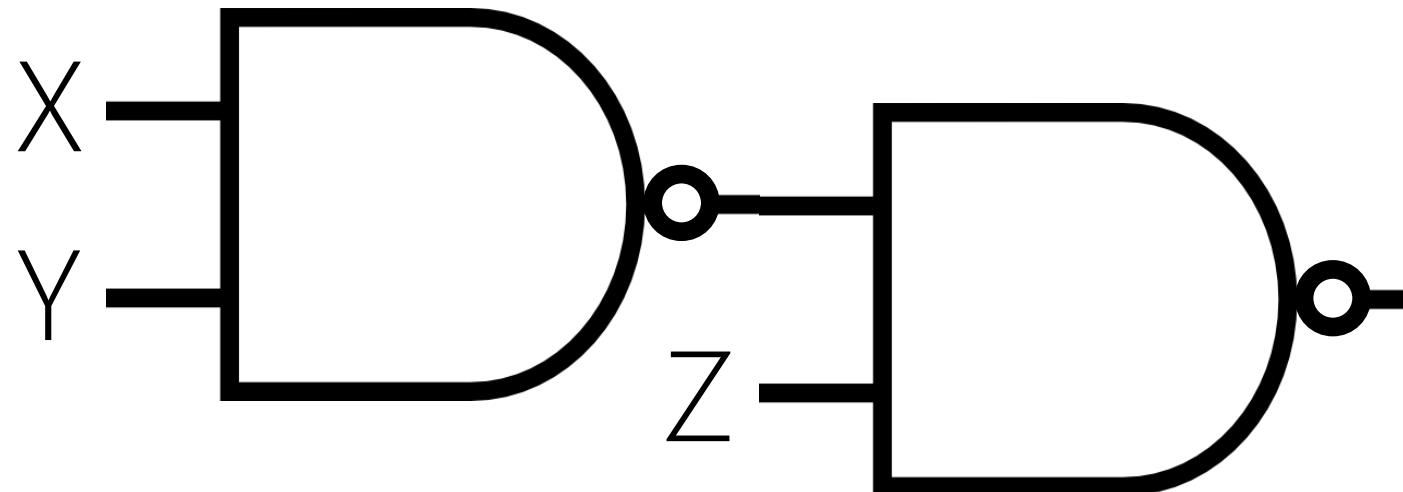

$$F = Z \uparrow (Y \uparrow X)$$


Associative?


Z	Y	X	$F = (Z(YX))' = Z \uparrow (Y \uparrow X)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

ANALYSIS II


System analysis is given the structure of a system, find its functionality.

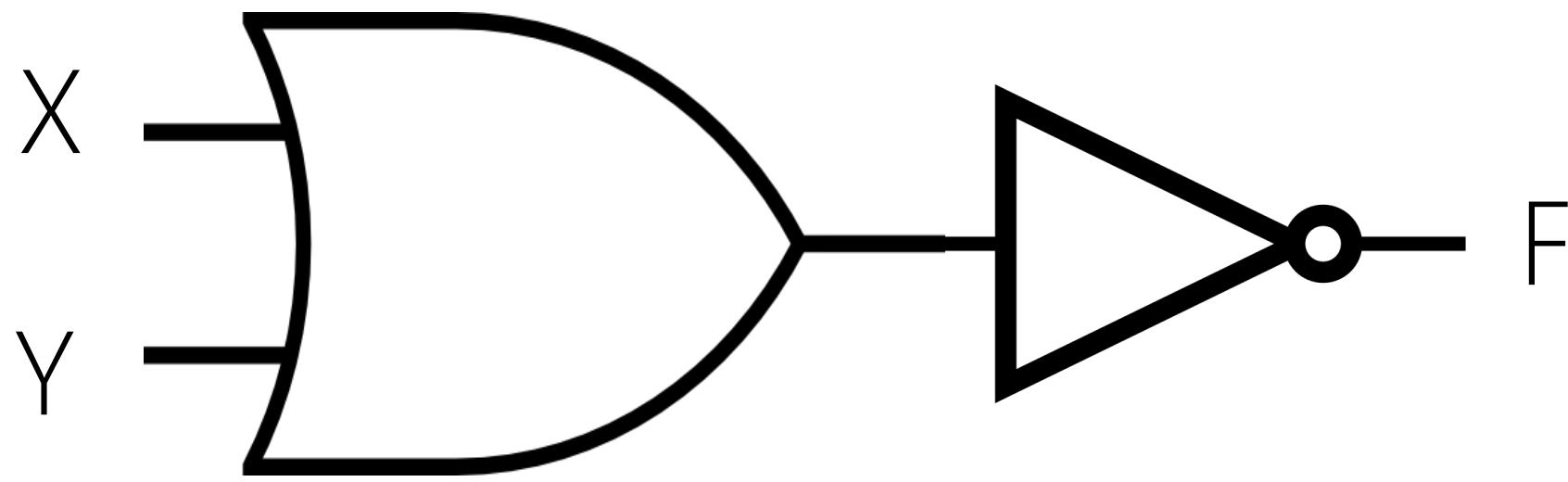Determine the functionality exhibited by a structure.




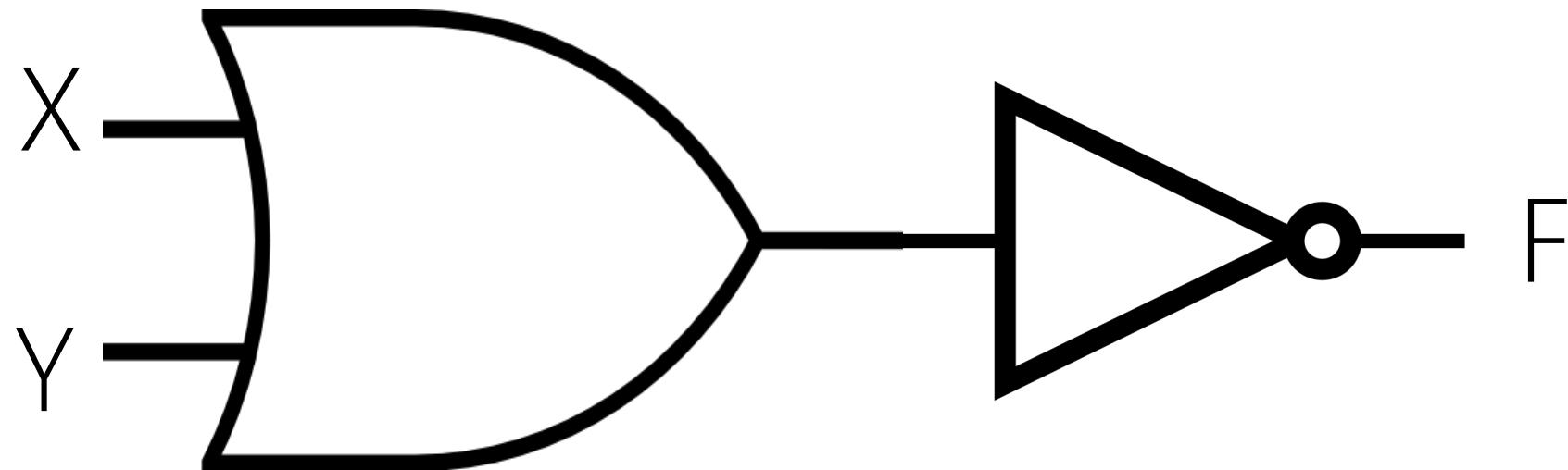


Y	X	$F = ?$
0	0	?
0	1	?
1	0	?
1	1	?

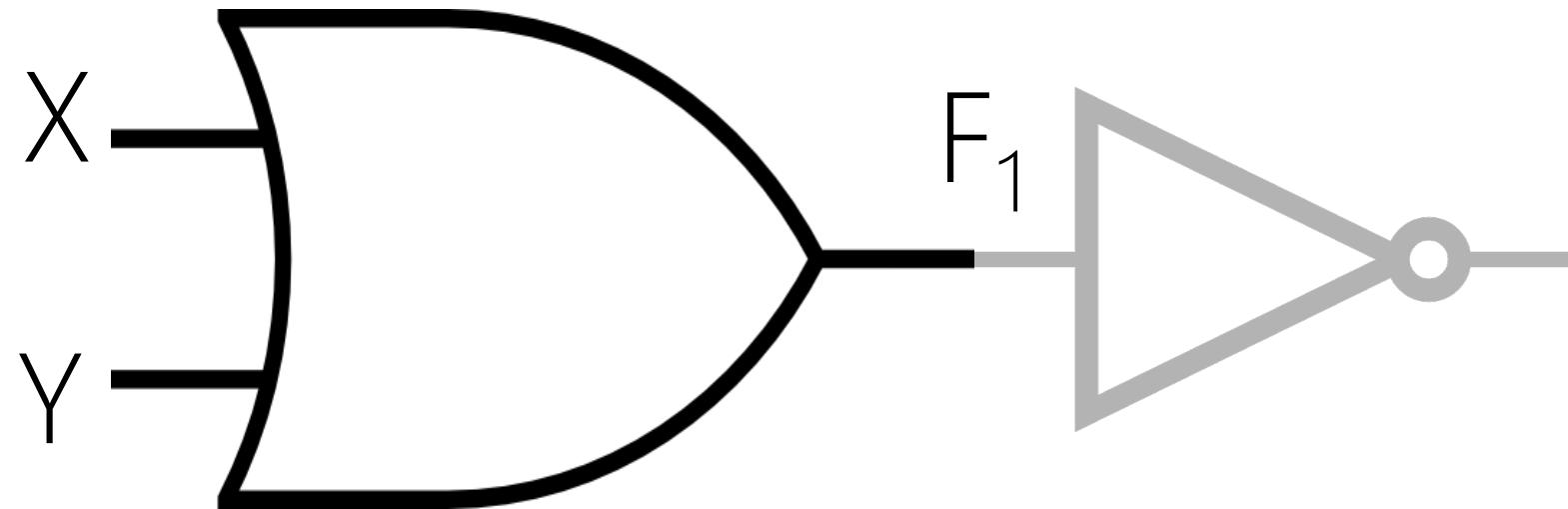


Y	X	$F_1 = Y + X$
0	0	0
0	1	1
1	0	1
1	1	1

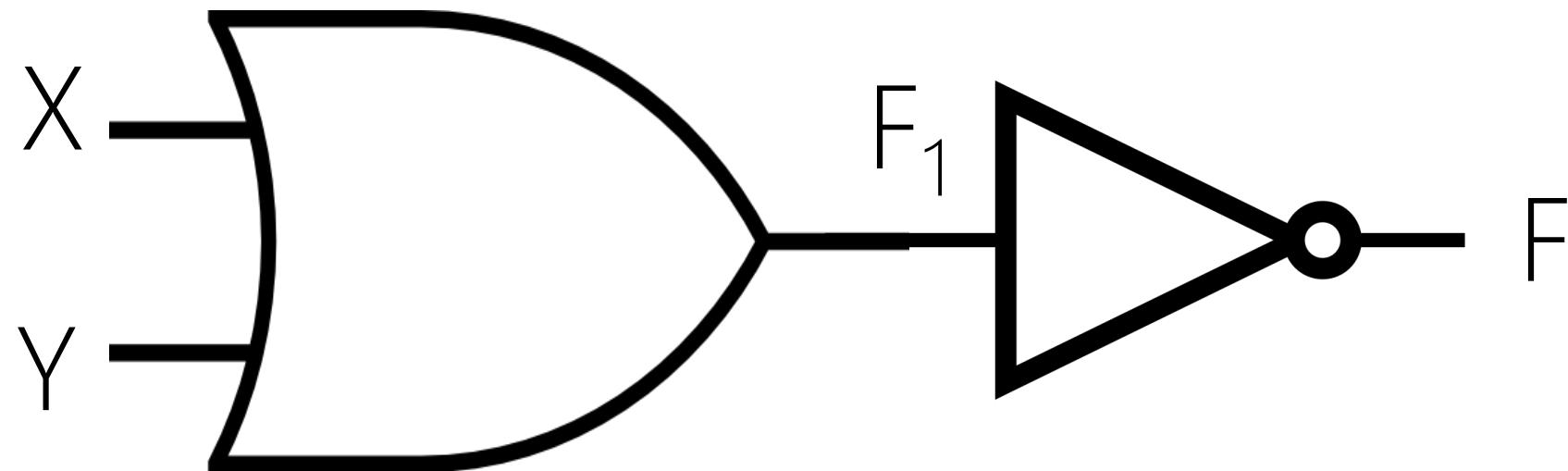


Y	X	$F_1 = Y + X$	$F = (Y + X)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

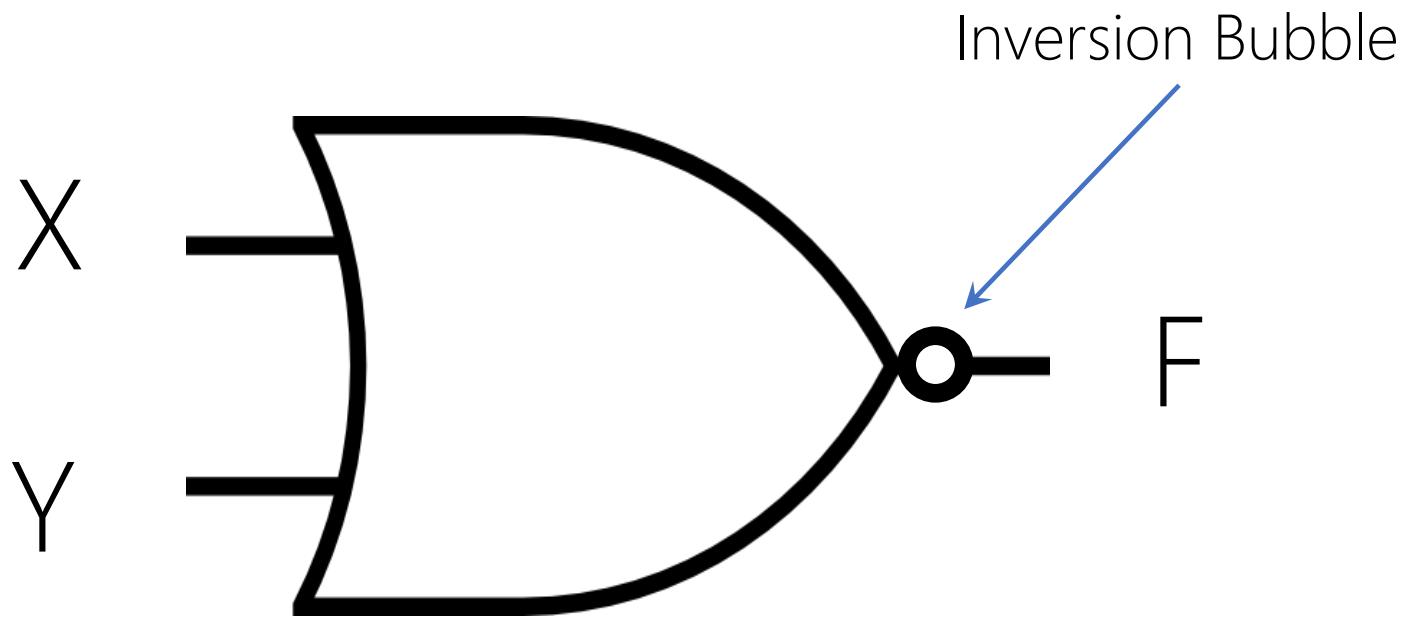

NOR (Not – OR)

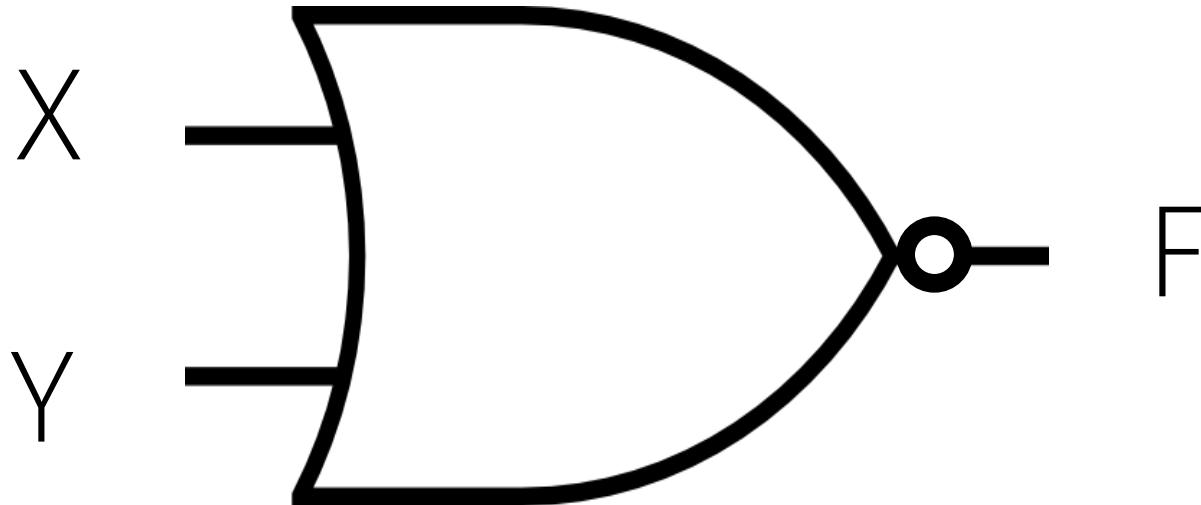


Y	X	$F = (Y+X)'$	$F=Y \downarrow X$
0	0	1	
0	1		0
1	0		0
1	1		0

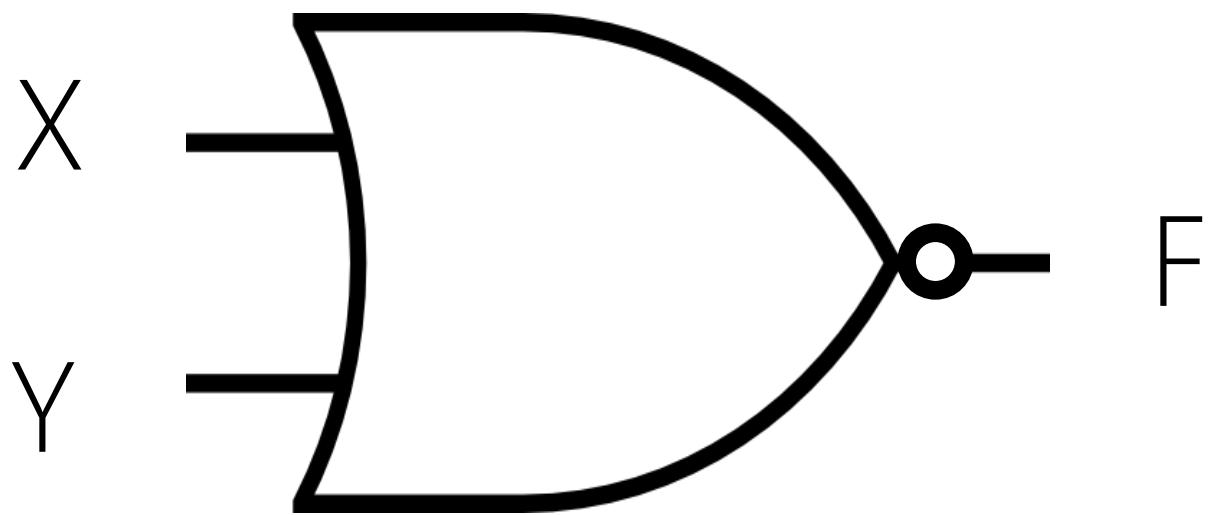


$$F = (Y + X)' = (X + Y)' = Y \downarrow X = X \downarrow Y$$

Commutative

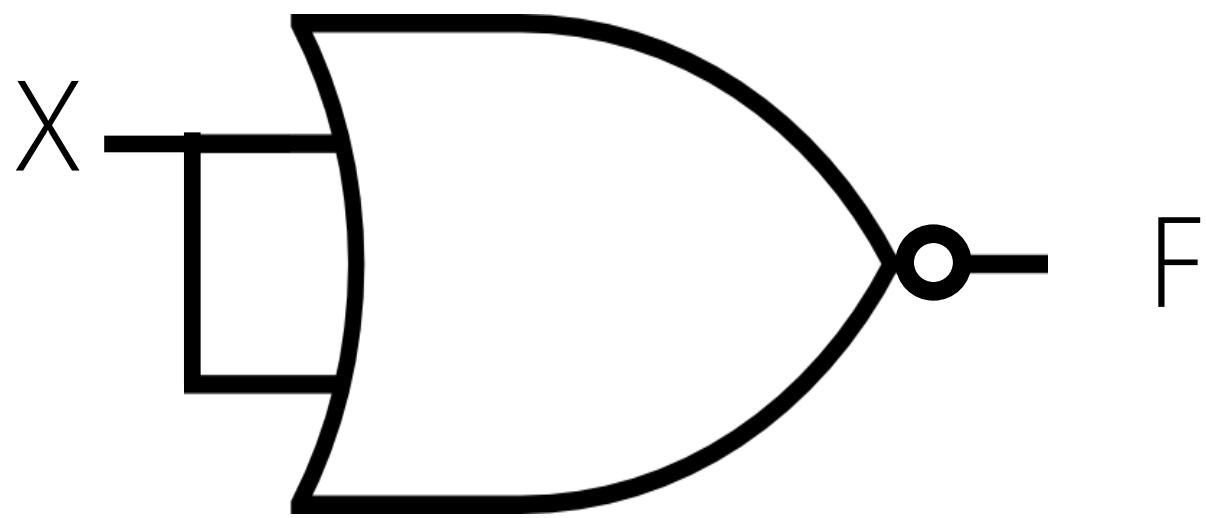

$$F=?$$

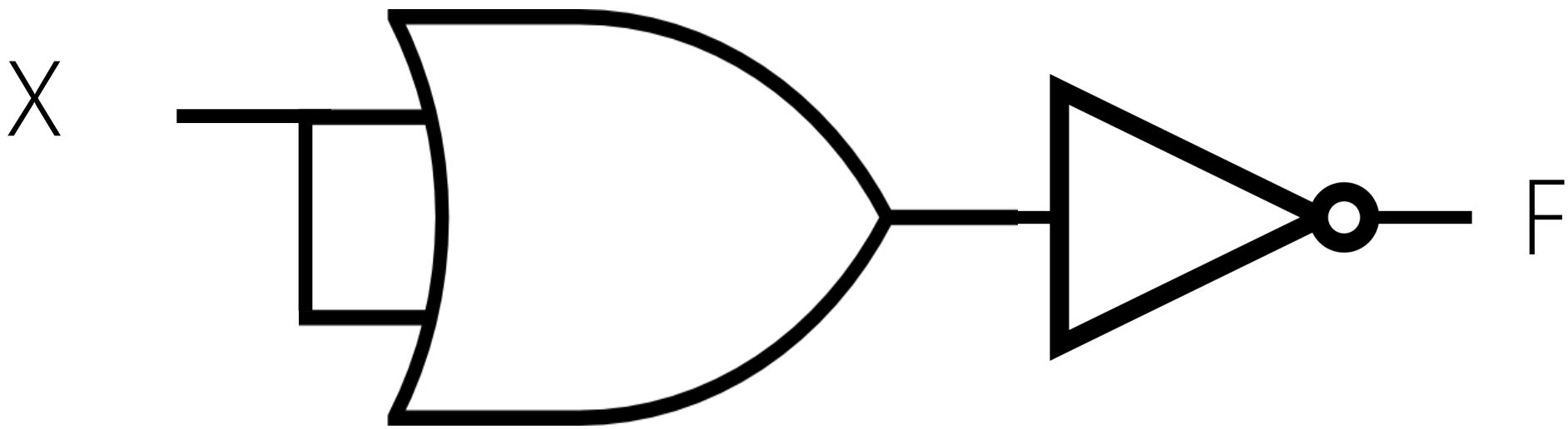


X

$F = ?$

0

1

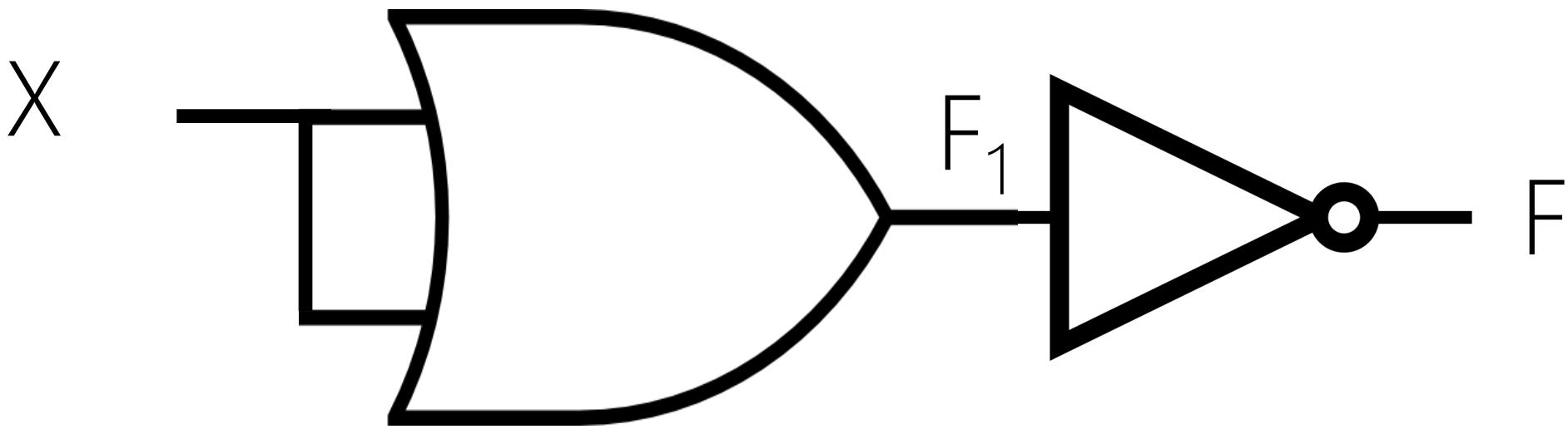

X

$F_1 = X + X$


$F = ?$

0

0

1

1

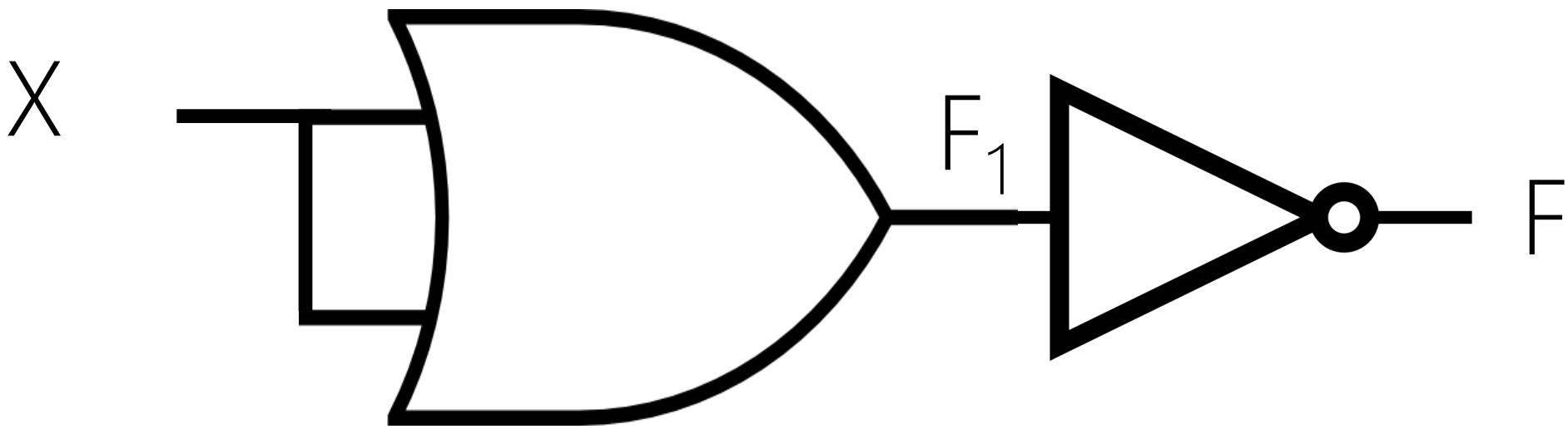

X

$F_1 = X + X$

$F = (X + X)'$

0


0

1

1

1

0

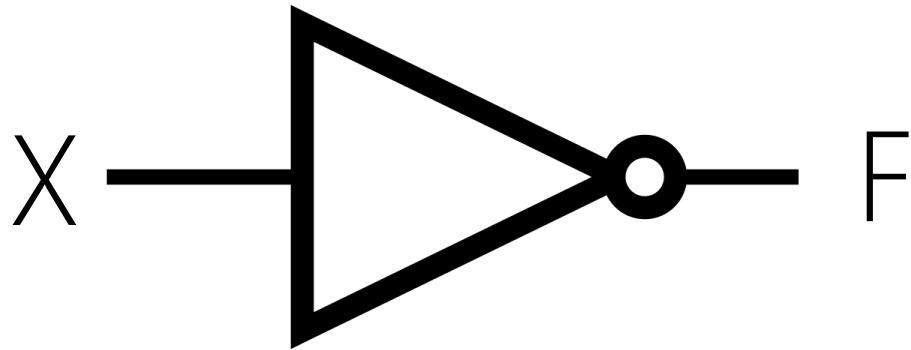

X

$$F = (X+X)' = X \downarrow X = X'$$

0


1

1


0

3-INPUT NOR


Z	Y	X	F=(Z+Y+X)'
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

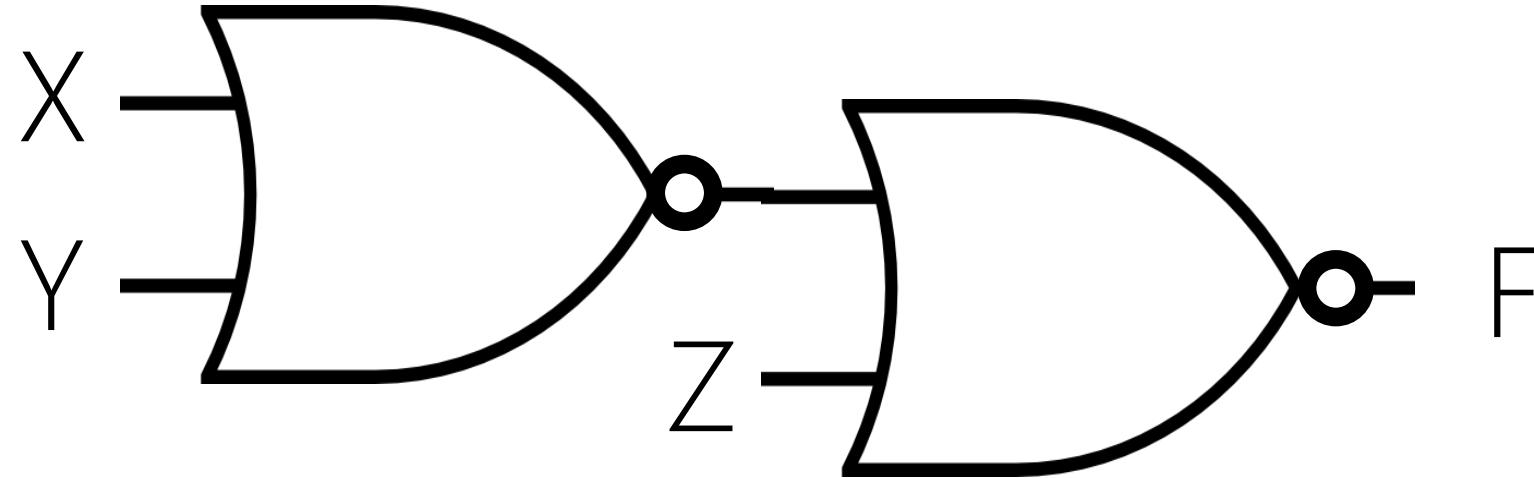

Z	Y	X	F = ?
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

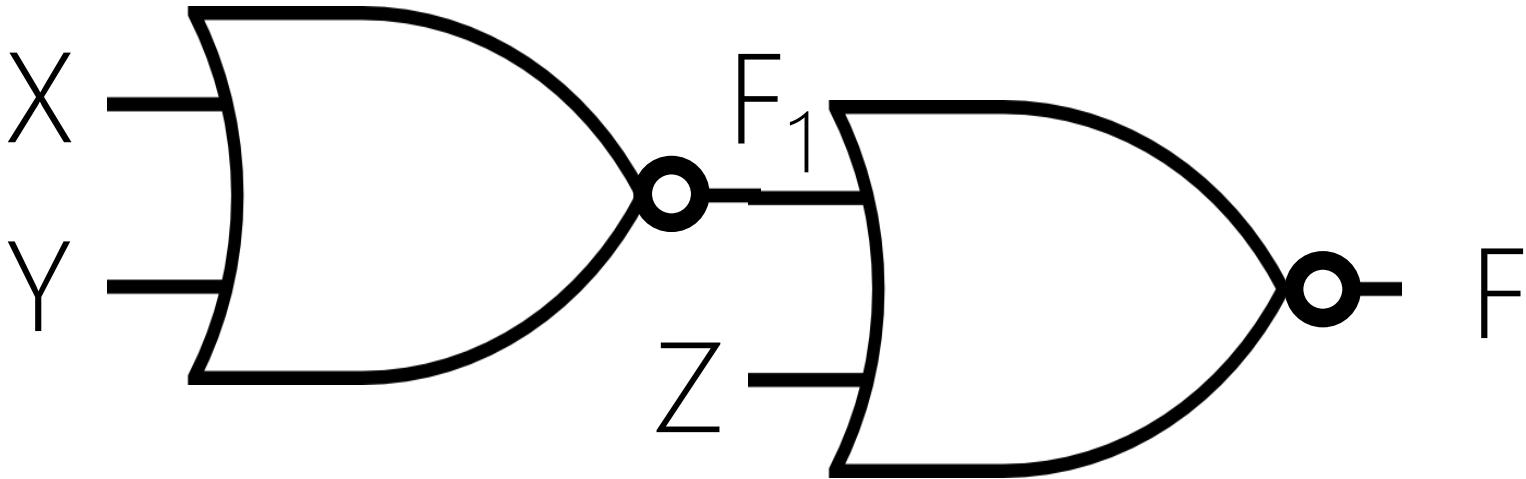


Z	Y	X	$F_1 = (Y+X)'$	$F = (Z+F_1)' = (Z+(Y+X))'$
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

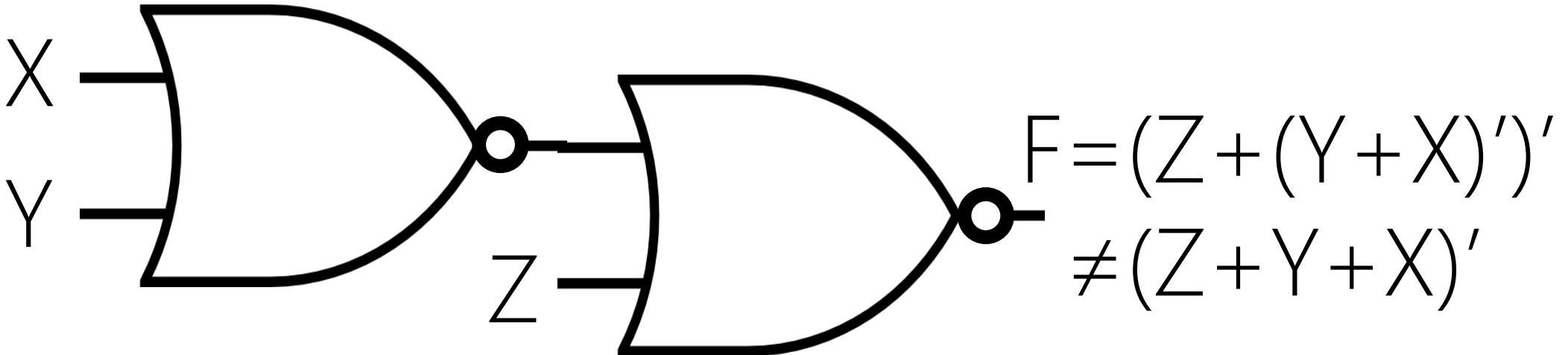


Z	Y	X	$F = (Z+F_1)' = (Z+(Y+X))'$	$F=(Z+Y+X)'$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

NOT (3-INPUT OR)

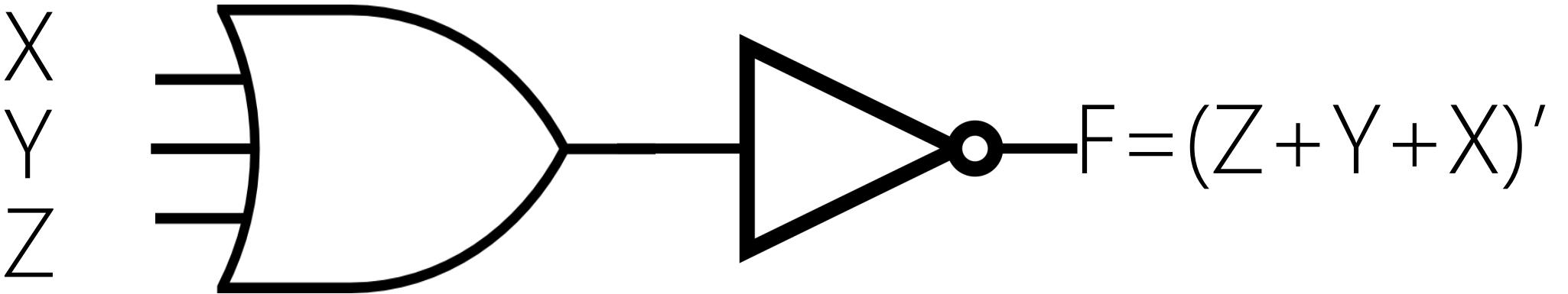

Z	Y	X	$F=(Z+Y+X)'$	$F=(Z+Y+X)'$
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0


X
Y
Z

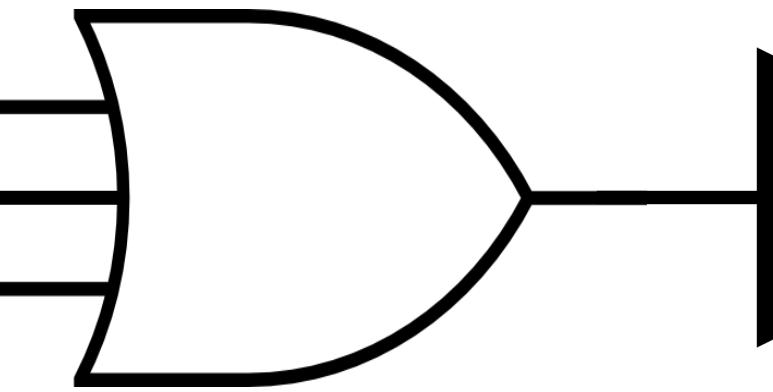


$$F = (Z + Y + X)'$$
$$F = (X + Y + Z)'$$

Associative

Z	Y	X	$F = (Z + Y + X)'$	$F = (Z + Y + X)'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

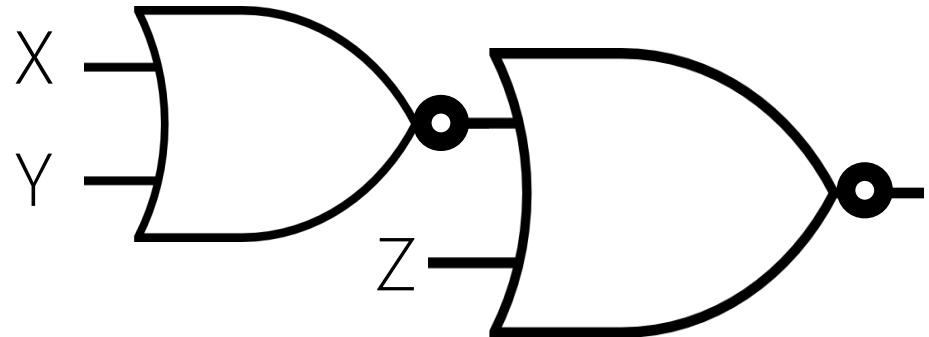


$$F_1 = (Z + (Y + X)')'$$

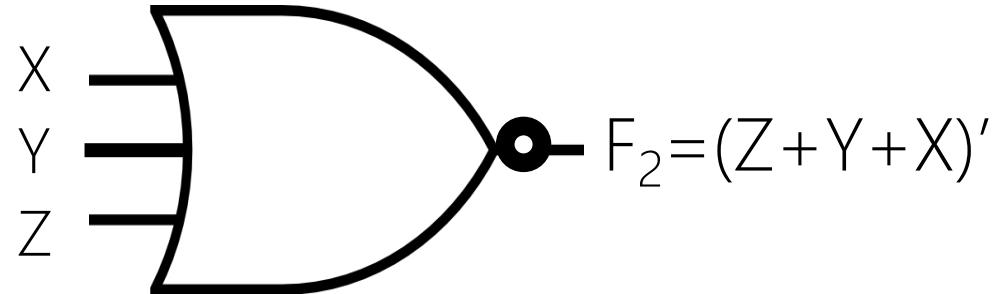

$$F_2 = (Z + Y + X)'$$

$F = (Z+Y+X)'$	F_1	F_2
Effective (True)	No!	Yes
Efficient (Fast)
Min. Cost

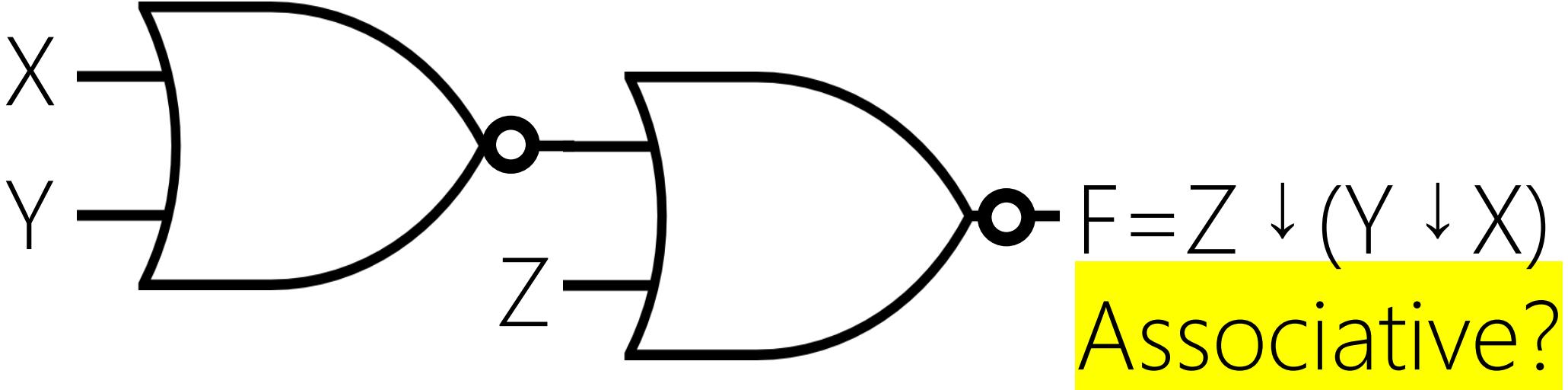

Z	Y	X	$F = (Z(YX)')' = Z \downarrow (Y \downarrow X)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

RECAP

GATE

WHEN F=1

NOT

The input is 0

AND

All the inputs are 1

OR

At least one input is 1

NAND

At least one input is 0

NOR

All the inputs are 0